

CS31001 COMPUTER ORGANIZATION AND ARCHITECTURE

Debdeep Mukhopadhyay,
CSE, IIT Kharagpur

Datapath Elements and Their Designs


Why Datapaths?

- *The speed of these elements often dominates the overall system performance so optimization techniques are important.*
- *However, as we will see, the task is non-trivial since there are multiple equivalent logic and circuit topologies to choose from, each with adv./disadv. in terms of speed, power and area.*
- *Datapath elements include shifters, adders, multipliers, etc.*

Bit-slicing method of constructing ALU

- **Bit slicing** is a technique for constructing a **processor** from modules of smaller bit width.
- Each of these components processes one **bit field** or "slice" of an **operand**.
- The grouped processing components would then have the capability to process the chosen full word-length of a particular software design.

Bit slicing

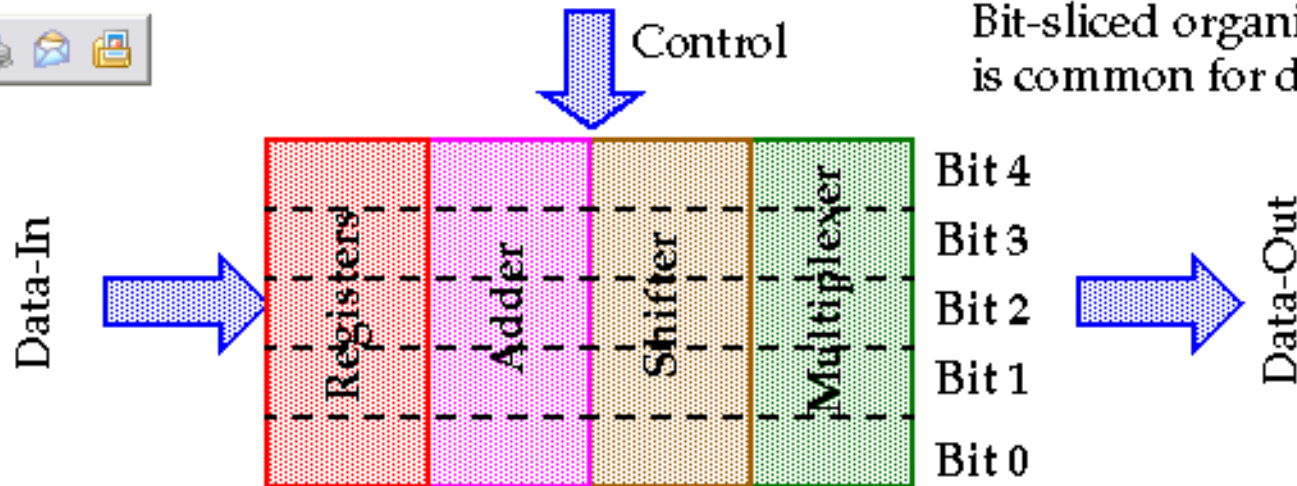

Bit-sliced organization is common for datapaths.

How can we develop architectures which are bit sliced?


Shifters

Sel1	Sel0	Operation	Function
0	0	$Y \leftarrow A$	No shift
0	1	$Y \leftarrow \text{shl}A$	Shift left
1	0	$Y \leftarrow \text{shr}A$	Shift right
1	1	$Y \leftarrow 0$	Zero outputs

What would be a bit sliced architecture of this simple shifter?

Using Muxes

Con[1:0]

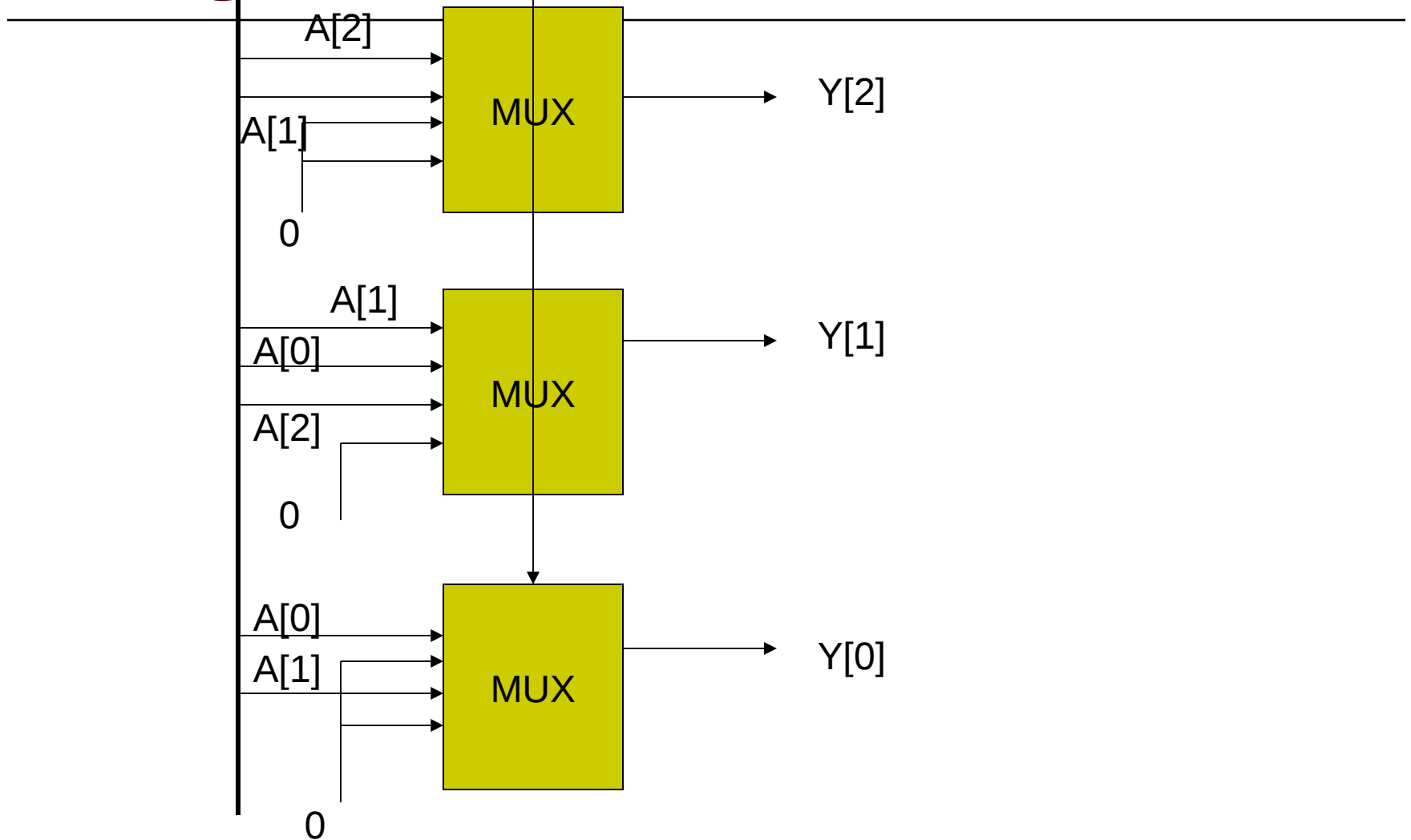

Verilog Code

```
module shifter(Con,A,Y);
    input [1:0] Con;
    input[2:0] A;
    output[2:0] Y;
    reg [2:0] Y;
    always @(A or Con)
    begin
        case(Con)
            0: Y=A;
            1: Y=A<<1;
            2: Y=A>>1;
            default: Y=3'b0;
        endcase
    end
endmodule
```


Combinational logic shifters with shiftin and shiftout

Sel	Operation	Function
0	Y<=A, ShiftLeftOut=0 ShiftRightOut=0	No shift
1	Y<=shl(A), ShiftLeftOut=A[5] ShiftRightOut=0	Shift left
2	Y<=shr(A), ShiftLeftOut=0 ShiftRightOut=A[0]	Shift Right
3	Y<=0, ShiftLeftOut=0 ShiftRightOut=0	Zero Outputs

Verilog Code

```
always@(Sel or A or ShiftLeftIn or ShiftRightIn);
begin
  A_width={ShiftLeftIn,A,ShiftRightIn};
  case(Sel)
    0: Y_width=A_width;
    1: Y_width=A_width<<1;
    2: Y_width=A_width>>1;
    3:Y_width=5'b0;
    default: Y_width=A_width;
  endcase
  ShiftLeftOut=Y_width[0];
  Y=Y_width[2:0];
  ShiftRightOut=Y_width[4];
end
```

Combinational 6 bit Barrel Shifter

Sel	Operation	Function
0	$Y \leq A$	No shift
1	$Y \leftarrow A \text{ rol } 1$	Rotate once
2	$Y \leftarrow A \text{ rol } 2$	Rotate twice
3	$Y \leftarrow A \text{ rol } 3$	Rotate Thrice
4	$Y \leftarrow A \text{ rol } 4$	Rotate four times
5	$Y \leftarrow A \text{ rol } 5$	Rotate five times

Verilog Coding

```
□ function [2:0] rotate_left;
input [5:0] A;
input [2:0] NumberShifts;
reg [5:0] Shifting;
integer N;
begin
    Shifting = A;
    for(N=1;N<=NumberShifts;N=N+1)
        begin
            Shifting={ Shifting[4:0],Shifting[5]};
        end
    rotate_left=Shifting;
end
endfunction
```

Verilog

□ always @(Rotate or A)

begin

case(Rotate)

0: Y=A;

1: Y=rotate_left(A,1);

2: Y=rotate_left(A,2);

3: Y=rotate_left(A,3);

4: Y=rotate_left(A,4);


5: Y=rotate_left(A,5);

default: Y=6'bx;

endcase

end

Another Way

 


Code is left as an exercise...

Single-Bit Addition

Half Adder

$C_{out} =$


A	B	C_o	S
0	0		
0	1		
1	0		
1	1		

 

Full Adder

$S =$
 $C_{out} =$

A	B	C	C_o	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 


Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C_o	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

$$S = A \oplus B \oplus C$$


$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Carry-Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Full adder

- Computes one-bit sum, carry:
 - $s_i = a_i \text{ XOR } b_i \text{ XOR } c_i$
 - $c_{i+1} = a_i b_i + a_i c_i + b_i c_i$
- Half adder computes two-bit sum.
- **Ripple-carry adder**: n-bit adder built from full adders.
- Delay of ripple-carry adder goes through all carry bits.

Verilog for full adder

```
module fulladd(a,b,carryin,sum,carryout);  
    input a, b, carryin; /* add these bits*/  
    output sum, carryout; /* results */  
  
    assign {carryout, sum} = a + b + carryin;  
        /* compute the sum and carry */  
endmodule
```

Verilog for ripple-carry adder

```
module nbitfulladd(a,b,carryin,sum,carryout)
  input [7:0] a, b; /* add these bits */
  input carryin; /* carry in*/
  output [7:0] sum; /* result */
  output carryout;
  wire [7:1] carry; /* transfers the carry between bits */

  fulladd a0(a[0],b[0],carryin,sum[0],carry[1]);
  fulladd a1(a[1],b[1],carry[1],sum[1],carry[2]);
  ...
  fulladd a7(a[7],b[7],carry[7],sum[7],carryout);
endmodule
```

Generate and Propagate

$$G[i] = A[i].B[i]$$

$$P[i] = A[i] \oplus B[i]$$

$$C[i] = G[i] + P[i].C[i-1]$$

$$S[i] = P[i] \oplus C[i-1]$$

$$G[i] = A[i].B[i]$$

$$P[i] = A[i] + B[i]$$

$$C[i] = G[i] + P[i].C[i-1]$$

$$S[i] = A[i] \oplus B[i] \oplus C[i-1]$$

Two methods to develop C[i] and S[i].

Both are correct

- Because, $A[i]=1$ and $B[i]=1$ (which may lead to a difference is taken care of by the term $A[i]B[i]$)
- How do we make an n bit adder?
- The delay of the adder chain needs to be optimized.


Carry-lookahead adder

- First compute carry propagate, generate:
 - $P_i = a_i + b_i$
 - $G_i = a_i b_i$
- Compute sum and carry from P and G:
 - $s_i = c_i \text{ XOR } P_i \text{ XOR } G_i$
 - $c_{i+1} = G_i + P_i c_i$

Carry-lookahead expansion

- Can recursively expand carry formula:
 - $c_{i+1} = G_i + P_i(G_{i-1} + P_{i-1}c_{i-1})$
 - $c_{i+1} = G_i + P_iG_{i-1} + P_iP_{i-1}(G_{i-2} + P_{i-1}c_{i-2})$
- Expanded formula does not depend on intermediate carries.
- Allows carry for each bit to be computed independently.

Depth-4 carry-lookahead

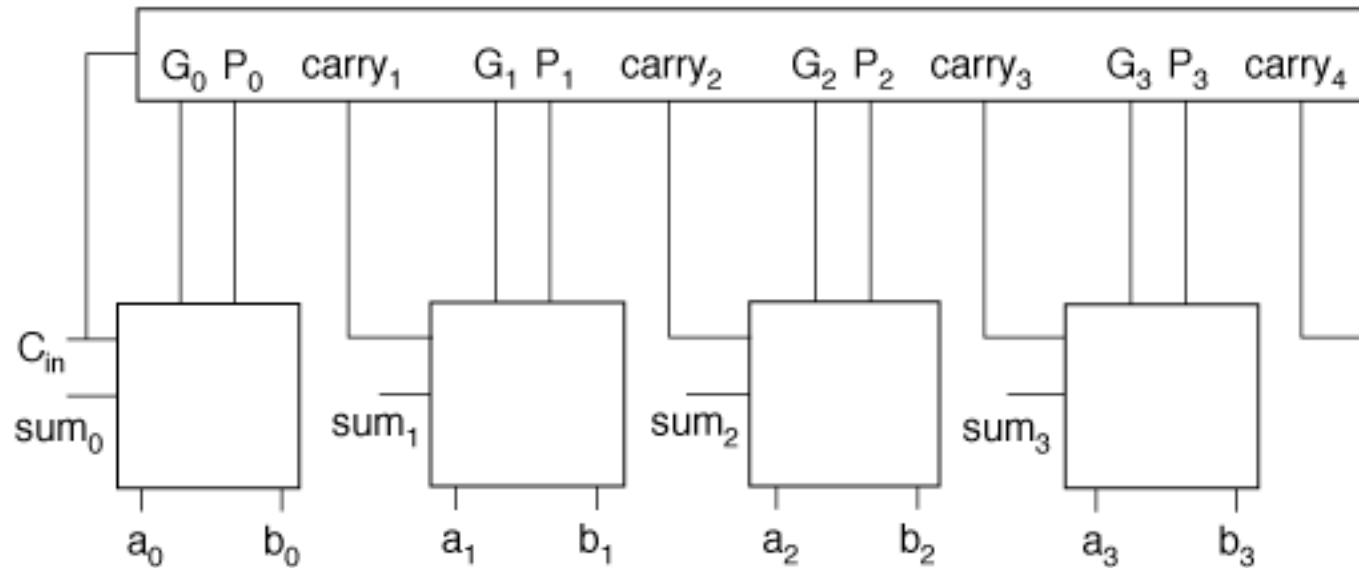

Analysis

- As we look ahead further logic becomes complicated.
- Takes longer to compute
- Becomes less regular.
- There is no similarity of logic structure in each cell.
- We have developed CLA adders, like Brent-Kung adder.

Verilog for carry-lookahead carry block

```
module carry_block(a,b,carryin,carry);
    input [3:0] a, b; /* add these bits*/
    input carryin; /* carry into the block */
    output [3:0] carry; /* carries for each bit in the block */
    wire [3:0] g, p; /* generate and propagate */

    assign g[0] = a[0] & b[0]; /* generate 0 */
    assign p[0] = a[0] ^ b[0]; /* propagate 0 */
    assign g[1] = a[1] & b[1]; /* generate 1 */
    assign p[1] = a[1] ^ b[1]; /* propagate 1 */

    ...

    assign carry[0] = g[0] | (p[0] & carryin);
    assign carry[1] = g[1] | p[1] & (g[0] | (p[0] & carryin));
    assign carry[2] = g[2] | p[2] &
        (g[1] | p[1] & (g[0] | (p[0] & carryin)));
    assign carry[3] = g[3] | p[3] &
        (g[2] | p[2] & (g[1] | p[1] & (g[0] | (p[0] & carryin))));

    □ endmodule
```

$$c_{i+1} = G_i + P_i(G_{i-1} + P_{i-1}c_{i-1})$$

Verilog for carry-lookahead sum unit

```
module sum(a,b,carryin,result);  
    input a, b, carryin; /* add these bits*/  
    output result; /* sum */  
  
    assign result = a ^ b ^ carryin;  
        /* compute the sum */  
endmodule
```

Verilog for carry-lookahead adder

```
□ module carry_lookahead_adder(a,b,carryin,sum,carryout);
  input [15:0] a, b; /* add these together */
  input carryin;
  output [15:0] sum; /* result */
  output carryout;
  wire [16:1] carry; /* intermediate carries */

  assign carryout = carry[16]; /* for simplicity */
  /* build the carry-lookahead units */
  carry_block b0(a[3:0],b[3:0],carryin,carry[4:1]);
  carry_block b1(a[7:4],b[7:4],carry[4],carry[8:5]);
  carry_block b2(a[11:8],b[11:8],carry[8],carry[12:9]);
  carry_block b3(a[15:12],b[15:12],carry[12],carry[16:13]);
  /* build the sum */
  sum a0(a[0],b[0],carryin,sum[0]);
  sum a1(a[1],b[1],carry[1],sum[1]);
  ...
  sum a15(a[15],b[15],carry[15],sum[15]);
endmodule
```




Dealing with the problem of carry propagation

1. Reduce the carry propagation time.
2. To detect the completion of the carry propagation time.

We have seen some ways to do the former. How do we do the second one?


Motivation

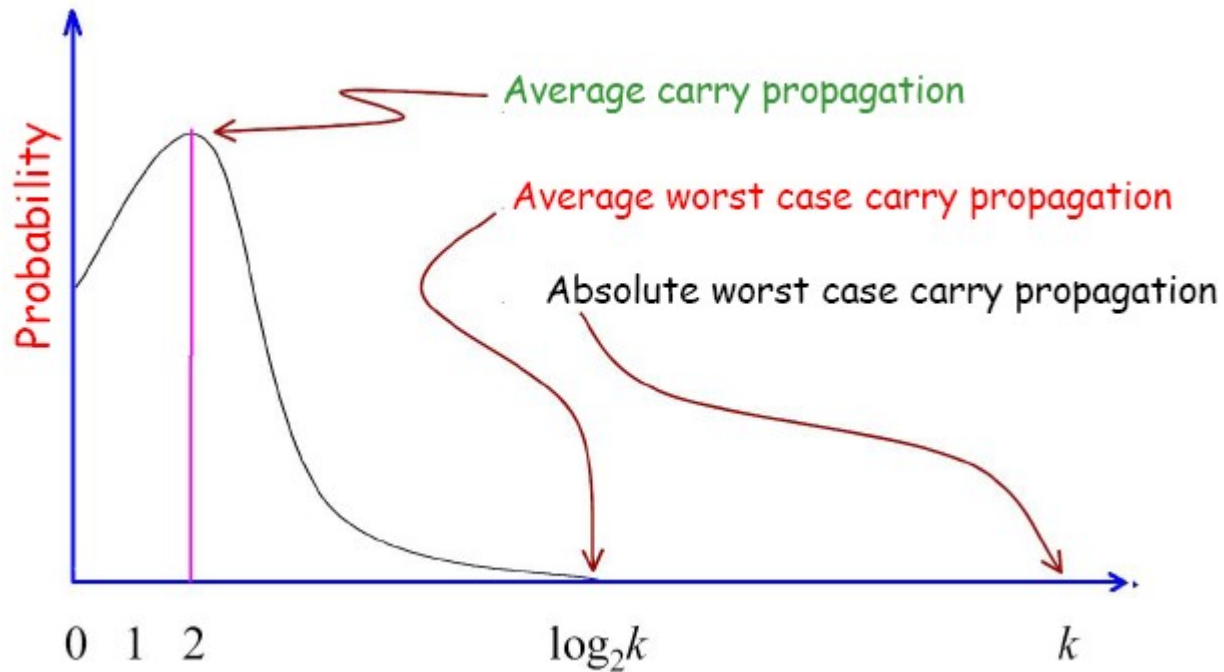

Carry Completion Sensing

A = **0** 0 1 1 **1** 0 **1** 1 **0** 1 1 0 1 **1** 0 **1**

 B = **0** 1 0 0 **1** 1 **1** 0 **0** 0 0 1 0 **1** 0 **1**



Can we compute the average length of carry chain?

- What is the probability that a chain generated at position i terminates at j ?
 - It terminates if both the inputs $A[j]$ and $B[j]$ are zero or 1.
 - From $i+1$ to $j-1$ the carry has to propagate.
 - $p=(1/2)^{j-i}$
 - So, what is the expected length?
 - Define a random variable L , which denotes the length of the chain.

Expected length

- The chain can terminate at $j=i+1$ to $j=k$ (the MSB position of the adder)
- Thus $L=j-i$ for a choice of j .
- Thus expected length is: **approximately 2!**

$$\sum_{j=i+1}^{k-1} (j-i)2^{-(j-i)} + (k-i)2^{-(k-1-i)}$$

(the carry definitely ends at position k , so we do not multiply $2^{-(k-1-i)}$ with $1/2$.)

$$\begin{aligned} &= \sum_{l=1}^{k-1-i} l2^{-l} + (k-i)2^{-(k-1-i)} = 2 - (k-i+1)2^{-(k-1-i)} + (k-i)2^{-(k-1-i)} \\ &= 2 - 2^{-(k-1-i)} \end{aligned}$$

$$[\text{Using, } \sum_{l=1}^p l2^{-l} = 2 - (p+2)2^{-p}]$$

Carry completion sensing adder

A=011101101101101

B=100111000010101

C=000000000000000

N=000000000000000

C=000101000000101

N=000000010000010

A=011101101101101

B=100111000010101

C=000101000000101

N=000000010000010

C=001111000001101

N=000000110000010

Carry completion sensing adder

A=011101101101101

B=100111000010101

C=001111000001101

N=000000110000010

C=011111000011101

N=000000110000010

A=011101101101101

B=100111000010101

C=011111000011101

N=000000110000010

C=111111000111101

N=000000110000010

Carry completion sensing adder

A=011101101101101

B=100111000010101

C=111111000111101

N=000000110000010

-

C=111111001111101

N=000000110000010

Carry completion sensing adder

- $(A[i], B[i]) = (0, 0) \Rightarrow (C_i, N_i) = (0, 1)$
- $(A[i], B[i]) = (1, 1) \Rightarrow (C_i, N_i) = (1, 0)$
- $(A[i], B[i]) = (0, 1) \Rightarrow (C_i, N_i) = (C_{i-1}, N_{i-1})$
- $(A[i], B[i]) = (1, 0) \Rightarrow (C_i, N_i) = (C_{i-1}, N_{i-1})$
- Stop, when for all i , $C_i \vee N_i = 1$


Justification

- C_i and N_i together is a coding for the carry.
- When $C_i=1$, carry can be computed. Make $N_i=0$
- When $C_i=0$ is the final carry, then indicate by $N_i=1$
- The carry can be surely stated when both A_i and B_i are 1's or 0's.


Carry-skip adder

- Looks for cases in which carry out of a set of bits is identical to carry in.
- Typically organized into b -bit stages.
- Can bypass carry through all stages in a group when all propagates are true: $P_i P_{i+1} \dots P_{i+b-1}$.
 - Carry out of group when carry out of last bit in group or carry is bypassed.

Carry-skip structure

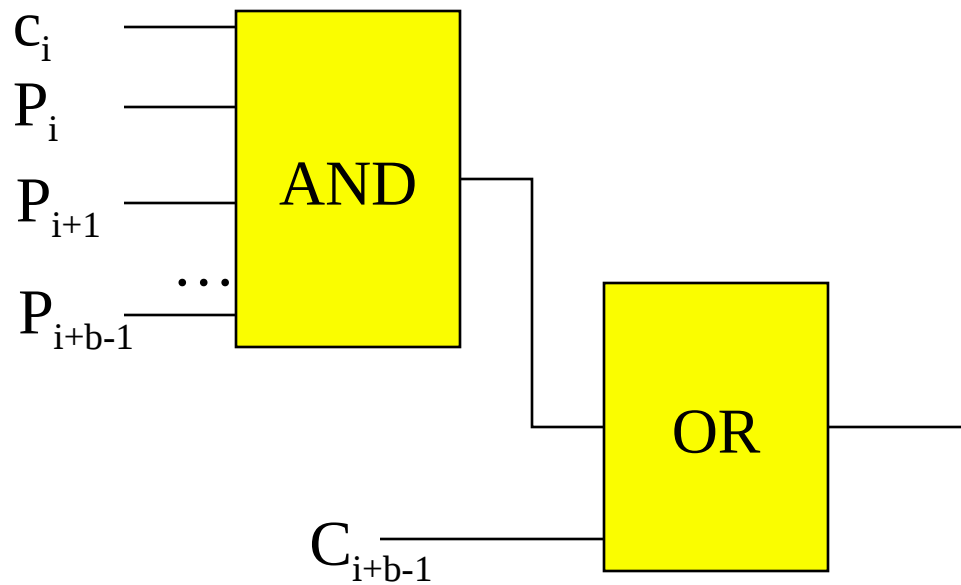


Carry-skip structure

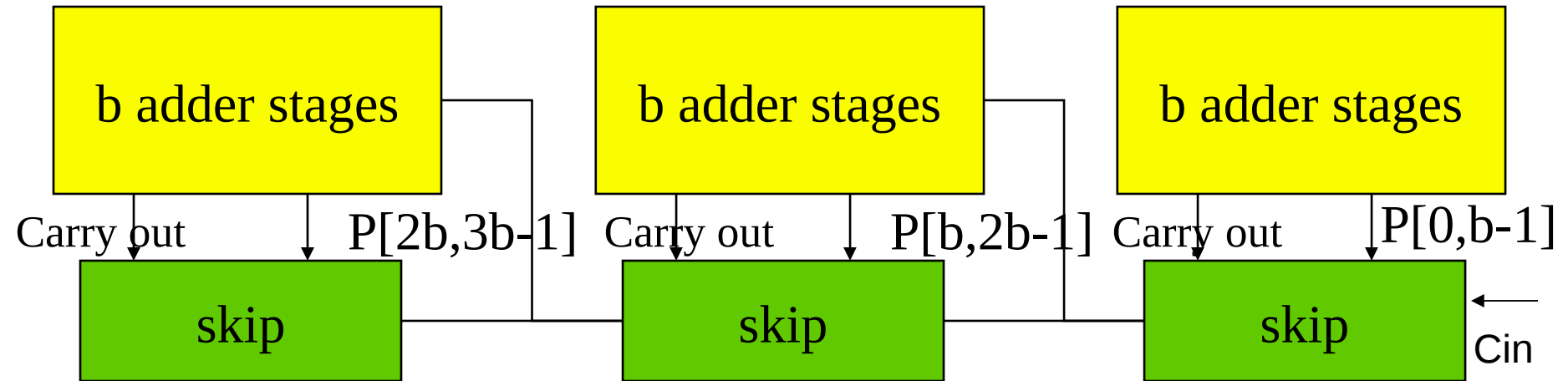

Worst-case carry-skip

 - Worst-case carry-propagation path goes through first, last stages:



Verilog for carry-skip add with P

```
module fulladd_p(a,b,carryin,sum,carryout,p);
    input a, b, carryin; /* add these bits*/
    output sum, carryout, p; /* results including propagate */

    assign {carryout, sum} = a + b + carryin;
        /* compute the sum and carry */
    assign p = a ^ b;
endmodule
```

Want to use ripple carry adder for the blocks

```
module fulladd_p(a,b,carryin,sum,carryout,p);  
    input a, b, carryin; /* add these bits*/  
    output sum, carryout, p; /* results including propagate */  
    $rtl_binding="ADD3_RPL";  
    assign {carryout, sum} = a + b + carryin;  
        /* compute the sum and carry */  
    assign p = a ^ b;  
endmodule
```



Directive to a synthesis tool!

Verilog for carry-skip adder

```
module carryskip(a,b,carryin,sum,carryout);
    input [7:0] a, b; /* add these bits */
    input carryin; /* carry in*/
    output [7:0] sum; /* result */
    output carryout;
    wire [8:1] carry; /* transfers the carry between bits */
    wire [7:0] p; /* propagate for each bit */
    wire cs4; /* final carry for first group */


    fulladd_p a0(a[0],b[0],carryin,sum[0],carry[1],p[0]);
    fulladd_p a1(a[1],b[1],carry[1],sum[1],carry[2],p[1]);
    fulladd_p a2(a[2],b[2],carry[2],sum[2],carry[3],p[2]);
    fulladd_p a3(a[3],b[3],carry[3],sum[3],carry[4],p[3]);
    assign cs4 = carry[4] | (p[0] & p[1] & p[2] & p[3] & carryin);
    fulladd_p a4(a[4],b[4],cs4, sum[4],carry[5],p[4]);

    ...
    assign carryout = carry[8] | (p[4] & p[5] & p[6] & p[7] & cs4);
endmodule
```

Delay analysis

- Assume that skip delay = 1 bit carry delay.
- Delay of k-bit adder with block size b:
 - $T = (b-1) + 0.5 + (k/b - 2) + (b-1)$
block 0 OR gate skips last block
- For equal sized blocks, optimal block size is $\sqrt{k/2}$.

Delay of Carry-Skip Adder

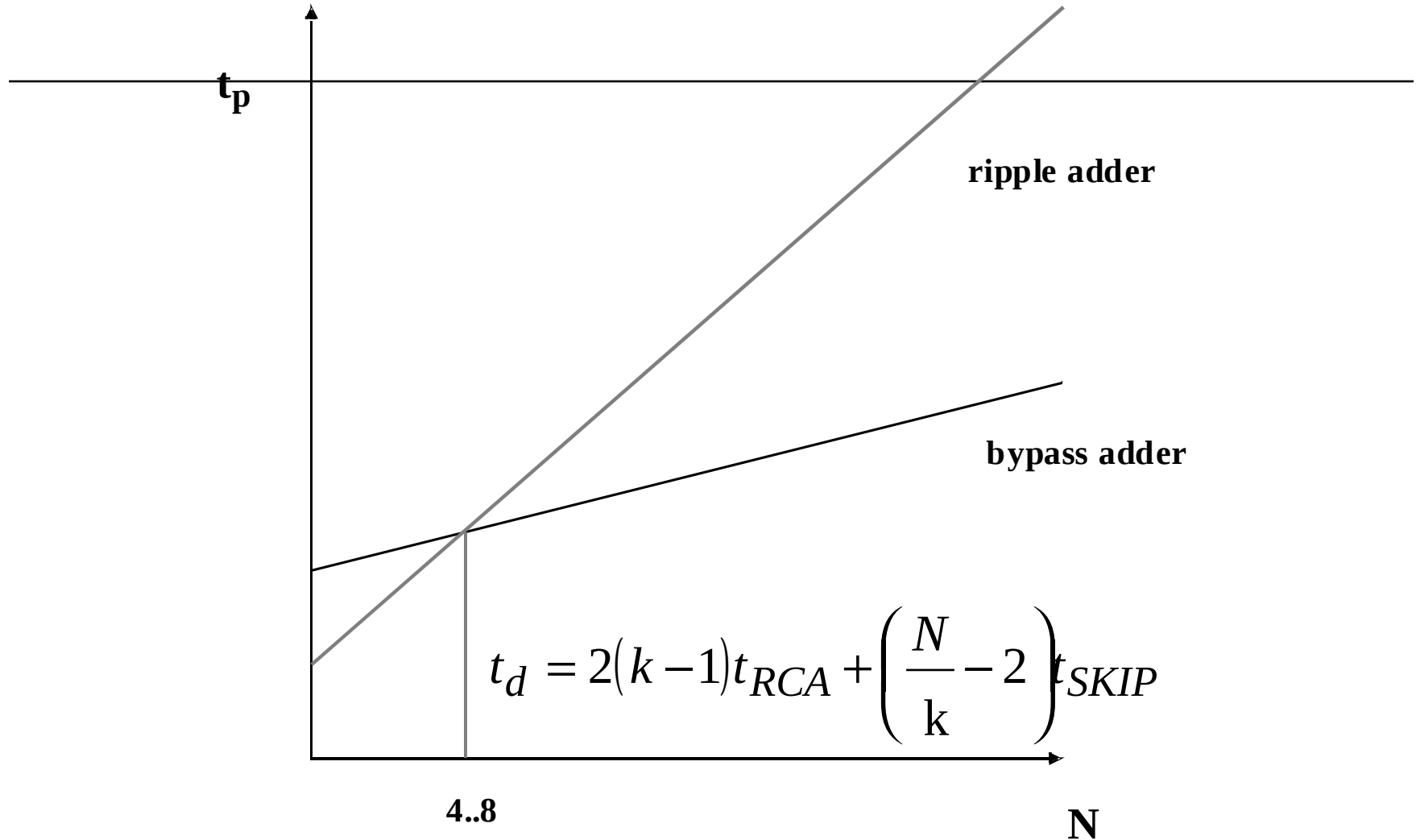




Carry-select adder

- Computes two results in parallel, each for different carry input assumptions.
- Uses actual carry in to select correct result.
- Reduces delay to multiplexer.

Carry-select structure

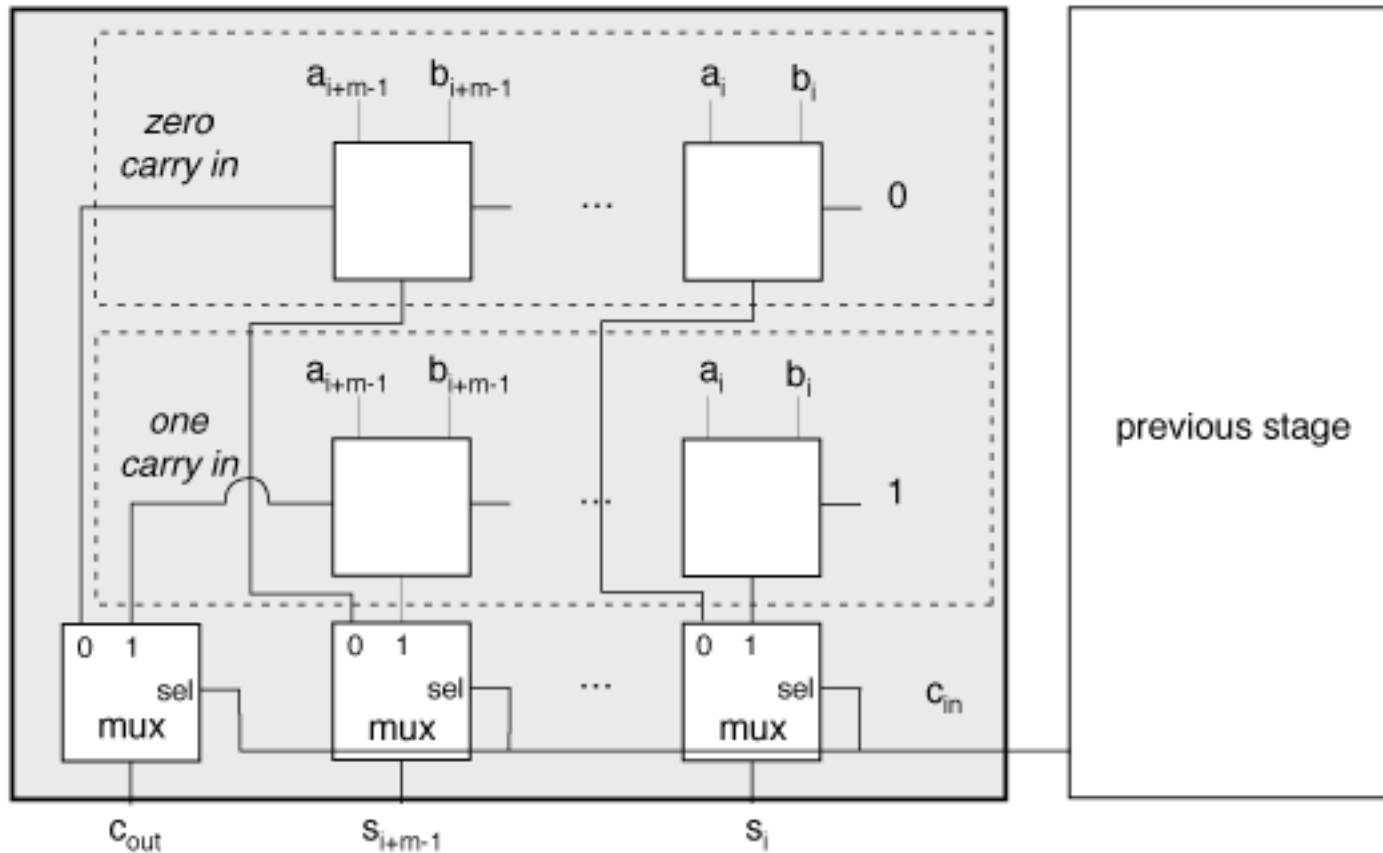


Carry-save adder

- Useful in multiplication.
- Input: 3 n-bit operands.
- Output: n-bit partial sum, n-bit carry.
 - Use carry propagate adder for final sum.
- Operations:
 - $s = (x + y + z) \bmod 2$.
 - $c = [(x + y + z) - 2] / 2$.


Carry Network is the Essence of a Fast Adder

g_i	p_i	Carry is:
0	0	annihilated or killed
0	1	propagated
1	0	generated
1	1	(impossible)

 

$$g_i = x_i y_i$$

$$p_i = x_i \oplus y_i$$

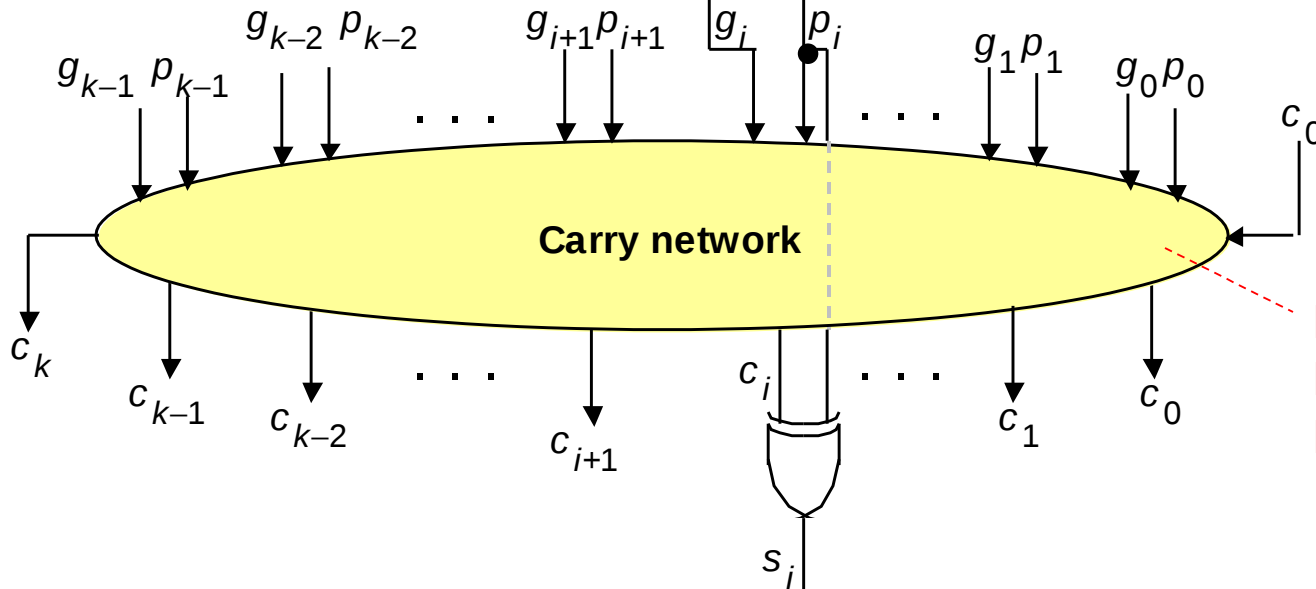

Ripple;
Skip;
Lookahead;
Parallel-prefix


Generic structure of a binary adder, highlighting its carry network.

Ripple-Carry Adder Revisited

The carry recurrence: $c_{i+1} = g_i \vee p_i c_i$

Latency of k -bit adder is roughly $2k$ gate delays:

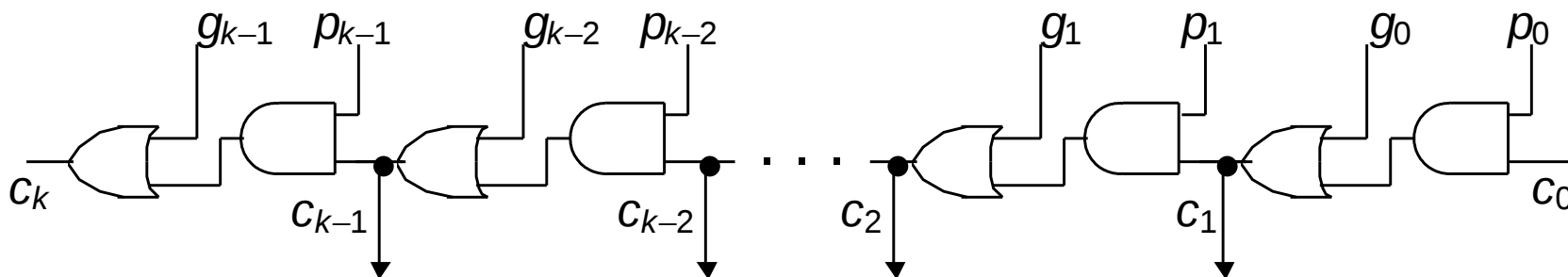1 gate delay for production of p and g signals, plus
 $2(k - 1)$ gate delays for carry propagation, plus
1 XOR gate delay for generation of the sum bits




Alternate view of a ripple-carry network in connection with the generic adder structure shown in Fig. 5.14.

The Complete Design of a Ripple-Carry Adder

g_i	p_i	Carry is:
0	0	annihilated or killed
0	1	propagated
1	0	generated
1	1	(impossible)

$$g_i = x_i y_i$$

$$p_i = x_i \oplus y_i$$

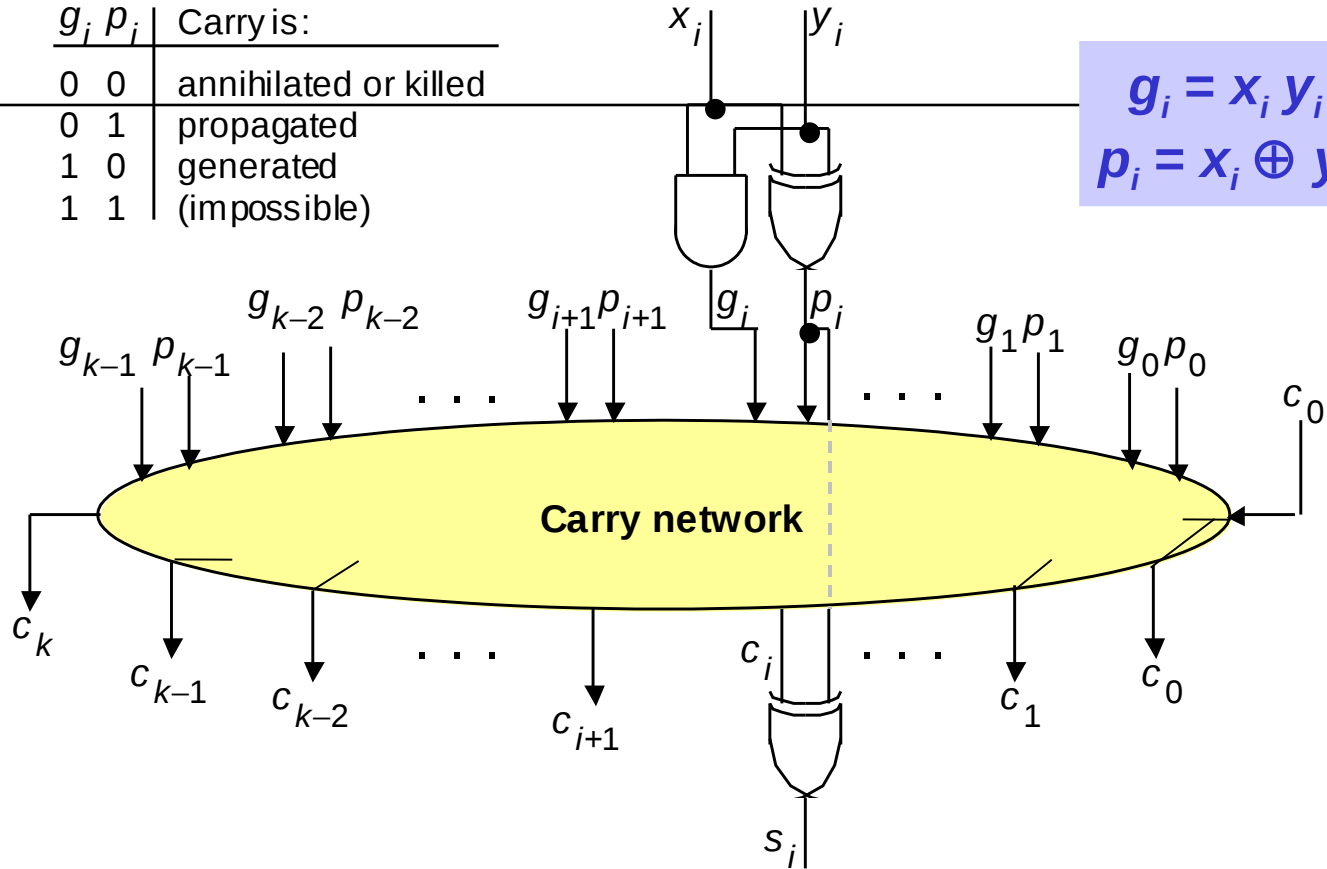

6.1 Unrolling the Carry Recurrence

Recall the *generate*, *propagate*, *annihilate (absorb)*, and *transfer* signals:


Signal	Radix r	Binary
g_i	is 1 iff $x_i + y_i \geq r$	$x_i y_i$
p_i	is 1 iff $x_i + y_i = r - 1$	$x_i \oplus y_i$
a_i	is 1 iff $x_i + y_i < r - 1$	$x_i' y_i' = (x_i \vee y_i)'$
t_i	is 1 iff $x_i + y_i \geq r - 1$	$x_i \vee y_i$
s_i	$(x_i + y_i + c_i) \bmod r$	$x_i \oplus y_i \oplus c_i$

The carry recurrence can be unrolled to obtain each carry signal directly from inputs, rather than through propagation

$$\begin{aligned}c_i &= g_{i-1} \vee c_{i-1} p_{i-1} \\ &= g_{i-1} \vee (g_{i-2} \vee c_{i-2} p_{i-2}) p_{i-1} \\ &= g_{i-1} \vee g_{i-2} p_{i-1} \vee c_{i-2} p_{i-2} p_{i-1} \\ &= g_{i-1} \vee g_{i-2} p_{i-1} \vee g_{i-3} p_{i-2} p_{i-1} \vee c_{i-3} p_{i-3} p_{i-2} p_{i-1} \\ &= g_{i-1} \vee g_{i-2} p_{i-1} \vee g_{i-3} p_{i-2} p_{i-1} \vee g_{i-4} p_{i-3} p_{i-2} p_{i-1} \vee c_{i-4} p_{i-4} p_{i-3} p_{i-2} p_{i-1} \\ &= \dots\end{aligned}$$

Note:
Addition symbol
vs logical OR

Full Carry Lookahead

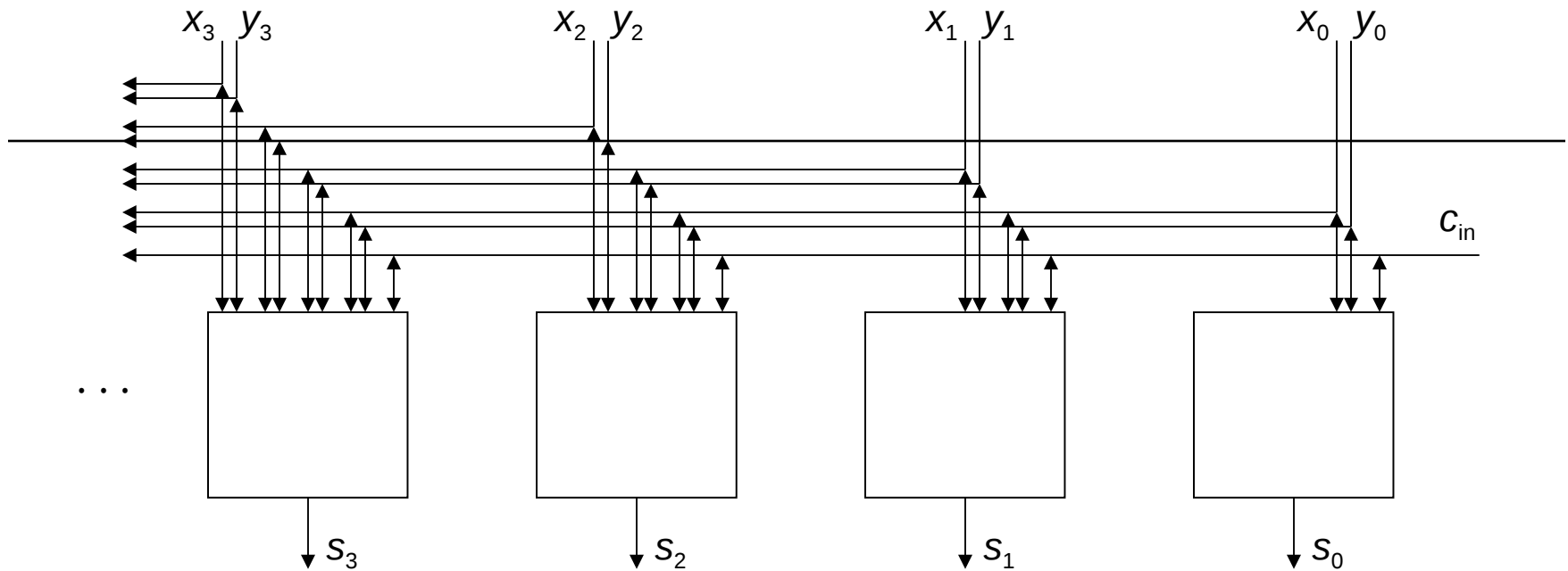

Theoretically, it is possible to derive each sum digit directly from the inputs that affect it

Carry-lookahead adder design is simply a way of reducing the complexity of this ideal, but impractical, arrangement by hardware sharing among the various lookahead circuits

Four-Bit Carry-Lookahead Adder

Complexity
reduced by
deriving the
carry-out
indirectly


Full carry lookahead is quite practical
for a 4-bit adder

$$c_1 = g_0 \vee c_0 p_0$$

$$c_2 = g_1 \vee g_0 p_1 \vee c_0 p_0 p_1$$

$$c_3 = g_2 \vee g_1 p_2 \vee g_0 p_1 p_2 \vee c_0 p_0 p_1 p_2$$
 
$$c_4 = g_3 \vee g_2 p_3 \vee g_1 p_2 p_3 \vee g_0 p_1 p_2 p_3 \\ \vee c_0 p_0 p_1 p_2 p_3$$



Four-bit carry network with
full lookahead.

Carry Lookahead Beyond 4 Bits

Consider a 32-bit adder

$$c_1 = g_0 \vee c_0 p_0$$

$$c_2 = g_1 \vee g_0 p_1 \vee c_0 p_0 p_1$$

$$c_3 = g_2 \vee g_1 p_2 \vee g_0 p_1 p_2 \vee c_0 p_0 p_1 p_2$$

⋮
⋮
⋮

$$c_{31} = g_{30} \vee g_{29} p_{30} \vee g_{28} p_{29} p_{30} \vee g_{27} p_{28} p_{29} p_{30} \vee \dots \vee c_0 p_0 p_1 p_2 p_3 \dots p_{29} p_{30}$$

No circuit sharing:
Repeated computations

32-input AND

32-input OR

High fan-ins necessitate
tree-structured circuits

Solution to the Fan-in Problem

High-radix addition (i.e., radix 2^h)

Increases the latency for generating g and p signals and sum digits, but simplifies the carry network (optimal radix?)


Multilevel lookahead

Example: 16-bit addition

Radix-16 (four digits)

Two-level carry lookahead (four 4-bit blocks)

 Either way, the carries c_4 , c_8 , and c_{12} are determined first




Carry-Lookahead Adder Design

Block *generate* and *propagate* signals

$$g_{[j,i+3]} = g_{i+3} \vee g_{i+2}p_{i+3} \vee g_{i+1}p_{i+2}p_{i+3} \vee g_i p_{i+1}p_{i+2}p_{i+3}$$



 
$$p_{[j,i+3]} = p_i p_{i+1} p_{i+2} p_{i+3}$$



Schematic diagram of a 4-bit lookahead carry generator.

$P_{[i,i+3]}$

  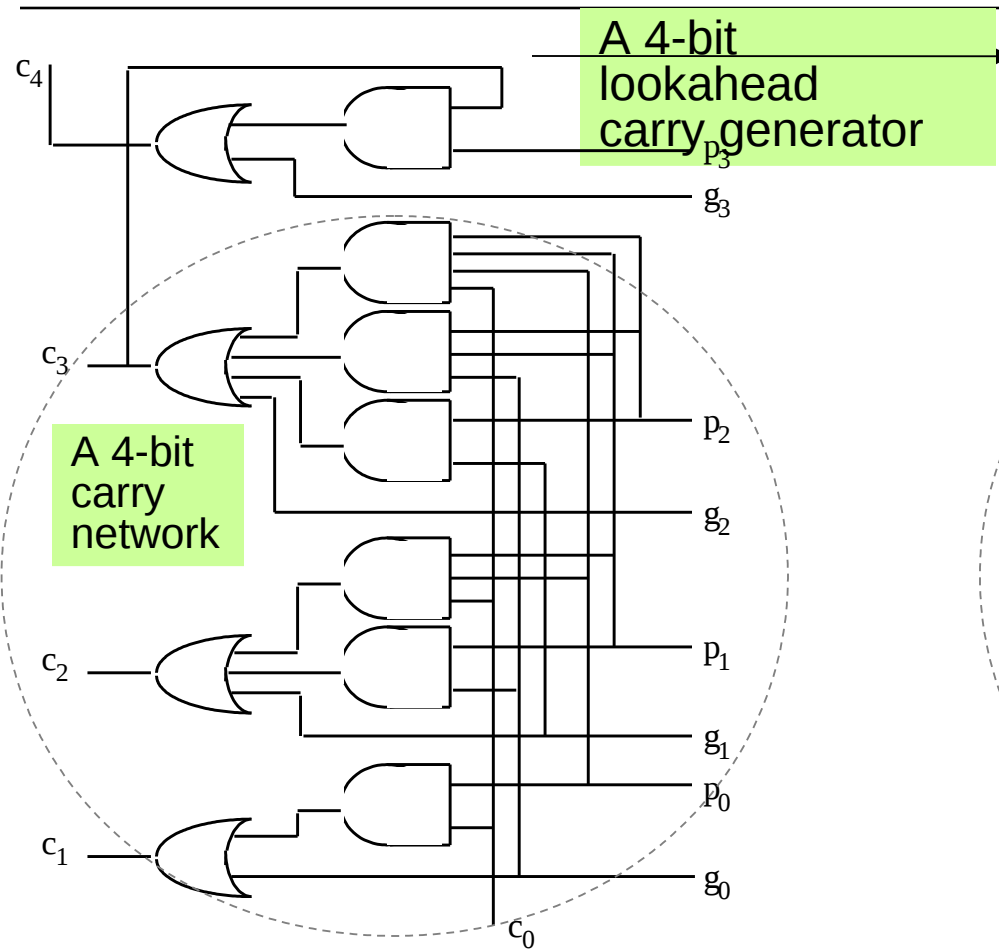A Building Block for Carry-Lookahead Addition



Combining Block g and p Signals

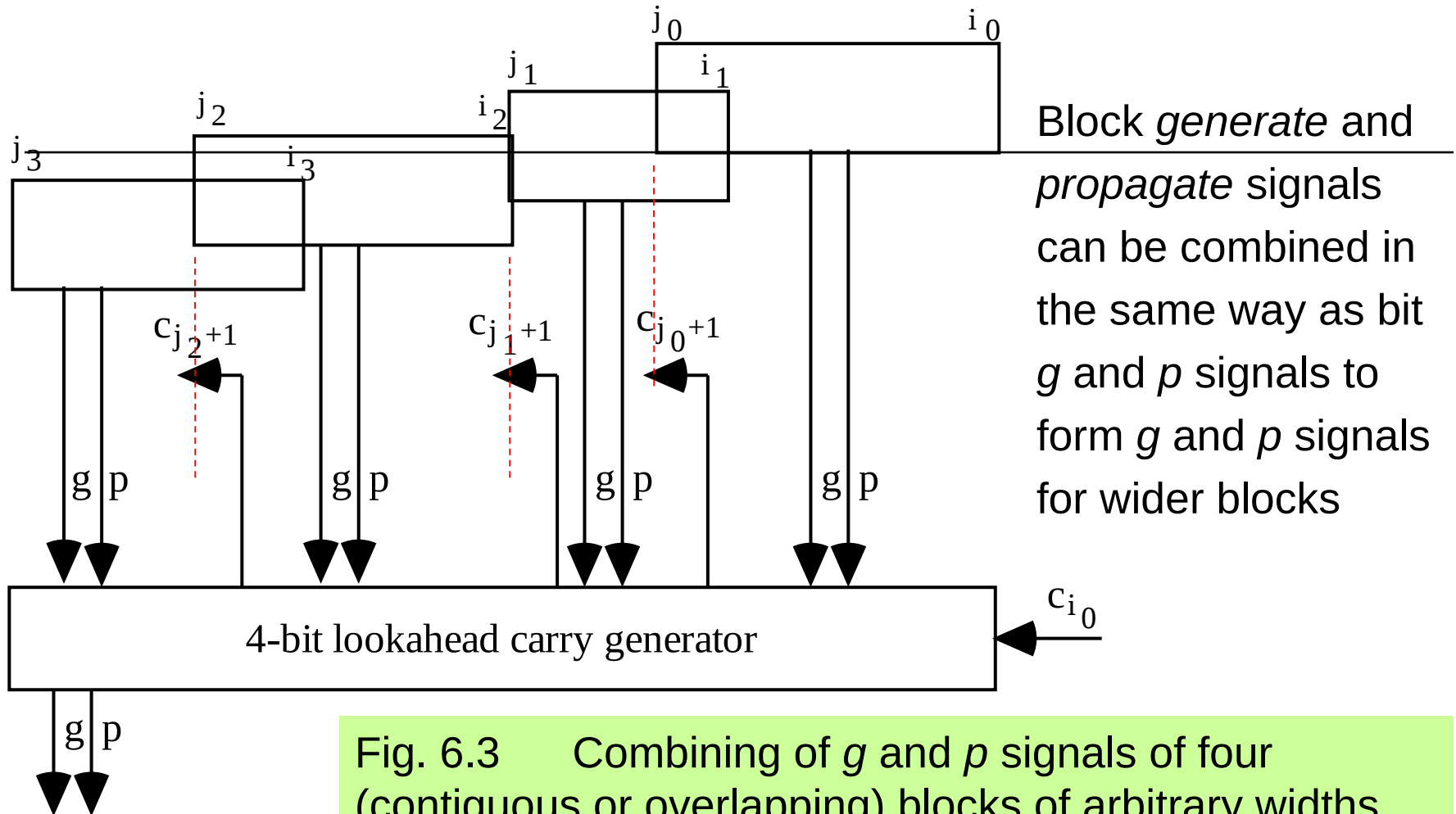


Fig. 6.3 Combining of g and p signals of four (contiguous or overlapping) blocks of arbitrary widths into the g and p signals for the overall block $[i_0, j_3]$.

A Two-Level Carry-Lookahead Adder

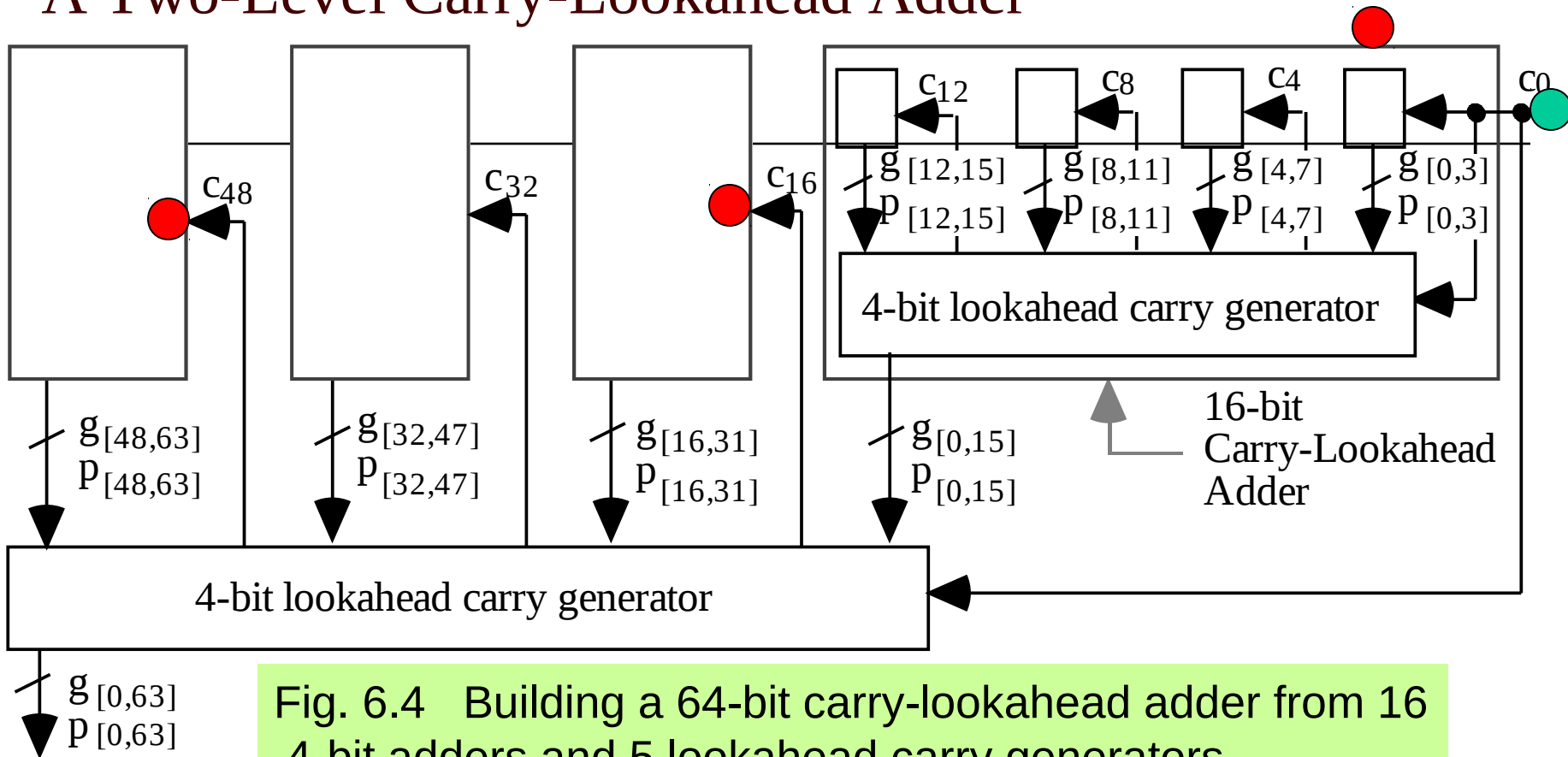


Fig. 6.4 Building a 64-bit carry-lookahead adder from 16 4-bit adders and 5 lookahead carry generators.

Carry-out:
$$c_{out} = g_{[0,k-1]} \vee c_0 p_{[0,k-1]} = x_{k-1} y_{k-1} \vee s_{k-1}' (x_{k-1} \vee y_{k-1})$$

Latency of a Multilevel Carry-Lookahead Adder

Latency through the 16-bit CLA adder consists of finding:

g and p for individual bit positions	1 gate level
g and p signals for 4-bit blocks	2 gate levels
Block carry-in signals c_4 , c_8 , and c_{12}	2 gate levels
Internal carries within 4-bit blocks	2 gate levels
Sum bits	2 gate levels


Total latency for the 16-bit adder 9 gate levels

(compare to 32 gate levels for a 16-bit ripple-carry adder)

Each additional lookahead level adds 4 gate levels of latency

Latency for k -bit CLA adder: $T_{\text{lookahead-add}} = 4 \log_4 k + 1$ gate levels

 Carry Determination as Prefix Computation



Combining of g and p signals of two (contiguous or overlapping) blocks B' and B'' of arbitrary widths into the g and p signals for block B .

Formulating the Prefix Computation Problem

The problem of carry determination can be formulated as:

Given $(g_0, p_0)(g_1, p_1) \dots (g_{k-2}, p_{k-2}) \quad (g_{k-1}, p_{k-1})$

Find $(g_{[0,0]}, p_{[0,0]}) \quad (g_{[0,1]}, p_{[0,1]}) \dots (g_{[0,k-2]}, p_{[0,k-2]}) \quad (g_{[0,k-1]}, p_{[0,k-1]})$
 $c_1 \quad c_2 \quad \dots \quad c_{k-1} \quad c_k$

Carry-in can be viewed as an extra (-1) position: $(g_{-1}, p_{-1}) = (c_{in}, 0)$

The desired pairs are found by evaluating all prefixes of

~~(g_0, p_0)~~ Φ ~~(g_1, p_1)~~ Φ \dots Φ (g_{k-2}, p_{k-2}) Φ (g_{k-1}, p_{k-1}) \rightarrow

The carry operator Φ is associative, but not commutative

$$[(g_1, p_1) \Phi (g_2, p_2)] \Phi (g_3, p_3) = (g_1, p_1) \Phi [(g_2, p_2) \Phi (g_3, p_3)]$$

Prefix sums analogy:

Given $x_0 \quad x_1 \quad x_2 \quad \dots \quad x_{k-1}$

Apr. 2012

Computer Arithmetic, Addition/Subtraction

Slide 66

Find $x_0 \quad x_0+x_1 \quad x_0+x_1+x_2 \quad \dots \quad x_0+x_1+\dots+x_{k-1}$

Example Prefix-Based Carry Network



 
 


Fig. 6.6 Four-input parallel prefix sums network and its corresponding carry network.

 


Brent-Kung Carry Network (8-Bit Adder)

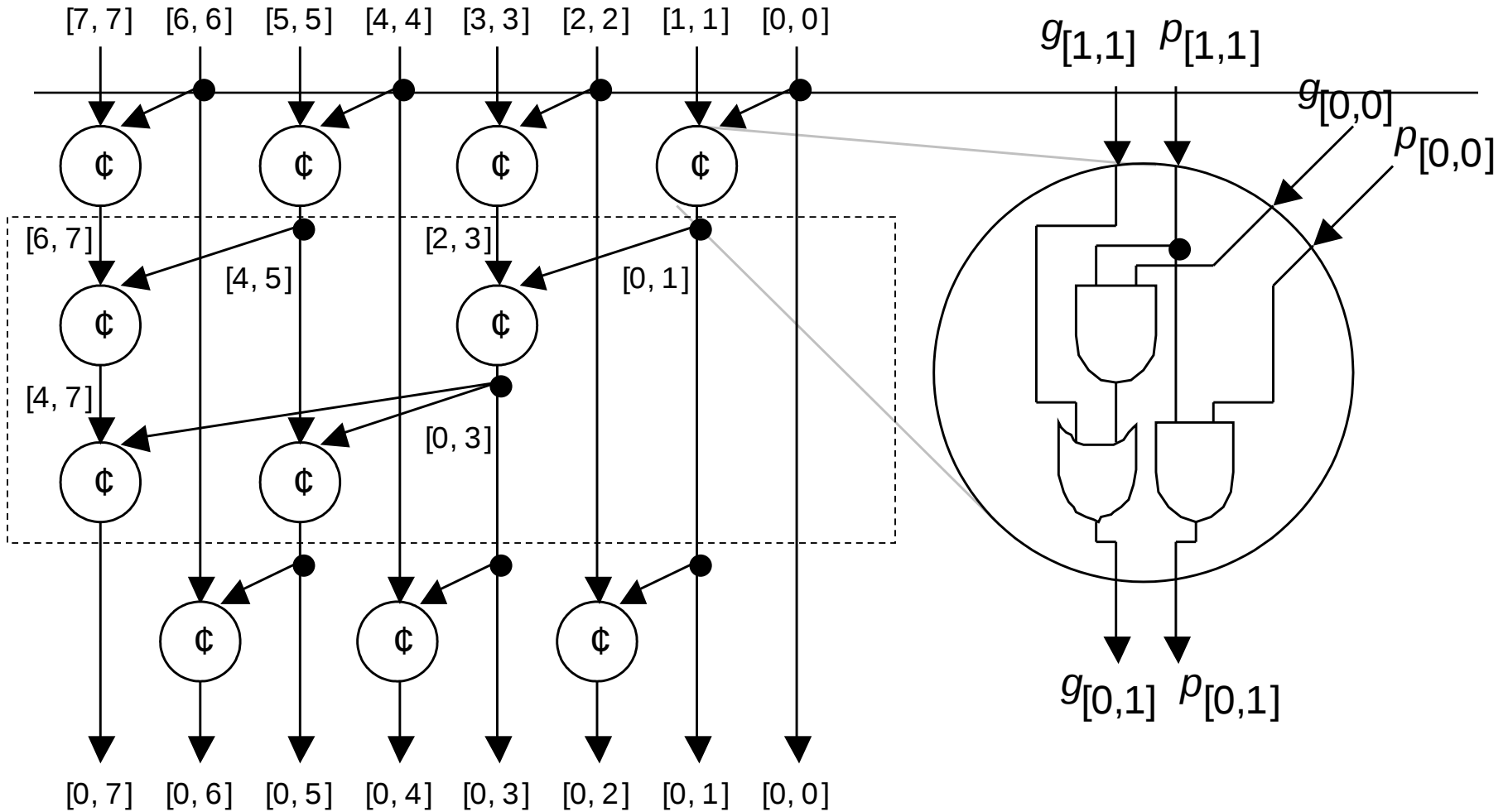

Brent-Kung Carry Network (16-Bit Adder)

 $x_{15} \ x_{14} \ x_{13} \ x_{12} \ x_{11} \ x_{10} \ x_9 \ x_8 \ x_7 \ x_6 \ x_5 \ x_4 \ x_3 \ x_2 \ x_1 \ x_0$



Reason for latency being $2 \log_2 k - 2$

Brent-Kung parallel prefix graph for 16 inputs.



Adder comparison

- Ripple-carry adder has highest performance/cost.
- Optimized adders are most effective in very long bit widths (> 48 bits).

ALUs

- ALU computes a variety of logical and arithmetic functions based on **opcode**.
- May offer complete set of functions of two variables or a subset.
- ALU built around adder, since carry chain determines delay.

