



CS31001 COMPUTER ORGANIZATION AND ARCHITECTURE

Debdeep Mukhopadhyay,
CSE, IIT Kharagpur



Instruction Execution Steps: The Multi Cycle Circuit

Performance of the Single Cycle Architecture

- The above design of control circuit is a stateless and combinational design.
- Each new instruction is read from the PC, and is executed in one single clock.
 - Thus $CPI=1$
- The clock cycle is determined by the longest instruction.

lw is the longest instruction

- lw execution includes all the possible steps:
 1. Instruction Excess: 2 ns
 2. Register Read: 1 ns
 3. ALU operation: 2 ns
 4. Data Cache Access: 2 ns
 5. Register Write-back: 1 nsTotal: 8 ns
- Thus a clock frequency of 125 MHz suffices.
So, for 1 instruction, $(1/125) \times 10^{-6}$ sec
Thus, 125 Million Instructions are executed per second (125 MIPS)

Obtaining better performance

- Note that the average instruction time is less, depends on the type of instruction, and their percentages in an application.
 - Rtype 44% 6 ns No data cache
 - Load 24% 8 ns
 - Store 12% 7ns No register write-back
 - Branch 18% 5ns Fetch+Register Read+Next-addr formation
 - Jump 2% 3ns Fetch + Instruction Decode
- Weighted average = 6.36 ns
- So, with a variable cycle time implementation, the performance is 157 MIPS
- However, this is not possible. But we see that a single cycle implementation has a poor performance.

Summary

- Clock cycle is determined by the slowest instruction.
- If the MIPS ISA includes more complex instructions, the disadvantage is more.
 - For example if we add a MULT/DIV instruction, then all operations need to be slowed down.
 - Thus MIPS does the MIPS/DIV instruction to a separate block (than the ALU block), with separate registers Hi and Lo.
 - sufficient time is kept to write back the results to the register file

Shorter Clock Cycles in Multi-cycle implementation

- The MIPS instructions typically has a set of actions, namely: memory access, register read, ALU operation, register write back.
- Each takes around 2 ns time.
- In a single cycle implementation, the worst-case (longest) time of the instructions is taken as the clock frequency.
- In a multi-cycle implementation, a subset of these actions is performed in one clock: thus the clock cycle can be much shorter.
- Every instructions takes several clock cycles (thus CPI $\neq 1$)

Comparison between the two approaches

- Consider the execution of n instructions, with the following characteristics

Name	Time needed	No of basic operations

Instruction 1	t_1	i_1
...		
Instruction 2	t_n	i_n

Say, the $\max(t_1, \dots, t_n) = t$, and each basic operation takes t' time units.

Comparison between the two approaches

□ Single Cycle: Clock Period : t

$$\text{Total time} = nt$$

□ Multi Cycle: Clock Period: t'

$$\text{Total time} = (i_1 + \dots + i_n)t'$$


Thus, multi-cycle is better if:

$$(i_1 + \dots + i_n)t' < nt$$


$$\text{or, } (i_1 + \dots + i_n) < n(t/t')$$

$$\text{or, } I < nr$$

$$I=8, n=2, r=4$$

 

$I=7, n=2, r=4$

 


Multi-cycles of the Instructions

- Each instruction starts in the same way (at the same state) and passes through 3-5 clock cycles before being executed:
 1. Instruction Fetch Cycle
 2. Instruction Decode and Register Access
 3. update of PC (Jump/Branch), ALU operations: (-) in case of branch, (+) in case of lw/sw, varies (in case of ALU-type instructions)
 4. Memory Read (lw), Memory Write (sw)
 5. Register Write Back (lw)


Subtle Points/Differences from the single cycle implementation

- A single memory unit suffices (as read and write from and to memory) are at different clock cycles.
- Requirement of Instruction Register: This register has to hold the instructions to generate appropriate control signals through the multiple cycles until it is executed.

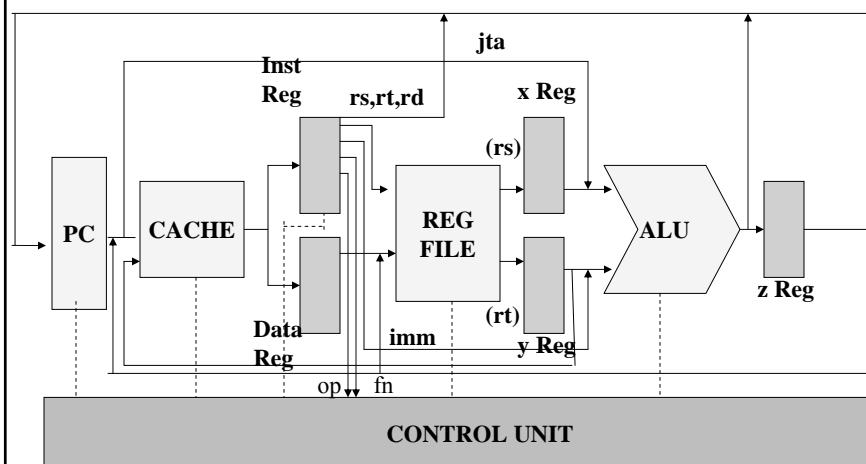Abstraction of Instruction Execution Unit




The control state machine

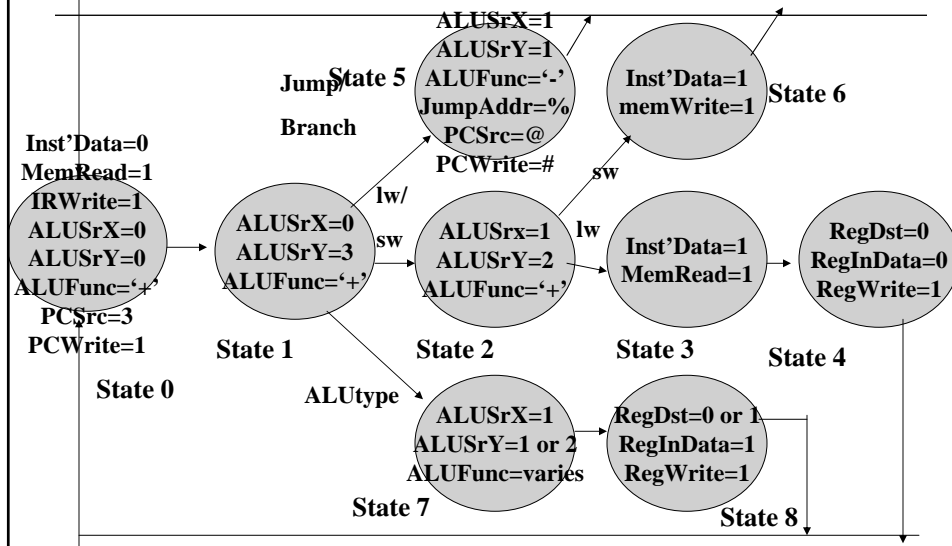


State 5

- %: 0 for j or jal, 1 for syscall, don't care for other instructions
- @: 0 for j, jal, syscall, 1 for jr, 2 for branches
- #: 1 for j, jr, jal, syscall, ALUzero(') for beq(bne), bit 31 of ALUout for bltz
- For jal, RegDst=2, RegInData=1, RegWrite=1

FSM Types

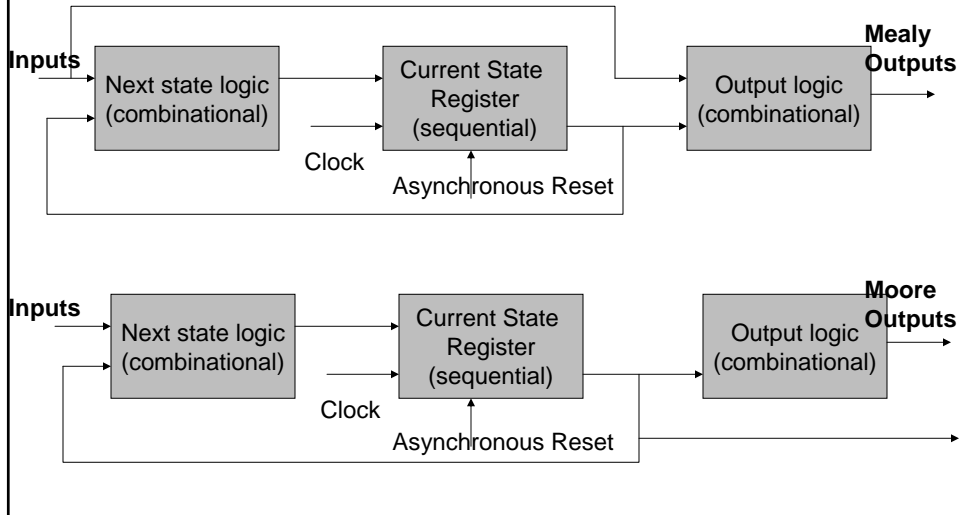

Coding FSMs in Verilog

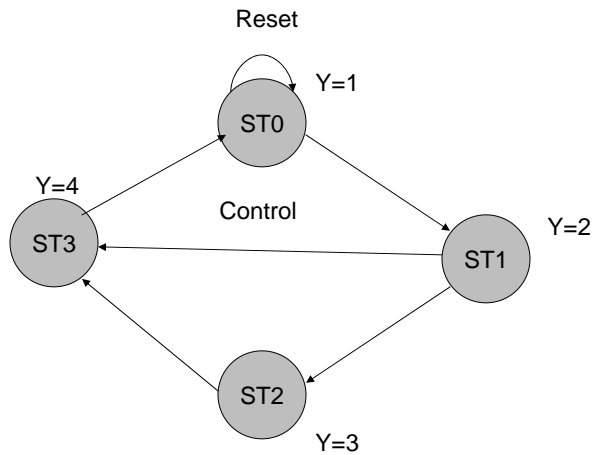

Issues

- State Encoding
 - sequential
 - gray
 - Johnson
 - one-hot

Encoding Formats

No	Sequential	Gray	Johnson	One-hot
0	000	000	0000	00000001
1	001	001	0001	00000010
2	010	011	0011	00000100
3	011	010	0111	00001000
4	100	110	1111	00010000
5	101	111	1110	00100000
6	110	101	1100	01000000
7	111	100	1000	10000000



Comments on the coding styles

- **Binary:** Good for arithmetic operations. But may have more transitions, leading to more power consumptions. Also prone to error during the state transitions.
- **Gray:** Good as they reduce the transitions, and hence consume less dynamic power. Also, can be handy in detecting state transition errors.



Coding Styles

- **Johnson:** Also there is one bit change, and can be useful in detecting errors during transitions. More bits are required, increases linearly with the number of states. There are unused states, so we require either explicit asynchronous reset or recovery from illegal states (even more hardware!)
- **One-hot:** yet another low power coding style, requires more no of bits. Useful for describing bus protocols.

Improper way

```
always @(posedge Clock or posedge Reset)
begin
    if(Reset) begin
        Y=1;
        STATE=ST0;
    end
end
```

Improper Way leads to unnecessary latches

```
else
    case(STATE)
        ST0: begin Y=1; STATE=ST1; end
        ST1: begin Y=2;
            if(Control) STATE=ST2;
            else STATE=ST3;
        ST2: begin Y=3; STATE=ST3; end
        ST3: begin Y=4; STATE=ST0; end
    endcase
end
```

Output Y is assigned under synchronous always block
so extra latches inferred.

Good FSMs

- Keep separate CS, NS and OL

Next State (NS)

```
always @(input or currentstate)
begin
  NextState=ST0;
  case(currentstate)
    ST0: begin
      NextState=ST1;
    end
    ST1: begin ...
    ...
    ST3:
      NextState=ST0;
  endcase
end
```


Current State (CS)

```
always @(posedge Clk or posedge reset)
begin
    if(Reset)
        currentstate=ST0;
    else
        currentstate=Nextstate;
end
```


Output Logic (OL)

```
always @(Currentstate)
begin
    case(Currentstate)
        ST0: Y=1;
        ST1: Y=2;
        ST2: Y=3;
        ST3: Y=4;
    end
end
```

The control state machine

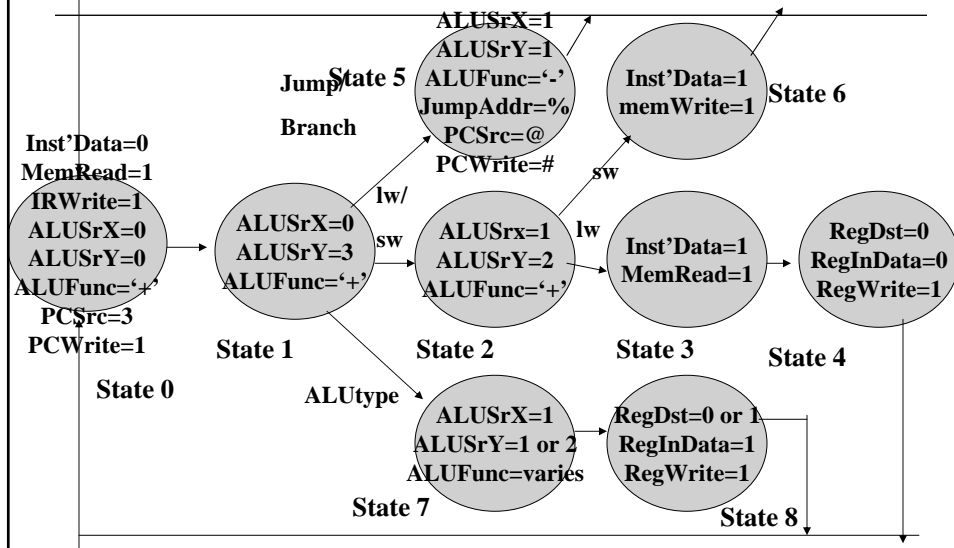

The Controller

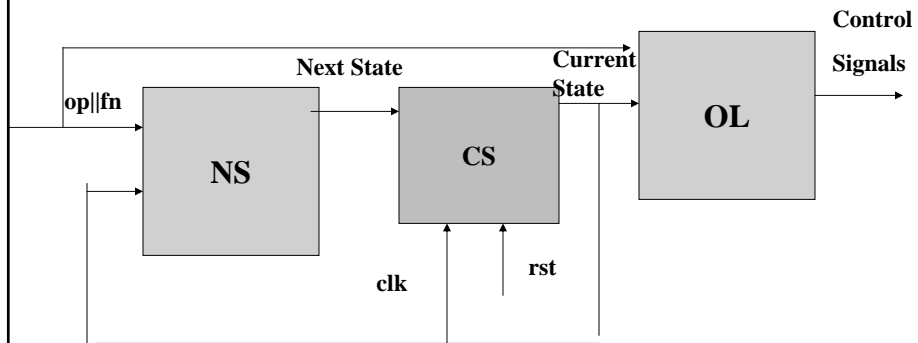

Performance of the Multicycle Design

- The multi-cycle implementation has a larger CPI than the single cycle implementation.
- Compute, the average CPI for:
 - Rtype 44%
 - Load 24%
 - Store 12%
 - Branch 18%
 - Jump 2%

Calculating CPI

Contribution to CPI

Rtype 44%: 4 cycles => 1.76

Load 24% : 5 cycles=> 1.20

Store 12%: 4 cycles=> 0.48

Branch 18%: 3 cycles=>0.54

Jump 2%: 3 cycles=> 0.06

Thus, average CPI = 4.04

Clock frequency = 500 MHz (for 2 ns clock duration)

This, corresponds to a performance of $500/4.04=123.8$
MIPS!!

Example

- Consider a MIPS++ processor, which is similar to our processor, except there are 3 types of R-type instructions:
 - R_a -type: half of all R-type instructions, 4 cycles
 - R_b -type: $\frac{1}{4}$ th of all R-type instructions, 6 cycles
 - R_c -type: $\frac{1}{4}$ th of all R-type instructions, 10 cycles
- With the same instruction mix in the last example, and assuming the slowest R-type instruction takes 16ns to execute in a single cycle implementation , derive the performance ration for a multi-cycle implementation.

Answer

- Single-cycle: 62.5 MIPS
Multi-cycle: 101.6 MIPS
- Inclusion of more **complex type instructions**, have small effect on the CPI of a multi-cycle implementation.
- However it has a significant effect on that of a single cycle implementation.

Microprogramming

- The control state machine resembles a program that has instructions, states, branching, and loops.
- We call such a hardware program a micro-program.
- Its basic steps are called as micro-instructions.
- Within each micro-instruction, there are different actions being performed, being called as micro-order.

Micro-program vs Hardwired Controller

- Instead of implementing the controller state machine in custom hardware, we can store the micro-instructions in a ROM.
- Hence, a program is broken into machine instructions.
- A machine instruction is in turn broken into a sequence of micro instructions.
- Each micro-instruction, thus defines a step in the execution of a machine language instruction.

Advantages

- More regular.
- Less dependent on the Instruction-set architecture.
 - The same hardware can be reused by simply changing the content of the ROM.
- Errors and omissions can be taken care of by simply changing the micro-program, rather than redesigning the circuit.
- Microprogramming is designing a suitable sequence of microinstructions to realize a particular ISA.


Disadvantage

- Lower speed compared to a hardwired control circuit.
- Each machine level instruction takes 3-5 ROM accesses to fetch the micro-instructions.
- After each micro-instruction has been read and placed in the micro-instruction register, sufficient time has to be given to allow the signals to stabilize and the actions to take place.

Micro-instruction format

- The design of the microcontrolled controller begins with a format.
- Each of the 20 control signals bear one-one relationship with the control bits.
- Except for the last 2 bit Sequence control signal.


MicroMIPS instruction format

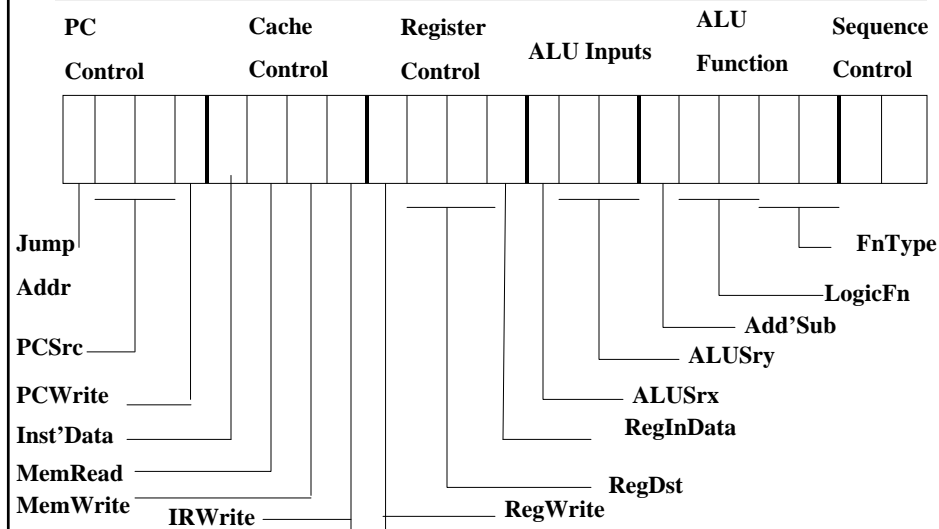

Sequence Control Bits

- The 2-bit sequence control bits allow for the control of micro-instruction sequencing in the same way that “PC control” affects the sequencing of machine language instruction.
- Option 0 is to advance to the next micro-instruction in sequence by incrementing the μ PC.
- Option 1 and 2 allow branching, depending on the opcode of the instruction.
- Option 3 is to go to the microinstruction 0 corresponding to state 0; this initiates the fetch phase of the next machine instruction.

Microprogrammed control unit

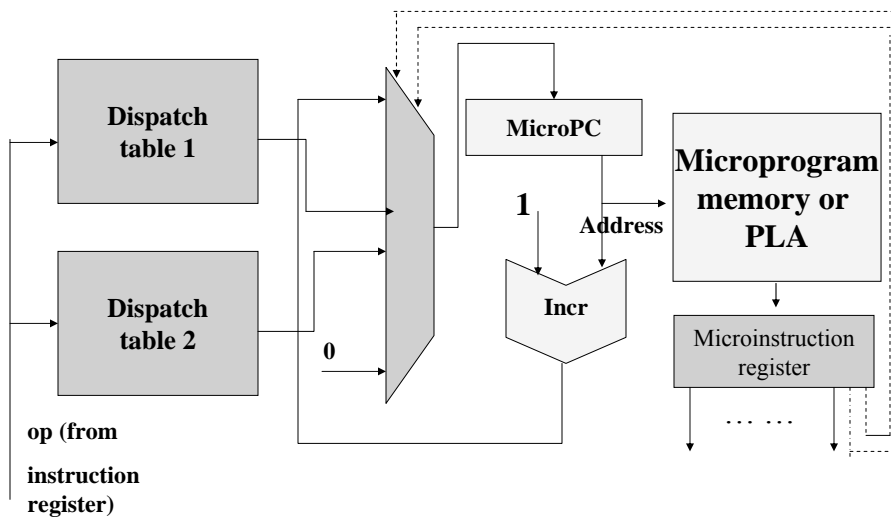

Dispatch tables

- Each of the two dispatch tables translates the opcode into a microinstruction address.
- Dispatch table 1 corresponds to the multi-way branch in going from cycle 2 to 3.
- Dispatch table 2 implements the branch between cycles 3 and 4.

Microinstruction field values and their symbolic names (default value is 0)

PC control	0001 PCjump	1001 syscall	X011 PCjreg	X101 PCbranch	X111 PCnext
Cache Control	0101 Cache Fetch	1010 Cache Store	1100 Cache Load		
Register Control	1000 rt←Data	1001 rt←z	1011 rd←z	1101 \$31←PC	
ALU inputs	000 PC◦ 4	011 PC◦ 4imm	101 x◦y	110 x◦imm	
ALU function	0xx10 + X1011 XOR	1xx01 < X1111 NOR	1xx10 - Xxx00 lui	X0011 Δ	X0111 V
Sequence Control	01 μPCdisp1	10 μPCdisp2	11 μPCfetch		

Micro-program

□ x111 0101 0000 000 0xx10 00

is equivalent to:

PCnext, Cache Fetch, PC + 4

Complete Micro-program

fetch:	PCnext,CacheFetch, PC+4 PC+4imm,μPCdisp1	State 0 (start) State 1
lui1:	lui(imm) rt←z, μPCfetch	State 7lui State 8lui
addi:	x+y rd←z, μPCfetch	State 7add State 8add
subi:	x-y rd←z, μPCfetch	State 7sub State 8sub
slt1:	x-y rd←z, μPCfetch	State 7slt State 8slt
addi1:	x+imm rd←z, μPCfetch	State 7addi State 8addi

Complete Micro-program (Contd.)

slti1:	x-imm rt ← z, μPCfetch	State 7slti State 8slti
and1:	x∧y rd ← z, μPCfetch	State 7and State 8and
or1:	x∨y rd ← z, μPCfetch	State 7add State 8add
xor1:	x∨y rd ← z, μPCfetch	State 7or State 8or
nor1:	x~∨y rd ← z, μPCfetch	State 7nor State 8nor
andi1:	x∧imm rt ← z, μPCfetch	State 7andi State 8andi

Complete Micro-program (Contd.)

ori1:	x∨imm rt ← z, μPCfetch	State 7ori State 8ori
xori1:	x⊕imm rd ← z, μPCfetch	State 7xori State 8xori
lsw1:	x+imm, μPCdisp2	State 2
lw2:	CacheLoad rd ← Data, μPCfetch	State 3 State 4
sw2:	CacheStore, μPCfetch	State 6

Complete Micro-program (Contd.)

j1:	PCjump, μ PCfetch	State 5j
jr1:	PCjreg, μ PCfetch	State 5jr
branch1:	PCbranch, μ PCfetch	State 5branch
jal1:	PCjump, $\$31 \leftarrow PC$, μ PCfetch	State 5jal
syscall:	PCsyscall, μ PCfetch	State 5syscall

Comments

- Each line represents micro-instructions.
- The label 1(2) is to indicate that they are arrived from dispatch table 1(2).
- The top-most microinstruction (fetch) is stored at ROM address 0.
- Thus starting the machine with μ PC cleared to 0, will cause program execution to start from location 0.

Assignment (not for submission)

Simplify the micro-instruction format, and design the micro-programs for the ISA, if the 5 ALU bits are directly generated in a separate decoder and fed to the ALU.

Horizontal vs Vertical Microinstruction

- The instruction discussed with separate bits for each of the 20 control bits of the datapath is called horizontal microinstruction.
- However, suitable encoding can reduce the size of the instructions.
 - Eg. the cache control field has four values, which can be encoded in 2 bits.
- Such an encoded instruction format is called as vertical microinstruction.
- However, they get slower as they need further decoders.