
 


 



CS 130 : Computer Systems - IV

*Shankar Balachandran
Dept. of Computer Science & Engineering
IIT Madras*


Recap



Recap

 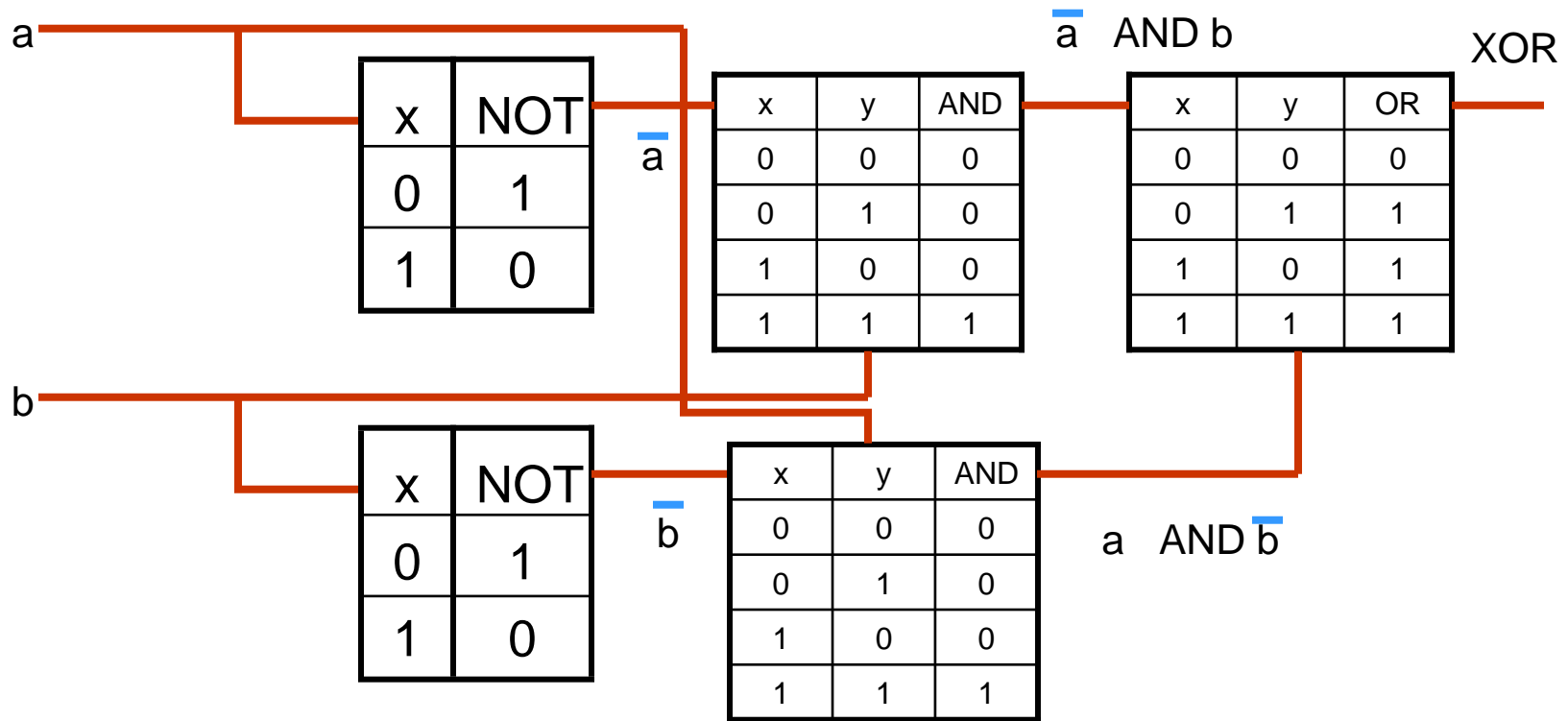

Recap

 

- Issues with scale
 - Computation
 - Storage
- Dealing with complexity
 - Break down the problem



Computers Also Have Constraints

- Computation
 - How fast can a computer run?
 - What kind of computations can it do?
- Storage
 - How much can it store?
 - How does it represent data?
- This is what engineering is about :
 - Solving problems under constraints
 - Usual mantra :
 - Better, cheaper, quicker




How Do Engineers Deal with Complexity?

- Design small sub-systems and put them together
- Deal with complexity, one subsystem at a time
- When you integrate subsystems
 - Make sure the whole assembly works fine too
- Use tools
- Current day hardware and software systems are both complex
 - Many ways to deal with complexity
 - Many are tested, many are not

Let's Revisit Binary Systems

 - 0's and 1's
- Simple Operation : Addition



Let's Build A Circuit For Adder


- Two binary variables
- What is the maximum value of sum?
- How many bits do we require to represent the sum?
- Let's design the circuit
 - Incoming data form inputs A and B
 - Outgoing data : Sum and Carry

| A | B | Carry | Sum |
|---|---|-------|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

You
recognize
the
tables?

Sum and Carry

- Carry := A AND B
- Sum := A XOR B

 


Want to Add Three Numbers?

| A | B | C | Sum | Carry Out |
|---|---|---|-----|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$$\text{Sum} = A \text{ XOR } B \text{ XOR } C$$


$$\text{COUT} = A.B + B.C + C.A$$

Circuit For This Binary Adder

 


What if You Want to Add More Binary Values?

 - You cannot use this table based approach
- Use the engineering approach
 - Break down the problem



Need to add four numbers!

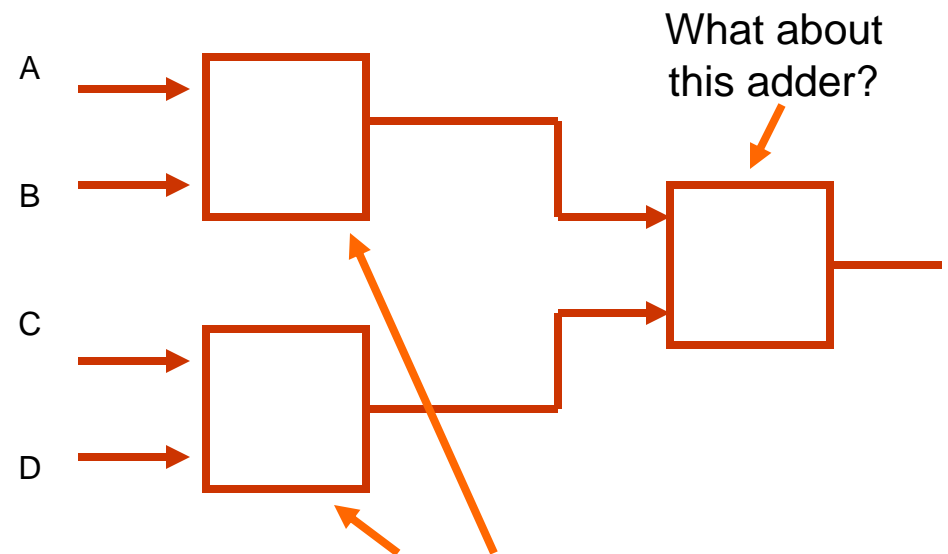

These adders take two inputs



Let's Add Two Numbers Again

- Now the numbers that we are going to add are multi-bit numbers
 - Like the examples that we saw before
- How do we attack this problem?
 - Go back to how you do decimal addition.
- You should ask me a few questions now 😊
 - Hint : Define **multi**
 - How big is multi?
- What if the numbers are two-bit numbers?
 - Lookup?
 - Iterative?

Two Binary Adders So Far


- Half Adder
 - Takes two binary inputs and adds them up
 - Gives sum and carry as output
- Full Adder
 - Takes three binary inputs and adds them up
 - Gives sum and carry as output
- Can we use half-adders and full-adders and do multi-bit addition?
 - YES!

A binary addition diagram showing the sum of 3 and 1. The numbers are written in red: 011 (3) and 001 (1). The sum is 100 (4). The carry is 1. The diagram includes blue labels for bit positions 2² and 2¹, and an orange arrow labeled 'Carry' pointing to the right. The sum is labeled 'Sum' at the bottom right.


$$\begin{array}{r} 3 \\ 1 \\ + \\ \hline 4 \end{array} \quad \begin{array}{r} 2^2 \quad 2^1 \\ 011 \\ 001 \\ \hline 100 \end{array} \quad \begin{array}{l} \text{Carry} \\ \text{Sum} \end{array}$$

Multi-Bit Adder

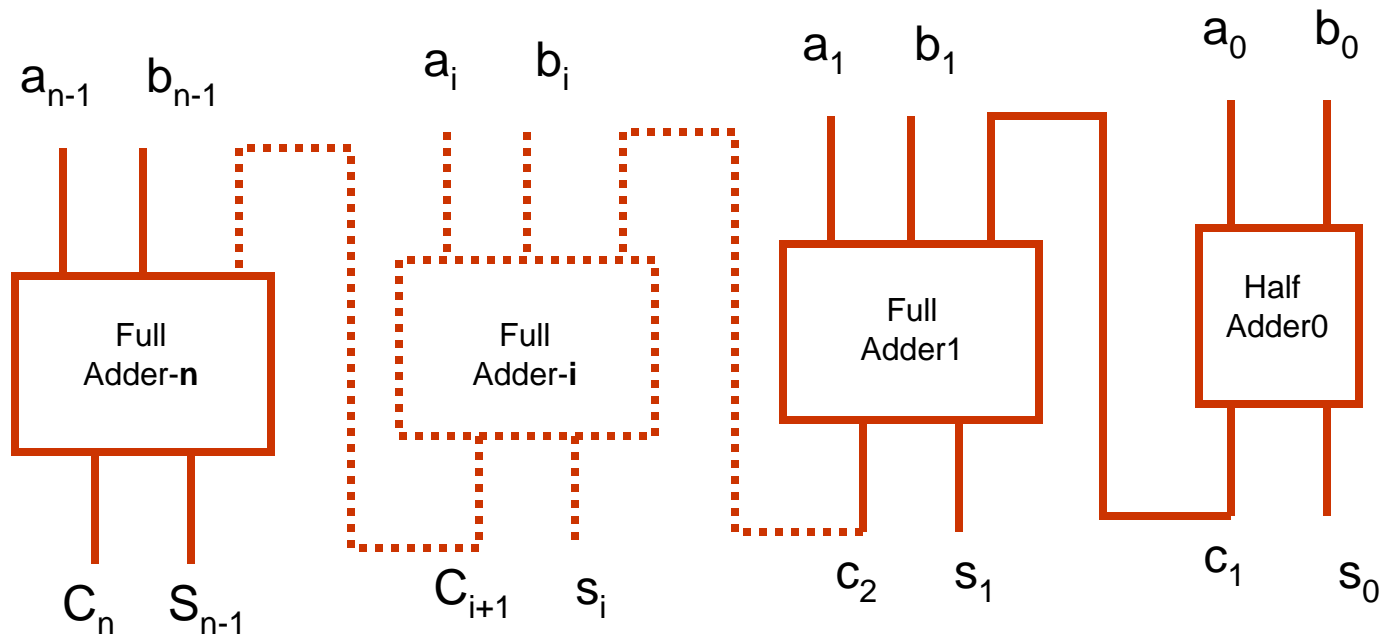- Let $A = a_{n-1} \dots a_2 a_1 a_0$
- Let $B = b_{n-1} \dots b_2 b_1 b_0$
- How many bits in Sum?
- How many bits in carry?



Example

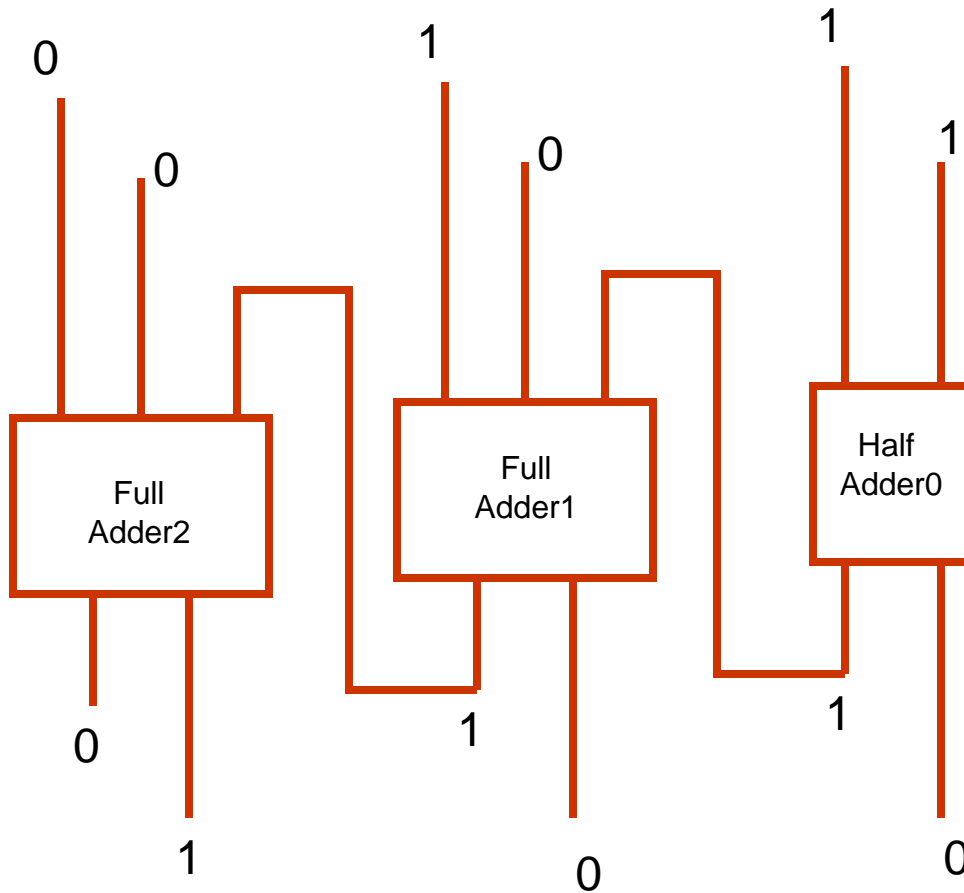

$$\begin{array}{r} 2^2 \quad 2^1 \\ + \quad 011 \\ \quad 001 \\ \hline \quad 100 \end{array}$$