 


Introduction To HDL

Verilog HDL


Debdeep Mukhopadhyay
debdeep@cse.iitm.ernet.in

How it started!




- Gateway Design Automation
- Cadence purchased Gateway in 1989.
- Verilog was placed in the public domain.
- Open Verilog International (OVI) was created to develop the Verilog Language as IEEE standard.

The Verilog Language

 


- Originally a modeling language for a very efficient event-driven digital logic simulator
- Later pushed into use as a specification language for logic synthesis
- Now, one of the two most commonly-used languages in digital hardware design (VHDL is the other)
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Combines structural and behavioral modeling styles

Concurrency

 


- Verilog or any HDL has to have the power to model concurrency which is natural to a piece of hardware.
- There may be pieces of two hardware which are even independent of each other.
- Verilog gives the following constructs for concurrency:
 - always
 - assign
 - module instantiation
 - non-blocking assignments inside a sequential block

However...

 


- The simulating machine is sequential.
- no-matter how many processors I have, I can write one more process which also have to be simulated concurrently.
- So, the processes are scheduled sequentially so that we have a feeling of parallelism:
 - like the desktop of our PC where we may open an editor, a netscape and so on. We have a feeling that they are executed parallelly, but in reality there is a serialization involved.

Race...

 


- So, always blocks (for example) are parallel...
- Even though they are not actually.
- So, which always block gets executed first? My simulation results will depend upon that!
- Standards do not say anything.
- It may be that the last always block is executed first...
- and so we have race!

How do we overcome race?

 

- We shall see in the class...
- Try to think of a clean hardware and you will not have race

Multiplexer Built From Primitives

 

```
module mux(f, a, b, sel);
```

← Verilog programs built from modules

```
output f;
```

← Each module has an interface

```
input a, b, sel;
```

```
and    g1(f1, a, nsel),
```

Module may contain structure: instances of primitives and other modules


```
      g2(f2, b, sel);
```

←


```
or     g3(f, f1, f2);
```

```
not g4(nsel, sel);
```

```
endmodule
```

 

Multiplexer Built From Primitives

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;
```


Identifiers not
explicitly defined
default to wires

```
and    g1(f1, a, nsel),  
       g2(f2, b, sel);  
or     g3(f, f1, f2);  
not    g4(nsel, sel);
```

```
endmodule
```

 

Multiplexer Built With Always

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
reg f;
```

```
always @(a or b or sel)  
  if (sel) f = b;  
  else f = a;
```


```
endmodule
```

Modules may contain one or more *always* blocks

 Sensitivity list contains signals whose change triggers the execution of the block



Multiplexer Built With Always

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
reg f;
```

```
always @(a or b or sel)  
if (sel) f = b;  
else f = a;
```


```
endmodule
```

A *reg* behaves like memory:
holds its value until
imperatively assigned
otherwise

 Body of an *always*
block contains
traditional imperative
code




Mux with Continuous Assignment

 


```
module mux(f, a, b, sel);  
output f;  
input a, b, sel;  
  
assign f = sel ? b : a;  
  
endmodule
```

LHS is always set to the value on the RHS

 Any change on the right causes re-evaluation




Identifiers in Verilog

 


- Any Sequence of letter, digits, dollar sign, underscore.
- First character must be a letter or underscore.
- It cannot be a dollar sign.
- Cannot use characters such as hyphen, brackets, or # in verilog names

Verilog Logic Values

 


- Predefined logic value system or value set : '0', '1', 'x' and 'z';
- 'x' means uninitialized or unknown logic value
- 'z' means high impedance value.

Verilog Data Types

 


- Nets: wire, supply1, supply0
- reg
- wire:
 - i) Analogous to a wire in an ASIC.
 - ii) Cannot store or hold a value.
- Integer

The reg Data Type

 


- Register Data Type: Comparable to a variable in a programming language.
- Default initial value: 'x'
- ```
module reg_ex1;
 reg Q; wire D;
 always @(posedge clk) Q=D;
```
- A reg is not always equivalent to a hardware register, flipflop or latch.
- ```
module reg_ex2; // purely combinational  
  reg c;  
  always @(a or b) c=a|b;  
endmodule
```


Difference between driving and assigning

 

- Programming languages provide variables that can contain arbitrary values of a particular type.
- They are implemented as simple memory locations.
- Assigning to these variables is the simple process of storing a value into the memory location.
- Verilog reg operates in the same way. Previous assignments have no effect on the final result.

Example

 

- module assignments;
reg R;
initial R<=#20 3;
initial begin
 R=5; R=#35 2;
end
initial begin
 R<=#100 1;
 #15 R=4;
 #220;
 R=0;
end
endmodule


The variable R is shared by all the concurrent blocks.

R takes the value that was last assigned.

This is like a hardware register which also stores the value that was last loaded into them.


But a reg is not necessarily a hardware register.

Wire: helps to connect

 

- Consider a set of tristate drivers connected to a common bus.
- The output of the wire depends on *all* the outputs and not on the last one.
- To model connectivity, any value driven by a device must be driven continuously onto that wire, in parallel with the other driving values.

Code

 

```
• module simple(A,B,C,sel,Z);
  input A, B, C;
  input [1:0] sel;
  output Z;
  reg Z;
  always @(A or B or C or SEL)
  begin
    2'b00: Z=1'bz;
    2'b01: Z=A;
    2'b10: Z=B;
    2'b11: Z=C;
  endcase
end
endmodule
```


```
• module simple(A,B,C,sel,Z);
  input A, B, C;
  input [1:0] sel;
  output Z;

  assign Z=(SEL==2'b01)?A:1'bz;
  assign Z=(SEL==2'b10)?B:1'bz;
  assign Z=(SEL==2'b11)?C:1'bz;

endmodule
```


Inferred as a multiplexer.
But we wanted drivers!

Numbers

 


- Format of integer constants:
Width' radix value;
- Verilog keeps track of the sign if it is assigned to an integer or assigned to a parameter.
- Once verilog loses sign the designer has to be careful.

Hierarchy

 

- Module interface provides the means to interconnect two verilog modules.
- Note that a reg cannot be an input/ inout port.
- A module may instantiate other modules.

Instantiating a Module

 

- Instances of


```
module mymod(y, a, b);
```

- Lets **instantiate** the module,

```
mymod mm1(y1, a1, b1); // Connect-by-position
```


```
mymod mm2(.a(a2), .b(b2), .y(c2)); // Connect-by-name
```

Sequential Blocks

 


- Sequential block is a group of statements between a begin and an end.
- A sequential block, in an always statement executes repeatedly.
- Inside an initial statement, it operates only once.

Procedures

 

- A Procedure is an always or initial statement or a function.
- Procedural statements within a sequential block executes concurrently with other procedures.

Assignments

 


- module assignments
// continuous assignments
always // beginning of a procedure
begin //beginning of a sequential block
//....Procedural assignments
end
endmodule
- A Continuous assignment assigns a value to a wire like a real gate driving a wire.

```
module holiday_1(sat, sun, weekend);  
input sat, sun; output weekend;  
// Continuous assignment  
assign weekend = sat | sun;  
endmodule
```


```
module holiday_2(sat, sun, weekend);  
input sat, sun; output weekend;  
reg weekend;  
always @(sat or sun)  
weekend = sat | sun; // Procedural  
endmodule // assignment
```

Blocking and Nonblocking Assignments

 

- Blocking procedural assignments must be executed before the procedural flow can pass to the subsequent statement.
- A Non-blocking procedural assignment is scheduled to occur without blocking the procedural flow to subsequent statements.

Nonblocking Statements are odd!

 

```
a = 1;
```

```
b = a;
```

```
c = b;
```

Blocking assignment:

```
a = b = c = 1
```

```
a <= 1;
```

```
b <= a;
```

```
c <= b;
```


Nonblocking assignment:

```
a = 1
```

```
b = old value of a
```


```
c = old value of b
```

Nonblocking Looks Like Latches

 


- RHS of nonblocking taken from latches
- RHS of blocking taken from wires


a = 1;
b = a;
c = b;

 

a <= 1;
b <= a;
c <= b;

 

Examples

 

- **Blocking:**
always @(A1 or B1 or C1 or M1)
begin
 M1=#3(A1 & B1);
 Y1= #1(M1|C1);
end
- **Non-Blocking:**
always @(A2 or B2 or C2 or M2)
begin
 M2<=#3(A2 & B2);
 Y2<=#1(M1 | C1);
end


Statement executed at time t causing M1 to be assigned at t+3

Statement executed at time t+3 causing Y1 to be assigned at time t+4

Statement executed at time t causing M2 to be assigned at t+3


Statement executed at time t causing Y2 to be assigned at time t+1.
Uses old values.

 Order dependency of Concurrent Statements



- Order of concurrent statements does not affect how a synthesizer synthesizes a circuit.
- It can affect simulation results.

 Order dependency of Concurrent Statements




- always @(posedge clock)

```
begin: CONCURR_1
```

```
Y1<=A;
```

```
end
```

 

- always @(posedge clock)

```
begin: CONCURR_2
```

```
if(Y1) Y2=B; else Y2=0;
```

```
end
```


Can you figure out the possible mismatch of simulation with synthesis results?

Explanation of the mismatch



- The actual circuit is a *concurrent* process.
- The first and second flip flop are operating parallel.
- However if the simulator simulates CONCURR_1 block before CONCURR_2, we have an error. Why?
- So, how do we solve the problem?

Solution

 

- always @(posedge clock)

```
begin
```

```
  Y1<=A;
```

```
  if(Y1==1)
```

```
    Y2<=B;
```


```
  else
```

```
    Y2<=0;
```

```
end
```

*With non-blocking assignments
the order of the assignments
is immaterial...*


Parameterized Design

 

- ```
module vector_and(z, a, b);
 parameter cardinality = 1;
 input [cardinality-1:0] a, b;
 output [cardinality-1:0] z;
 wire [cardinality-1:0] z = a & b;
endmodule
```
- We override these parameters when we instantiate the module as:  

```
module Four_and_gates(OutBus, InBusA, InBusB);
 input [3:0] InBusA, InBusB; output[3:0] OutBus;
 Vector_And #(4) My_And(OutBus, InBusA, InBusB);
endmodule
```

# Functions (cont'd)

 


- Function Declaration and Invocation
  - Declaration syntax:

```
function <range_or_type> <func_name>;
 <input_declaration(s)>
 <variable_declaration(s)>
 begin // if more than one statement needed
 <statements>
 end // if begin used
endfunction
```

# Function Examples

## Controllable Shifter

 

```
module shifter;
`define LEFT_SHIFT 1'b0
`define RIGHT_SHIFT 1'b1
reg [31:0] addr, left_addr,
 right_addr;
reg control;


initial
begin
 ...
end

always @(addr)begin
 left_addr =shift(addr,
 `LEFT_SHIFT);
 right_addr
 =shift(addr,`RIGHT_SHIFT);
end


function [31:0]shift;
input [31:0] address;
input control;
begin
 shift = (control==`LEFT_SHIFT)
 ?(address<<1) : (address>>1);
end
endfunction

endmodule
```


# How Are Simulators Used?

 

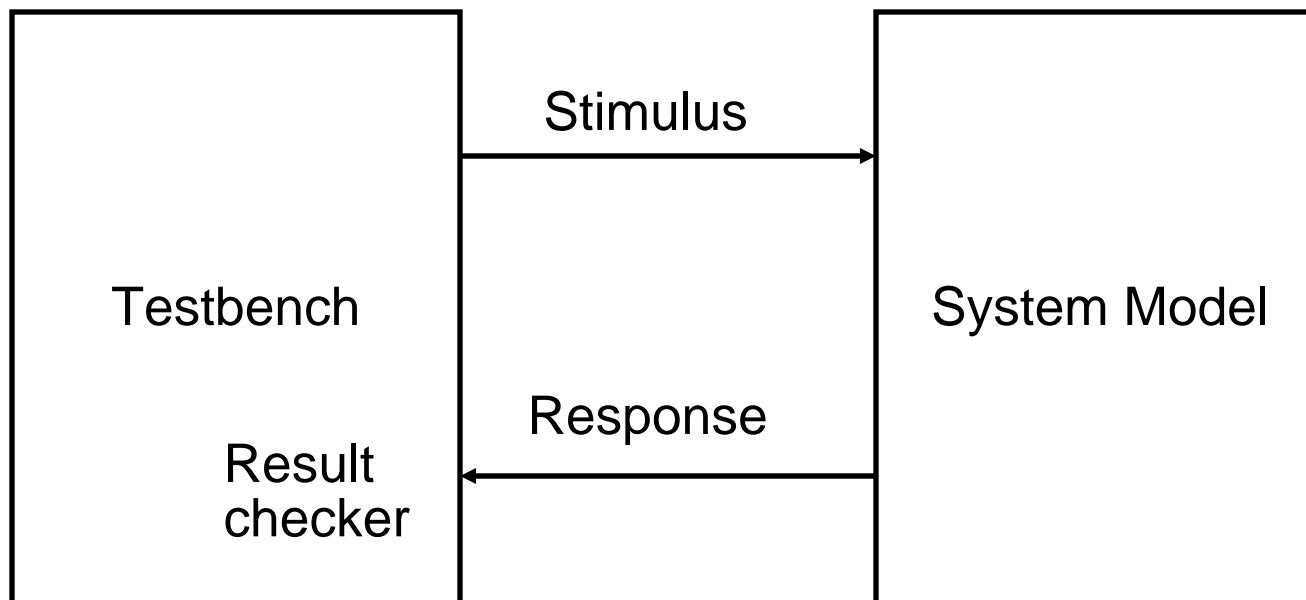- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously



# Looking back at our multiplexer

 


- “Dataflow” Descriptions of Logic

```
//Dataflow description of mux
module mux2 (in0, in1, select, out);
 input in0,in1,select;
 output out;
 assign out = (~select & in0)
 | (select & in1);
endmodule // mux2
```

Alternative:

```
assign out = select ? in1 : in0;
```

# TestBench of the Multiplexer

 

- Testbench



```
module testmux;
 reg a, b, s;
 wire f;
 reg expected;

 mux2 myMux (.select(s), .in0(a), .in1(b), .out(f));


 initial
 begin
 s=0; a=0; b=1; expected=0;
 #10 a=1; b=0; expected=1;
 #10 s=1; a=0; b=1; expected=1;
 end
 initial
 $monitor(
 "select=%b in0=%b in1=%b out=%b, expected out=%b time=%d",
 s, a, b, f, expected, $time);
endmodule // testmux
```



# A Car Speed Controller

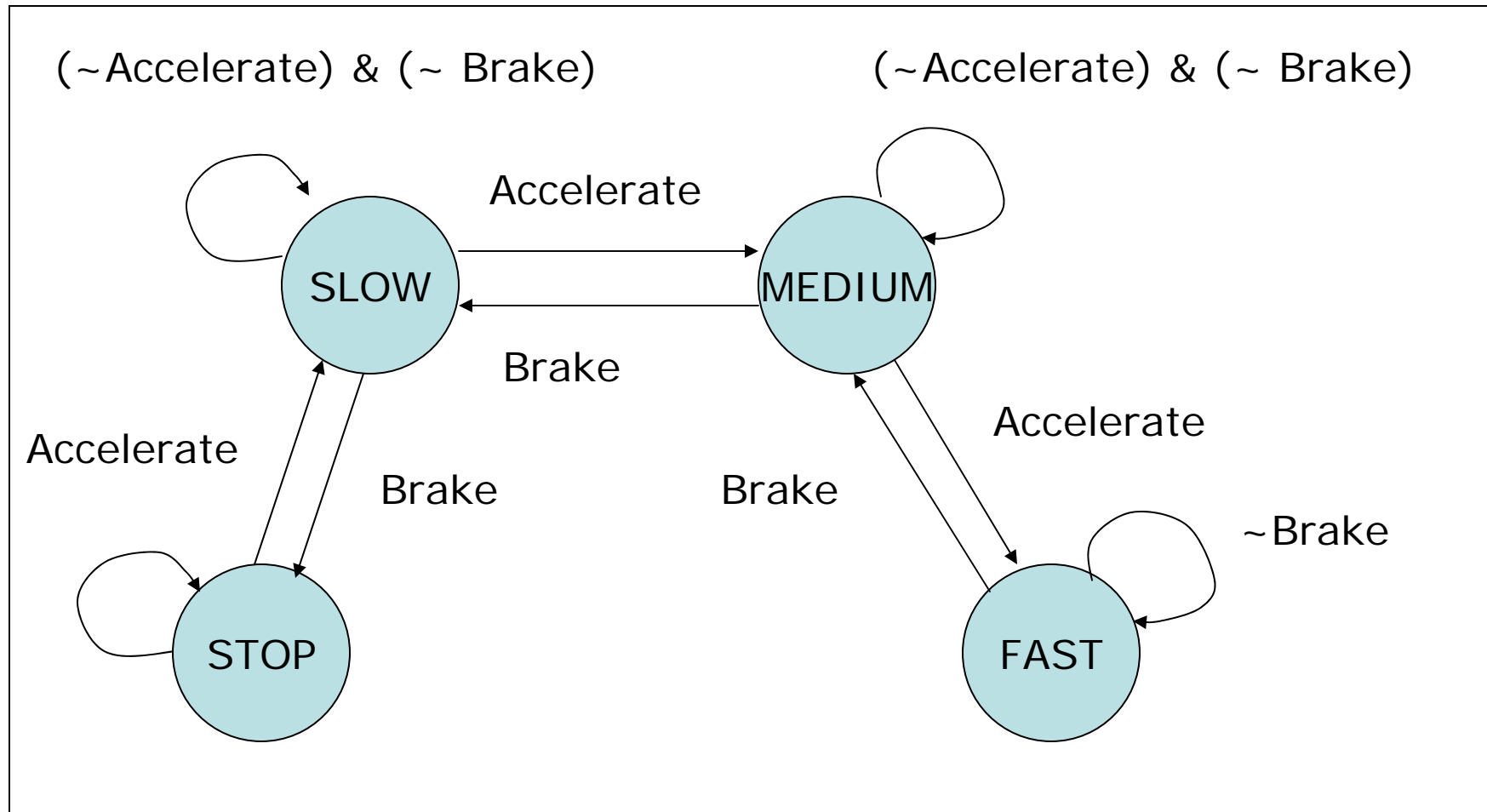 


# Car Controller Coding

 

```
module fsm_car_speed_1(clk, keys, brake, accelerate,
 speed);
 input clk, keys, brake, accelerate;
 output [1:0] speed;
 reg [1:0] speed;

 parameter stop = 2'b00,
 slow = 2'b01,
 mdium = 2'b10,
 fast = 2'b11;
```

# Car Controller (contd.)

 


```
always @(posedge clk or
 negedge keys)
begin
 if(!keys)
 speed = stop;
 else if(accelerate)
 case(speed)
 stop: speed = slow;
 slow: speed = mdium;
 mdium: speed = fast;
 fast: speed = fast;
 endcase
end
```


```
else if(brake)
 case(speed)
 stop: speed = stop;
 slow: speed = stop;
 mdium: speed = slow;
 fast: speed = mdium;
 endcase
else
 speed = speed;
end

endmodule
```

# A Better Way!

 

 - We keep a separate control part where the next state is calculated.
- The other part generates the output from the next state.
- We follow this architecture in the coding of any finite state machines, like ALU, etc. (to be discussed later)



```
module fsm_car_speed_2(clk, keys,
 brake, accelerate, speed);
 input clk, keys, brake, accelerate;
 output [1:0] speed;
 reg [1:0] speed;
 reg [1:0] newspeed;
```

```
 parameter stop = 2'b00,
 slow = 2'b01,
 mdium = 2'b10,
 fast = 2'b11;
```

```
always @(keys or brake or
 accelerate or speed)
```

```
begin
 case(speed)
 stop:
 if(accelerate)
 newspeed = slow;


 else
 newspeed = stop;
```

```
 slow:
 if(brake)
 newspeed = stop;
 else if(accelerate)
 newspeed = mdium;
 else
 newspeed = slow;
 mdium:
 if(brake)
 newspeed = slow;
 else if(accelerate)
 newspeed = fast;
 else
 newspeed = mdium;
 fast:
 if(brake)
 newspeed = mdium;
 else
 newspeed = fast;
 default:
 newspeed = stop;
 endcase
end
```

```
always @(posedge clk or
 negedge keys)
begin
 if(!keys)
 speed = stop;
 else
 speed = newspeed;
end

endmodule
```
 
## Conclusion : Write codes which can be translated into hardware !



The following cannot be translated into hardware( non - synthesizable):

- Initial blocks
  - Used to set up initial state or describe finite testbench stimuli
  - Don't have obvious hardware component
- Delays
  - May be in the Verilog source, but are simply ignored
- In short, write codes with a hardware in your mind. In other words do not depend too much upon the tool to decide upon the resultant hardware.
- Finally, remember that you are a better designer than the tool.