

# Boolean State Transformation

## Boolean Gates


- **Boolean gates** transform the state of a **Boolean system**.
- Conventionally a **Boolean gate** is a map  $f : \{0, 1\}^n \rightarrow \{0, 1\}$ , where  $n$  is the number of input lines and there is only one output line.

For a large  $n$ , an  $n$ -input gate may be decomposed in smaller **realisable** gates.

## Boolean Gates

- But if the system state is represented by *n*-bits then a state transition map is  $g : \{0, 1\}^n \rightarrow \{0, 1\}^n$ .
- The map  $g$  may be viewed as an  $n$  input and  $n$  output gate. This also may be realised using smaller gates.
- Following diagram is an example.

## Boolean Gate Array

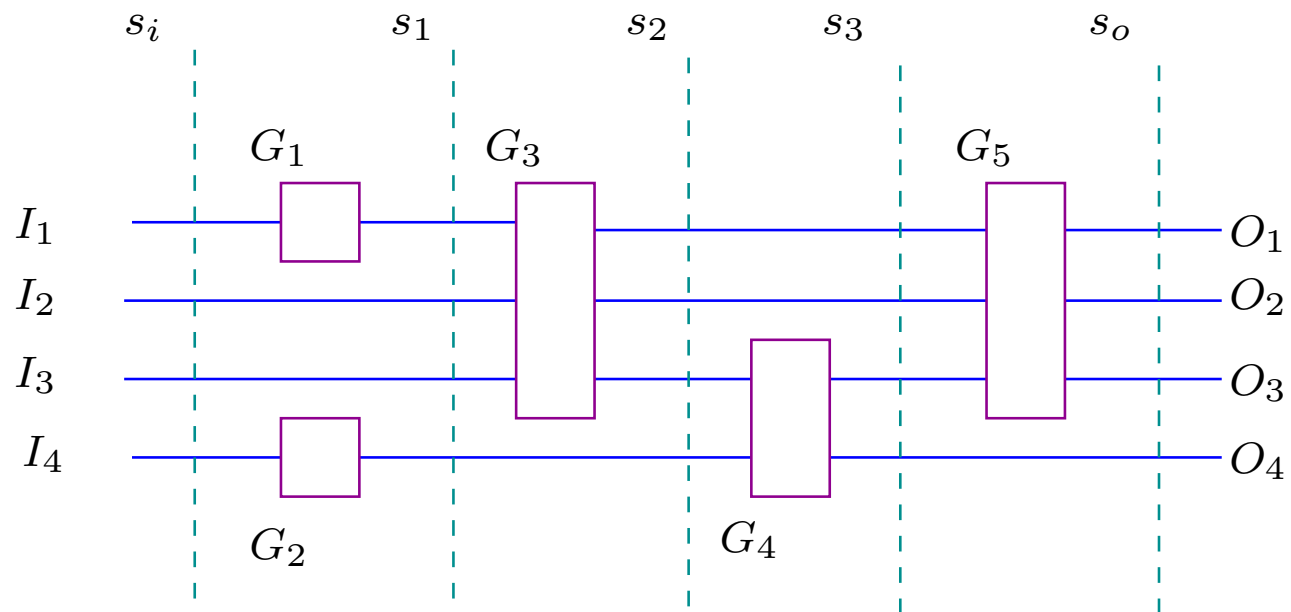

**Note**

- $s_i$  is the input state,  $s_o$  is the output state.
- $s_1, s_2, s_3$  are intermediate states.
- Transition from  $s_0$  to  $s_1$  is through the gates  $G_1, I, I, G_2$ , where  $I$  may be viewed as **identity map**.
- This transition may be viewed as a 4-bit transformation  $G_1 \otimes I \otimes I \otimes G_2$ .
- Other transitions are similar.

## 1-bit Boolean Gates

There are **four** one variable **Boolean functions**.

- Two **constant functions**:  $c_0 : 0 \mapsto 0, 1 \mapsto 0$ ,  
 $c_1 : 0 \mapsto 1, 1 \mapsto 1$ ,
- the **identity map**  $i_1 : 0 \mapsto 0, 1 \mapsto 1$ , and
- the **not gate**  $\neg : 0 \mapsto 1, 1 \mapsto 0$ .

## 1-bit Linear Algebra

If we encode Boolean 0 as  $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$  and 1 as  $\begin{bmatrix} 0 \\ 1 \end{bmatrix}$ , the following transformation matrices represent the four gates.

$$C_0 = \begin{bmatrix} 1 & 1 \\ 0 & 0 \end{bmatrix}, C_1 = \begin{bmatrix} 0 & 0 \\ 1 & 1 \end{bmatrix}, i_1 = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}, \neg : \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

The  $i_1$  and  $\neg$  gate are **invertible**, but other two are not.

## 1-bit Linear Algebra

$$\begin{array}{l}
 c_0(0) \\
 c_1(0) \\
 \neg 0 \\
 \neg 1
 \end{array}
 =
 \begin{array}{c}
 \left[ \begin{array}{cc} 1 & 1 \\ 0 & 0 \end{array} \right] \\
 \left[ \begin{array}{cc} 0 & 0 \\ 1 & 1 \end{array} \right] \\
 \left[ \begin{array}{cc} 0 & 1 \\ 1 & 0 \end{array} \right] \\
 \left[ \begin{array}{cc} 0 & 1 \\ 1 & 0 \end{array} \right]
 \end{array}
 =
 \begin{array}{c}
 \left[ \begin{array}{c} 1 \\ 0 \end{array} \right] \\
 \left[ \begin{array}{c} 1 \\ 0 \end{array} \right] \\
 \left[ \begin{array}{c} 1 \\ 0 \end{array} \right] \\
 \left[ \begin{array}{c} 0 \\ 1 \end{array} \right]
 \end{array}
 =
 \begin{array}{c}
 \left[ \begin{array}{c} 1 \\ 0 \end{array} \right] \\
 \left[ \begin{array}{c} 0 \\ 1 \end{array} \right] \\
 \left[ \begin{array}{c} 0 \\ 1 \end{array} \right] \\
 \left[ \begin{array}{c} 1 \\ 0 \end{array} \right]
 \end{array}
 =
 \begin{array}{c}
 0, \\
 1, \\
 1, \\
 0.
 \end{array}$$



## 1-Bit Boolean Transformation Matrix

- A  $2 \times 2$  matrix over  $\mathbb{F}_2$  is a valid transformation matrix for a single-bit if every column has exactly one 1.
- This restriction is due to our encoding of 0 and 1.
- We get  $2 \times 2 = 4$  valid transformation matrices corresponding to  $c_0$ ,  $c_1$ ,  $i_1$  and  $\neg$ .
- Only two of them are **reversible**.

## Reversibility

- **Reversibility** of computation or **invertibility** of an operator is an issue even in classical computation.
- It is known from thermodynamics that there is no increase in **entropy** in a **reversible process**.
- But completely **isentropic circuits** are impossible to design.

## Reversibility

- There are **adiabatic circuits** that use **reversible logic** to reduce power consumption during switching.
- **Landauer's principle** claims that any “**logically irreversible**” change in **information** causes more change in entropy.
- A **physical reversibility** demands **logical reversibility**.

## Reversibility

- We shall see that **state transition** in a quantum mechanical system is **reversible**.
- Only the **reversible classical logical gates** may have quantum mechanical counterpart.
- So we explore the classical Boolean gates that are **reversible** as well as **universal**.

## Tensor Product

We define the **tensor product** of two **2-dimensional vectors**  $\vec{x} = \begin{bmatrix} a \\ b \end{bmatrix}$  and  $\vec{y} = \begin{bmatrix} c \\ d \end{bmatrix}$  over some field  $F$  as

$$\begin{bmatrix} a \\ b \end{bmatrix} \otimes \begin{bmatrix} c \\ d \end{bmatrix} = \begin{bmatrix} a \begin{bmatrix} c \\ d \end{bmatrix} \\ b \begin{bmatrix} c \\ d \end{bmatrix} \end{bmatrix} = \begin{bmatrix} ac \\ ad \\ bc \\ bd \end{bmatrix}.$$

This can be generalised to higher dimensions.

## 2-Bit Boolean Data

1-bit Boolean data is encoded as  $0 = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$  and  $1 = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$ . Two bit Boolean data may be viewed as the **tensor product** of two 1-bit vectors.

## 2-Bit Boolean Data

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 1 \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} \cdot$$

$$\begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} \cdot$$

## 2-Bit Boolean Data

$$\begin{bmatrix} 0 \\ 1 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \end{bmatrix} \cdot$$

$$\begin{bmatrix} 0 \\ 1 \end{bmatrix} \otimes \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} \cdot$$



## 2-bit Boolean Data

Four possible combinations of inputs,  
**00,01,10,11** are encode as four **4-vectors**.

$$00 : \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}, 01 : \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}, 10 : \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \end{bmatrix}, 11 : \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} .$$

This can be generalised for  $n$ -bits.

## 2-bit Boolean Gates

- There are **sixteen** 2-variable conventional **Boolean functions** e.g. **and, nand, or, nor** etc.
- They correspond to maps from  $\{0, 1\}^2 \rightarrow \{0, 1\}$ .
- But we are interested about state transition maps from  $\{0, 1\}^2 \rightarrow \{0, 1\}^2$  that are **reversible**.
- There are total  $4^4 = 256$  such maps.

## 2-Bit Boolean Transformation Matrix

- Similar to 1-bit transformations, a 2-bit transformation is a  $4 \times 4$  matrix over  $\mathbb{F}_2$ . It is a **valid** if every column has exactly one 1.
- There are  $4 \times 4 = 256$  valid transformations corresponding to 256 maps  $\{0, 1\}^2 \rightarrow \{0, 1\}^2$ .
- But only  $4!$  among them are reversible, where every column has exactly one 1.


## Universality and Reversibility

- But is there any **universal gate** out these 24 **reversible gates**?
- One possibility is to consider the **tensor products** of **1-bit reversible gates** e.g.  $\neg \otimes i_1$  or  $\neg \otimes \neg$  - but they cannot be **universal**.
- Another temptation is to try with a **pair** of **conventional gates** and see what happens.
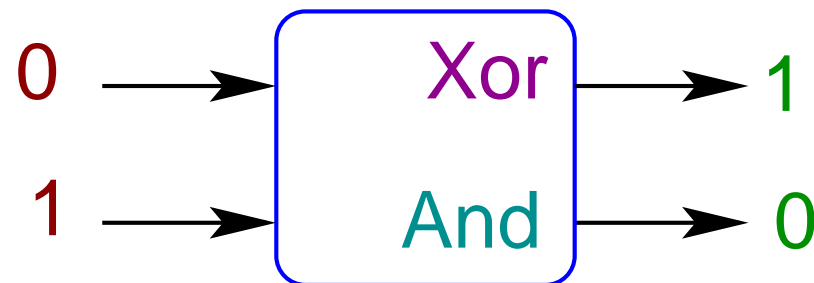
## Xor-And Transformation

Here is an example of a 2-bit transformation matrix of a pair of conventional gates.

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 1(01) \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1(10) \\ 0 \end{bmatrix}$$



### Note

- The transformation matrix of **Xor-And** pair is not invertible - the 4<sup>th</sup>-row has all zeros.
- An **invertible transformation matrix** correspond to a **permutation** of rows of  $4 \times 4$  identity matrix.

## CNOT Gate

- A **controlled not (CNOT)** gate, has invertible transition matrix.
- Its inputs are  $(c, d)$ , where  $c$  is the **control input** and  $d$  is the **data input**.
- The mapping is  $(c, d) \mapsto (c, c \oplus d)$ .

$$CNOT(c, d) = \begin{cases} (0, d) & \text{if } c = 0, \\ (1, \neg d) & \text{if } c = 1. \end{cases}$$

## CNOT Transition Matrix




$$CNOT(1,0) = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} = (1,1)$$

- CNOT is inverse of itself.
- $CNOT(CNOT(c, d)) = CNOT(c, c \oplus d) = (c, c \oplus (c \oplus d)) = (c, d)$ .




Diagram

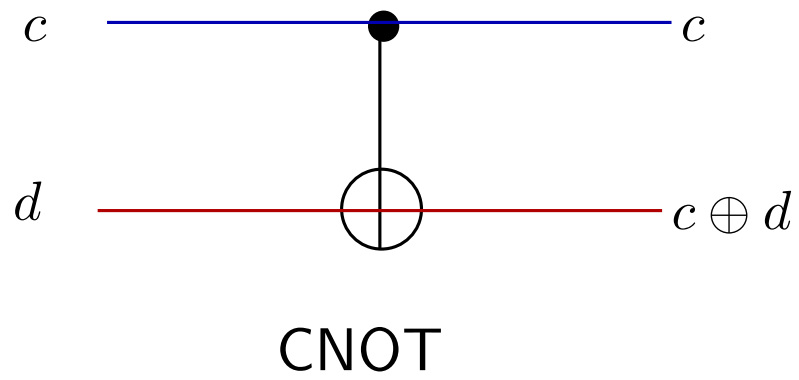
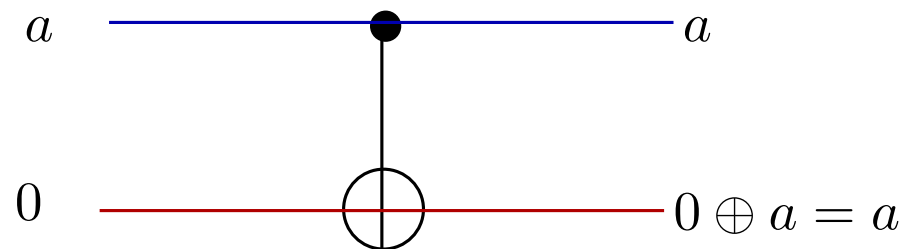
## CNOT can Copy a Bit

We can copy (clone) a bit using CNOT:

$$(a, 0) \mapsto (a, a \oplus 0) = (a, a).$$



CNOT

This is actually creating a **FANOUT**.

### Note

- Tensor products of 1-bit reversible gate are  $i_1 \otimes i_1, i_1 \otimes \neg, \neg \otimes i_1, \neg \otimes \neg$ .

- CNOT cannot be realised using them.

- It is  $\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \otimes \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} \otimes \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$ ,

where  $\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes [1 \ 0]$  and

$$\begin{bmatrix} 0 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \otimes [0 \ 1].$$

## 2-bit Universal Gate is Impossible

The truth-table for a 2-bit reversible gate is as follows:

$i_1$	$i_0$	$o_1$	$o_0$
0	0	$x_0$	$y_0$
0	1	$x_1$	$y_1$
1	0	$x_2$	$y_2$
1	1	$x_3$	$y_3$

## 2-bit Universal Gate is Impossible

- The output of a **reversible** gate is a **permutation** of  $\{00, 01, 10, 11\}$ .
- It has exactly two 0's and two 1's per **output column** of the truth table.
- But  $i_1 \wedge i_0$  has three 0's and  $i_1 \vee i_0$  has three 1's in their output.
- None of them can be produced by a two bit **reversible** gate.

## Reversible and Universal Boolean Gates

- The 2-bit **CNOT** gate is **reversible**.
- There are 24 reversible 2-Bit Boolean transformations. But that set cannot generate all logic function.
- 3-bit transformations are map from  $\{0, 1\}^3 \rightarrow \{0, 1\}^3$ . There are  $8^8 = 16777216$  such transformations. But out of which  $8! = 40320$  are **reversible**.

## Universal Reversible Gates

- One 3-bit reversible transformation is **Toffoli gate** or **CCNOT gate**. It was invented by **Tommaso Toffoli** from Italy.
- The **Toffoli gate** or **CCNOT gate** is known to be **universal**.

## Toffoli or CCNOT Gate

Following is the map of CCNOT gate:

$(x, y, c) \mapsto (x, y, c \oplus (x \wedge y))$ , where  $x, y$  remains unchanged,

$$c = \begin{cases} \neg c & \text{if } x = 1 = y, \\ c & \text{otherwise.} \end{cases}$$

If  $c = 0$ , the 3<sup>rd</sup> output is  $0 \oplus (x \wedge y) = x \wedge y$ .




## CCNOT Gate Transition Matrix

CCNOT transition matrix is its own inverse.

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$$

Diagram

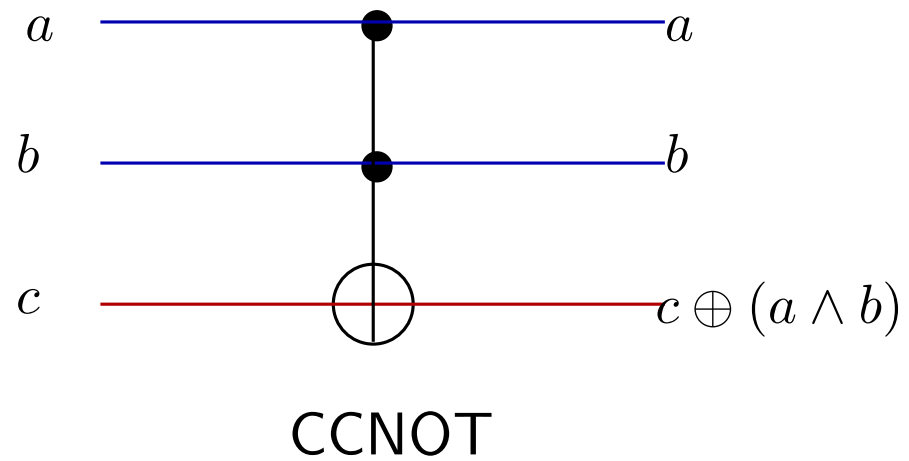

**NOT, NAND and FANOUT from CCNOT**

CCNOT gate can implement **NOT**, **NAND** and **COPY/FANOUT** operations if logic '0' and '1' are available.

$$(1, 1, c) \mapsto (1, 1, \neg c),$$

$$(a, b, 1) \mapsto (a, b, 1 \oplus (a \wedge b)) = (a, b, \neg(a \wedge b)),$$

$$(1, a, 0) \mapsto (1, a, 0 \oplus (1 \wedge a)) = (1, a, a).$$

## OR using only CCNOT


We know that  $\neg(\neg a \wedge \neg b) = a \vee b$ .

1.  $a$  and  $b$  are actual input. We use several ‘ancilla’ input.
2. Use two CCNOT gates to create a copies of  $a$  and  $b$ .
3. Use two CCNOT gates to compute  $\neg a$  and  $\neg b$ .

OR using only CCNOT

4. Finally another CCNOT gate to compute  $\neg(\neg a \wedge \neg b)$ .
5. We are not taking care of crossovers.

## OR using CCNOT

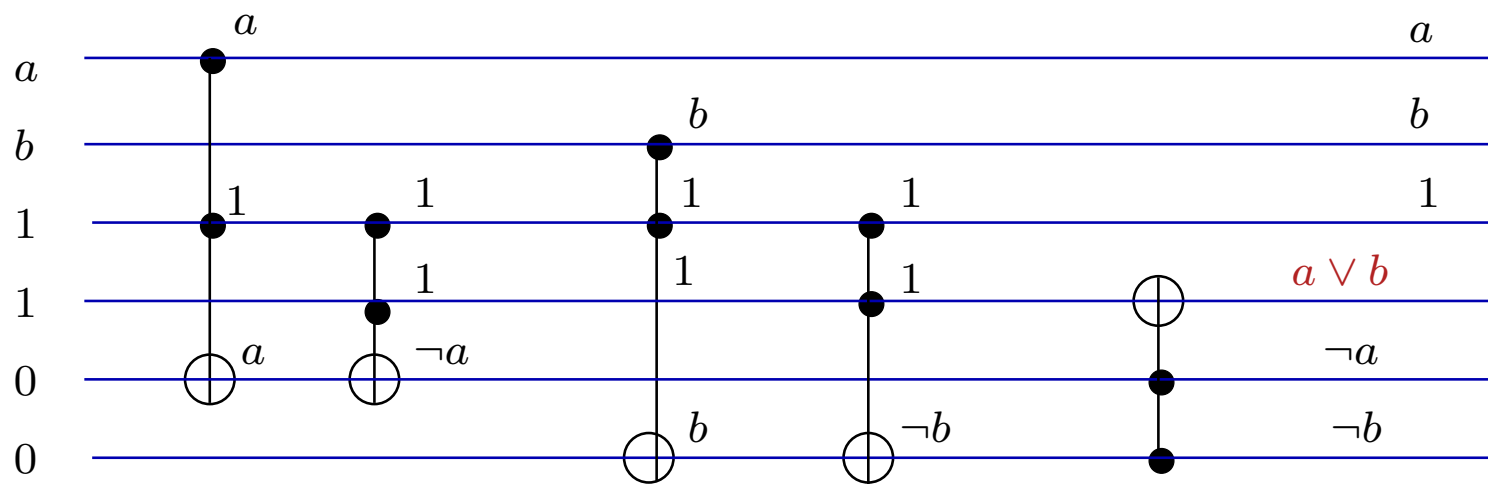

### Note

Note that we have not taken care of **cross-over** of bits in the diagram. There are several **'ancilla'** inputs in state '0' and '1'. Also there are several useless outputs.

### Note

It is not very difficult to create a 3-bit **reversible** transformation that will compute a 2-bit function e.g. **or** when the 3<sup>rd</sup>-bit has a fixed value. Look at the following **truth table**.



## Truth Table

$a$	$b$	$c$	$o_1$	$o_2$	$o_3$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	0	1
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	1	0

When  $c = 0$ ,  $o_3 = a \vee b$ . Other bits are filled to maintain **reversibility**.

## Transition Matrix

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$$

There are three permutations  
(2, 3), (4, 5), (6, 7).

## OR using CCNOT and NOT

- Another way of getting **OR** using **CCNOT** and **NOT** are as follows.
- We negate the input  $a, b$  and keep  $c$  unchanged.
- This can be done by applying the transformation

$$\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \otimes \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \otimes \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

to a **3-bit** vector.

## Tensor Product of Matrices

$$\begin{aligned}
 \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \otimes \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} &= \begin{bmatrix} a_{11} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} & a_{12} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \\ a_{21} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} & a_{22} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \end{bmatrix} \\
 &= \begin{bmatrix} a_{11}b_{11} & a_{11}b_{12} & a_{12}b_{11} & a_{12}b_{12} \\ a_{11}b_{21} & a_{11}b_{22} & a_{12}b_{21} & a_{12}b_{22} \\ a_{21}b_{11} & a_{21}b_{12} & a_{22}b_{11} & a_{22}b_{12} \\ a_{21}b_{21} & a_{21}b_{22} & a_{22}b_{21} & a_{22}b_{22} \end{bmatrix}
 \end{aligned}$$

## Tensor Product $\neg \otimes \neg \otimes I$

$$\begin{aligned}
 & \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \otimes \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \otimes \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \\
 &= \begin{bmatrix} 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \end{bmatrix} \otimes \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}
 \end{aligned}$$

### Tensor Product $\neg \otimes \neg \otimes I$

We encode  $(x, y, c) : (0, 0, 0), \dots, (1, 1, 1)$  as an 8-dimensional Boolean vectors

$000 \equiv (1, 0, \dots, 0), \dots, 111 \equiv (0, \dots, 0, 1)$ .

Operator  $\neg \otimes \neg \otimes I$  gives the desired result.

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} : (1, 0, 0) \mapsto (0, 1, 0).$$

## Tensor Product $CCNOT \circ (\neg \otimes \neg \otimes I)$

- The transformation  $(\neg \otimes \neg \otimes I)$  is clearly reversible (universal property).
- $CCNOT \circ (\neg \otimes \neg \otimes I)$  transforms  $(x, y, c) \mapsto (\neg x, \neg y, c \oplus (\neg x \wedge \neg y))$ .
- We can apply  $\neg \otimes \neg \otimes \neg$  on the result. This gives us  $x \vee y$  when  $c = 0$ .

### Tensor Product $(I \otimes I \otimes \neg)$

$$(\neg \otimes \neg \otimes \neg) \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$

$$(\neg \otimes \neg \otimes \neg) : (0, 1, 0) \mapsto (1, 0, 1)$$



## Fredkin Gate

- Another important 3-input reversible gate is the **Fredkin gate**.
- The input-output relation is  
 $(x, y, c) \mapsto (cy + \bar{c}x, cx + \bar{c}y, c)$  i.e.  
 $(x, y, 0) \mapsto (x, y, 0)$  and  $(x, y, 1) \mapsto (y, x, 1)$ .
- If  $c = 0$ ,  $x, y$  remains unchanged. If  $c = 1$ , the outputs are interchanged.

## Fredkin Gate is Universal


- CROSSOVER:  $(a, b, 1) \mapsto (b, a, 1)$ ,
- NOT and FANOUT:  $(1, 0, a) \mapsto (\bar{a}, a, a)$ ,
- AND:  $(0, b, a) \mapsto (a \wedge b, \bar{a} \wedge b, a)$ ,

## Fredkin Gate Transition Matrix

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Clearly **Fredkin gate** is its own inverse.

## Diagram

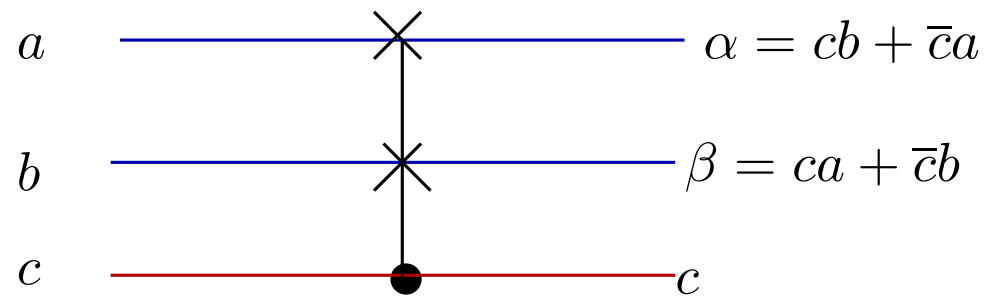


Fredkin



### Note

Both in case of **Toffoli gate** and in **Fredkin gate** we need some 'ancilla' input bits in state '0' or '1' to make them universal. They also produce **useless outputs** not used in subsequent stages.



## Fredkin using CNOT & CCNOT

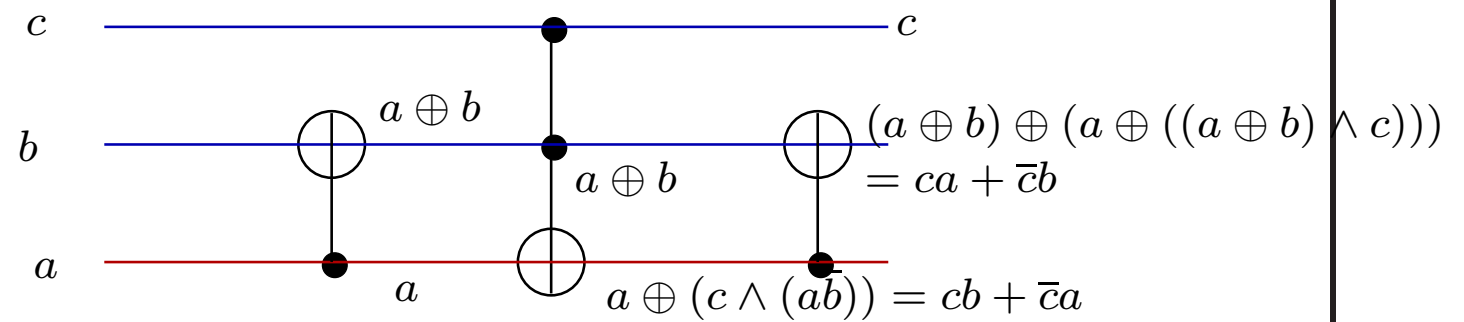

## NOT and FANOUT

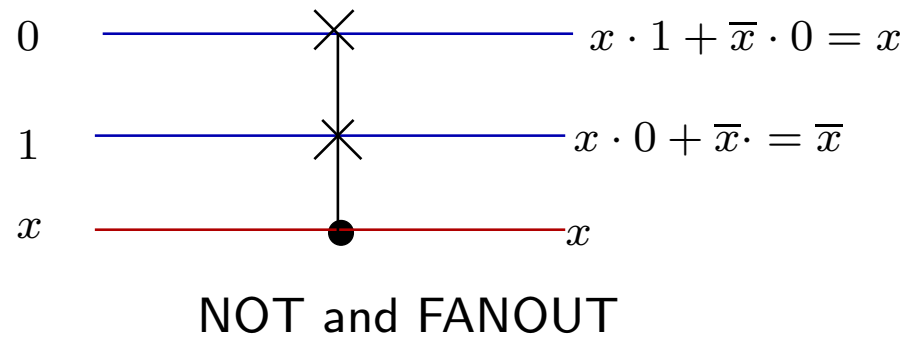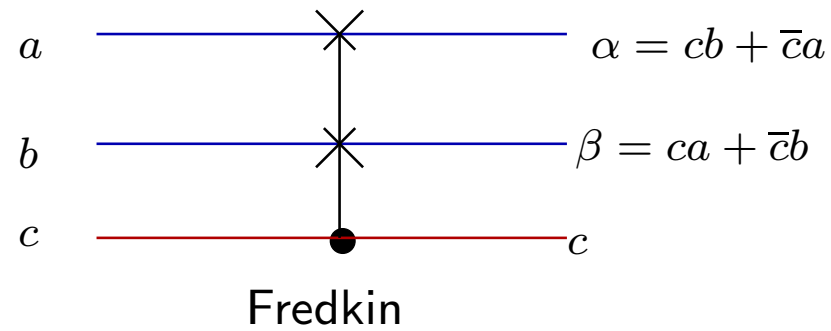

## AND and CCNOT

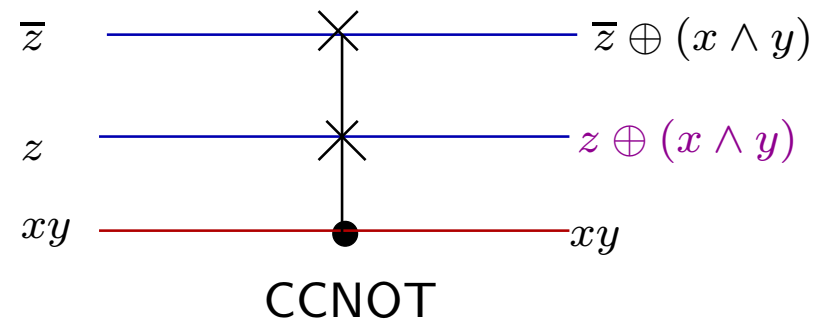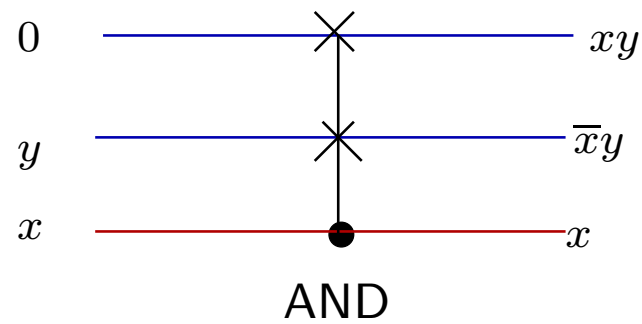




## CCNOT using Fredkin

1.  $c, x$  and  $y$  are actual input. We use several ‘ancilla’ input.
2. Use a Fredkin gate to create a copy of  $y$ .
3. Use the second Fredkin gate to compute  $x \wedge y$ .

### CCNOT using Fredkin

4. Use the third Fredkin gate to copy  $c$ .
5. Finally the fourth Fredkin gate computes  $c \oplus (x \wedge y)$ .
6. There are several output containing useless data.

## CCNOT using Fredkin

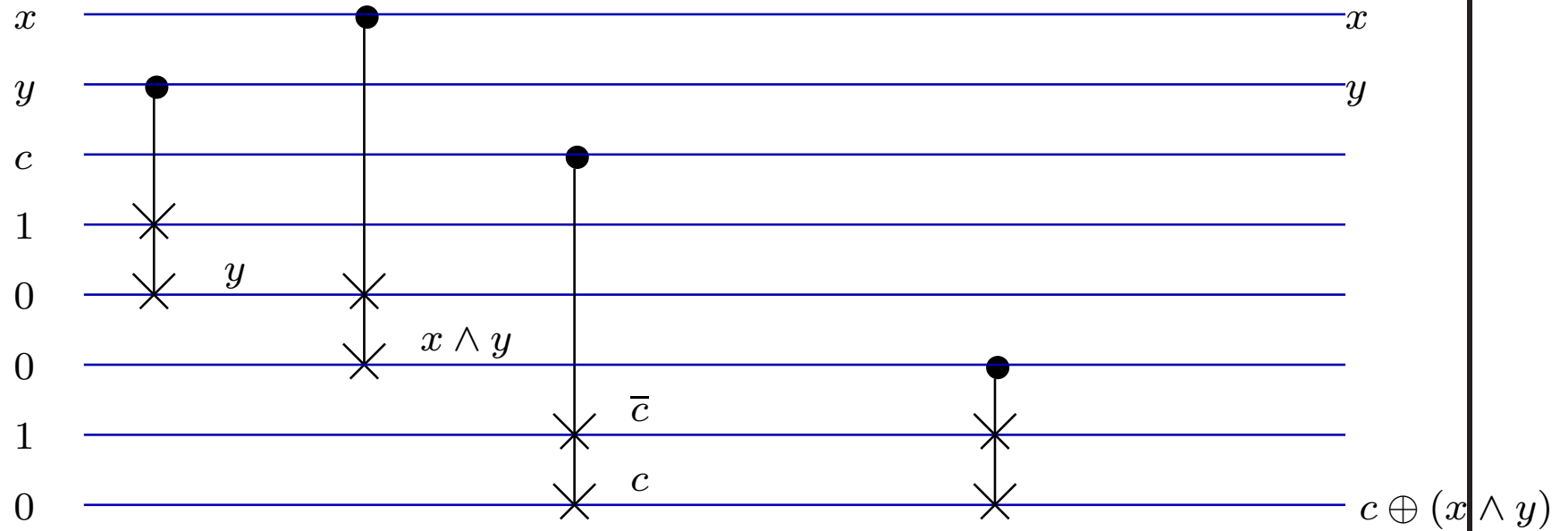

### Note

- We have several **reversible** and **universal** classical gates.
- Their quantum mechanical counterpart can be used to simulate classical computation.

## Probabilistic Circuit

- The linear algebra formalism of classical bits and gates can be generalised to probabilistic circuits.
- Suppose a single-bit is at state 0 with probability  $p$  and at state 1 with a probability  $1 - p$ .
- It is represented as a 2-dimensional real vector  $\begin{bmatrix} p \\ 1 - p \end{bmatrix}$ , where  $p \in [0, 1]$ .

## 1-bit Probabilistic Circuit

Applying our old transformation matrices we get,

$$C_0 \begin{bmatrix} p \\ 1-p \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} p \\ 1-p \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix},$$

$$\neg \begin{bmatrix} p \\ 1-p \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} p \\ 1-p \end{bmatrix} = \begin{bmatrix} 1-p \\ p \end{bmatrix}$$

Transformation matrix for probabilistic bits is **left stochastic** (each column adds to 1).

## 2-bit Probabilistic Circuit

If we consider two bits so that

- the probability is  $p_0$  for the  $0^{th}$ -bit to be 0 and the probability is  $p_1$  for the  $1^{st}$ -bit to be 0.
- The probabilities of 00, 01, 10, 11 are  $p_1p_0, p_1(1 - p_0), (1 - p_1)p_0, (1 - p_1)(1 - p_0)$  respectively.

## 2-bit Probabilistic Circuit

The joint probabilities of two bits may be represented as the following **tensor product** -

$$\begin{bmatrix} p_1 \\ 1 - p_1 \end{bmatrix} \otimes \begin{bmatrix} p_0 \\ 1 - p_0 \end{bmatrix} = \begin{bmatrix} p_1 p_0 \\ p_1 (1 - p_0) \\ (1 - p_1) p_0 \\ (1 - p_1) (1 - p_0) \end{bmatrix} .$$



## Xor-And on Probabilistic Bits

If we apply Xor-And transformation on two probabilistic bits, we get

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} p_1 p_0 \\ p_1(1-p_0) \\ (1-p_1)p_0 \\ (1-p_1)(1-p_0) \end{bmatrix} = \begin{bmatrix} p_1 p_0 \\ (1-p_1)(1-p_0) \\ p_1(1-p_0) + (1-p_1)p_0 \\ 0 \end{bmatrix}.$$

The interpretation of transformation makes sense.

## CNOT on Probabilistic Bits

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} p_1 p_0 \\ p_1(1-p_0) \\ (1-p_1)p_0 \\ (1-p_1)(1-p_0) \end{bmatrix} = \begin{bmatrix} p_1 p_0 \\ p_1(1-p_0) \\ (1-p_1)(1-p_0) \\ (1-p_1)p_0 \end{bmatrix}.$$

Again it has meaningful interpretation.

## References

- [ERWP] Quantum Computing: A Gentle Introduction by Eleanor Rieffel & Wolfgang Polak, Pub. MIT Press, 2011, ISBN 978-0-262-52667-8.
- [MNIC] Quantum Computation and Quantum Information by Michael A Nielsen & Isaac L Chuang, Pub. Cambridge University Press, 2002, ISBN 81-7596-092-2.
- [SA] Quantum Computing Since Democritus by Scott Aaronson, Pub. Cambridge University Press, 2013, ISBN 978-0-521-19956-8.
- [AAM] Classical and Quantum Computation by A Yu Kitaev, A H Shen & M N Vyalyi, Pub. American Mathematical Society (GSM vol 47) 2002, ISBN 978-1-4704-0927-2.

## References

[PRM] An Introduction to Quantum Computing by Phillip Kaye, Raymond Laflamme & Michele Mosca, Pub. Oxford University Press, 2007, ISBN 978-0-19-923677-0.