
Design Verification – *An Introduction*

Testing & Verification


Dept. of Computer Science & Engg, IIT Kharagpur




Pallab Dasgupta

Professor, Dept. of Computer Science & Engg.,
Professor-in-charge, AVLSI Design Lab,
Indian Institute of Technology Kharagpur

Main References

 

 
Hardware Design Verification: *Simulation and Formal Method-Based Approaches*
William K Lam
Prentice Hall Modern Semiconductor Design Series




A Roadmap for Formal Property Verification
Pallab Dasgupta
Springer

Course Web: <http://www.facweb.iitkgp.ernet.in/~pallab> and follow link to courses

Design, Validation and Testing

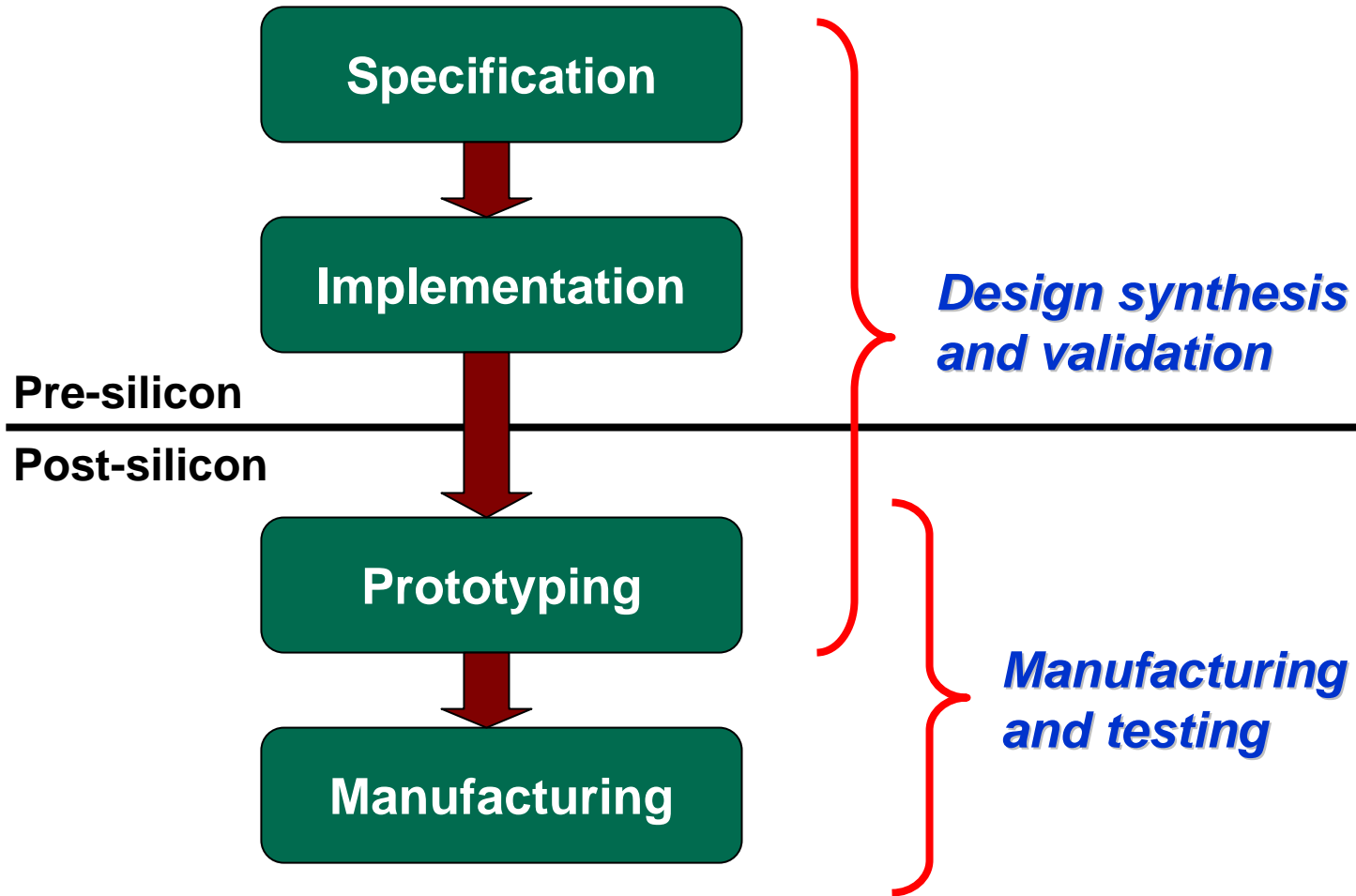

Design and Verification

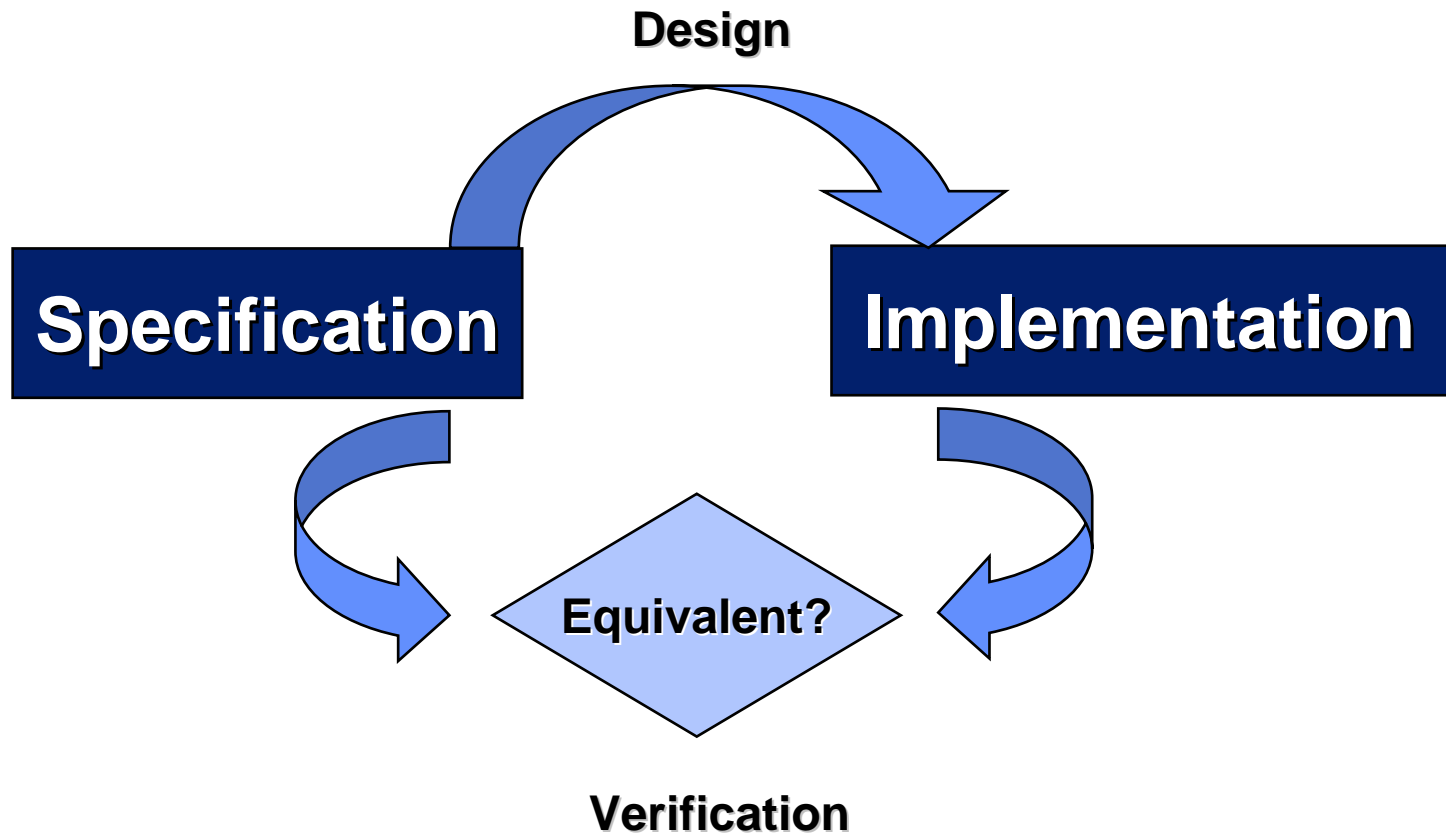

Design Challenges

Suppose we have to design
a pacemaker

Resource optimization

Reduce Cost

*Test automation and
Design-for-Test*

Improve Testability

*Algorithms for
better yield*

Improve Reliability

Improve Verifiability

*Verification reliability
and coverage*

Minimize Power

Power optimization during synthesis

Minimize Area

Area optimization during synthesis

Minimize Delay

Delay optimization during synthesis

Digital Design: Abstraction Levels



Exponential growth
in circuit size
(Moore's Law)



Register Transfer Level

```
always @(posedge clk)
begin
  if (!rst) begin a1 <= a2;
                 a2 <= ~a1; end;
end
```

Formalisms introduced
at the Entry-Level




Restricted semantics of
Programming Languages,
Communicating Concurrent
State Machines (CSM)

Gate Level

  

Boolean Logic
Finite State Machines



Transistor Level

   

Schematic



Design Example: 2-bit Gray Counter

  Gray Counter: Successive values should differ only in one bit. Reset signal resets the counter to zero.



State m/c Representation

Design Example: 2-bit Gray Counter

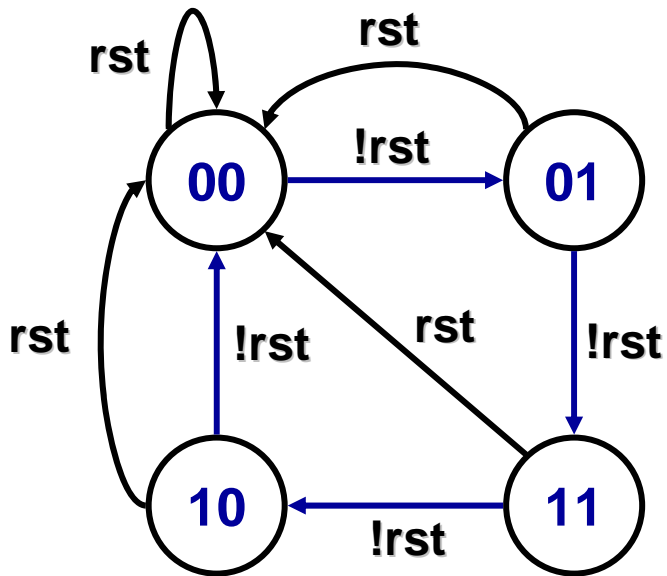 

State m/c Representation

State Transition Table

(s_0s_1)	rst	(n_0n_1)
00	0	01
00	1	00
01	0	11
01	1	00
10	0	00
10	1	00
11	0	10
11	1	00

Design Example: 2-bit Gray Counter

State Transition Table

(s_0s_1)	rst	(n_0n_1)
00	0	01
00	1	00
01	0	11
01	1	00
10	0	00
10	1	00
11	0	10
11	1	00

State Transition Functions:

$$n_0 = s_0's_1r' + s_0s_1r'$$

$$n_1 = s_0's_1'r' + s_0's_1r'$$

After Logic Minimization:

$$n_0 = s_1r'$$

$$n_1 = s_0'r'$$

Design Example: 2-bit Gray Counter

State Transition Functions:

$$n_0 = s_1 r'$$

$$n_1 = s_0' r'$$


Verilog Code (RTL):

```
module GrayCounter(s0, s1, rst)
input rst;
reg s0, s1;


always @ (posedge clk)
begin
    s0 <= s1 & ~rst;
    s1 <= ~s0 & ~rst;
end
endmodule
```



Synthesis

 

Abstractions in Design Flow

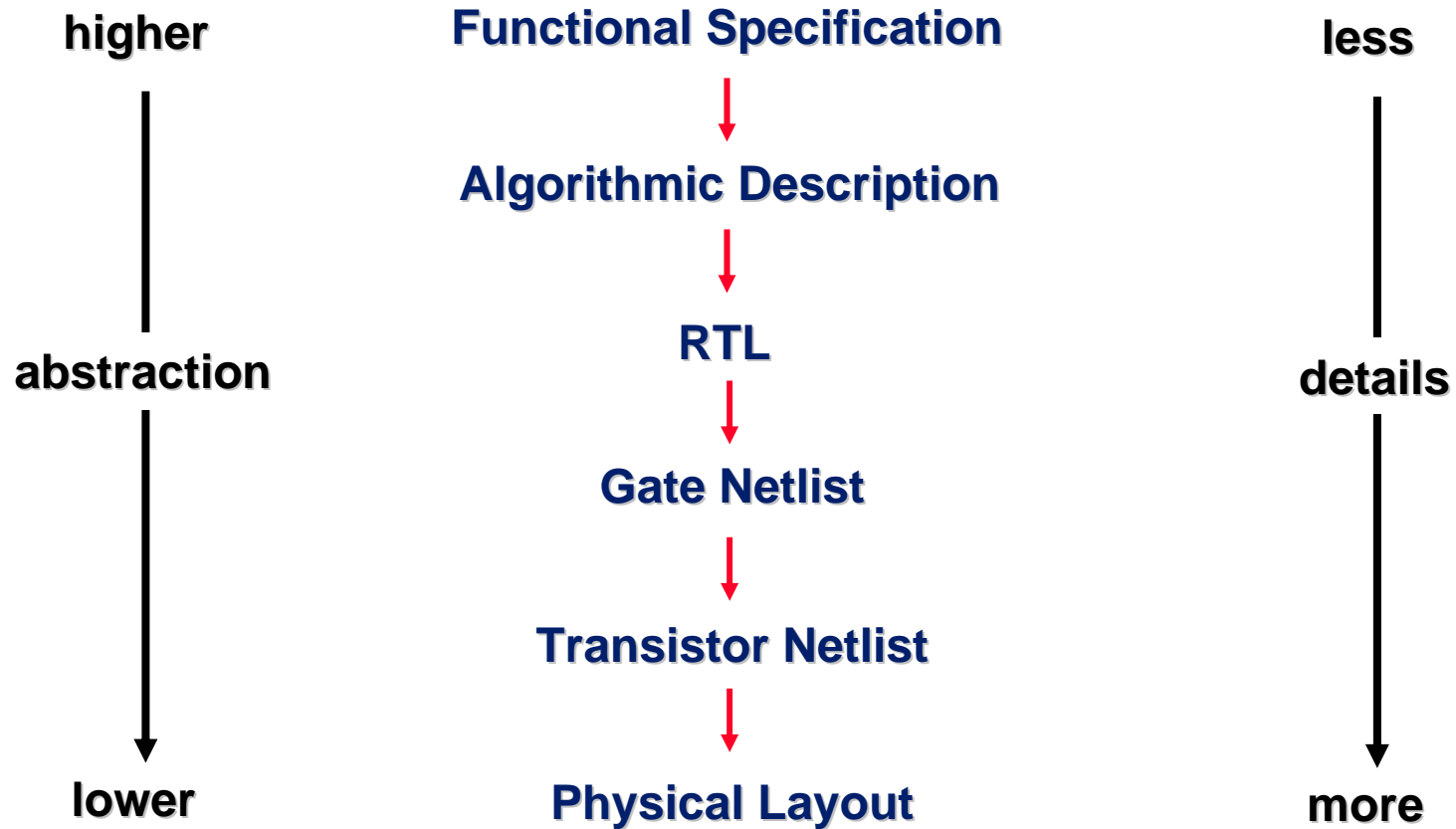

Design and Verification

