

# Switching Circuits and Logic Design

## CS21002 (section-1)

### Tutorial 2

---

1. Show that if there is a  $n$ -bit single-error correcting code for encoding objects in  $\{0, \dots, m-1\}$ , then  $m(n+1) \leq 2^n$ . Conclude that there is no single error correcting 6-bit code for decimal digits.
2. Show that the only sum-of-products representation of the parity function is the canonical sum of minterms representation.
3. Design a two-level code converter from BCD to 2-out-of-5.
4. You are supplied with just one NOT gate and an unlimited amount of AND and OR gates and are required to design a circuit that realizes the expression  $T(w, x, y, z) = w'x + x'y + xz'$ . Only unprimed variables are available as inputs.  
*Hint: You may find the map of  $T$  helpful.*
5. (a) Define a half subtractor, show its truth tables, and derive logic expressions for difference (D) and borrow (B) outputs.  
(b) Define a full subtractor, show its truth tables, and derive logic expressions for difference (D) and borrow (B) outputs.
6. A communication system is designed to transmit just two code words,  $A = 0010$  and  $B = 1101$ . However, owing to noise in the system, the received word may have as many as two errors. Design a combinational circuit that receives the words and that can correct one error and detect the existence of two errors. The circuit receives a 4-bit word ( $X = X_0X_1X_2X_3$ ) as input, and produces three switching output  $A$ ,  $B$  and  $C$ . On each input, exactly one output bit is 1. Output  $A$  will be equal to 1 if the transmitted word is  $A$  and there has been at most one error, output  $B$  will be equal to 1 if the transmitted word is  $B$  and there has been at most one error, and output  $C$  will be equal to 1 if the word received has two errors and thus cannot be corrected.

7. With the aid of a four-variable Karnaugh map, derive minimal sum-of-products expressions for each of the following functions:
- (a)  $f_1(w, x, y, z) = \sum(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$ ;
- (b)  $f_2(w, x, y, z) = \sum(0, 1, 5, 7, 8, 10, 14, 15)$ ;
- (c)  $f_3(w, x, y, z) = \sum(0, 2, 4, 5, 6, 8, 10, 12)$ .
8. Find the minimal sum-of-products and minimal product-of-sums expressions for  $f(w, x, y, z) = \prod(1, 4, 5, 6, 11, 12, 13, 14, 15)$ . Is your answer unique?
9. Given the function  $T(w, x, y, z) = \sum(1, 2, 3, 5, 13) + \sum(6, 7, 8, 9, 11, 15)$ :
- (a) find a minimal sum-of-products expression;
- (b) find a minimal product-of-sums expression;
- (c) compare the expressions obtained in (a) and (b); if they do not represent identical functions, explain why.
10. Figure out the adjacencies of a six-variable map. Show the representation of  $T(u, v, w, x, y, z) = u'w'y' + uwy + w'xy'z$ .
11. Show maps for four-variable functions with the following specifications. If this is impossible, explain why.
- (a) A function with eight minterms for which
- (i) there are no essential prime implicants.
- (ii) all the prime implicants are essential.
- (b) Repeat (a) for functions with nine minterms.
- (c) A function with an even number of prime implicants, of which exactly half are essential.
- (d) A function with six prime implicants, of which four are essential and two are covered by essential ones.
12. (a) Let  $f(x_1, x_2, \dots, x_n)$  be equal to 1 if and only if exactly  $k$  of the variables equal 1. How many prime implicants does this function have?
- (b) Repeat (a) for the case where  $f$  assumes the value 1 if and only if  $k$  or more of the variables are equal to 1.