 


# COMPUTER ARCHITECTURE



## Processor: Multi- Cycle Datapath & Control

(Based on text: David A. Patterson & John L. Hennessy, *Computer Organization and Design: The Hardware/Software Interface*, 3<sup>rd</sup> Ed., Morgan Kaufmann, 2007)



# COURSE CONTENTS

---

- Introduction
- Instructions
- Computer Arithmetic
- Performance
- **Processor: Datapath**
- **Processor: Control**
- Pipelining Techniques
- Memory
- Input/Output Devices

# PROCESSOR: DATAPATH & CONTROL



---

- Multi-Cycle Datapath
- Multi-Cycle Control
- Additional Registers and Multiplexers




# Multicycle Approach

---

- Break up an instruction into steps, each **step** takes a **cycle**:
  - **balance** the amount of work to be done
  - restrict each cycle to use only **one** major functional unit
  - Different instructions take **different** number of cycles to complete
- At the **end** of a **cycle**:
  - store values for use in later cycles (easiest thing to do)
  - introduce additional “internal” **registers** for such **temporal** storage
- **Reusing** functional units (reduces hardware cost):
  - Use **ALU** to compute address/result and to increment PC
  - Use **memory** for both instructions and data

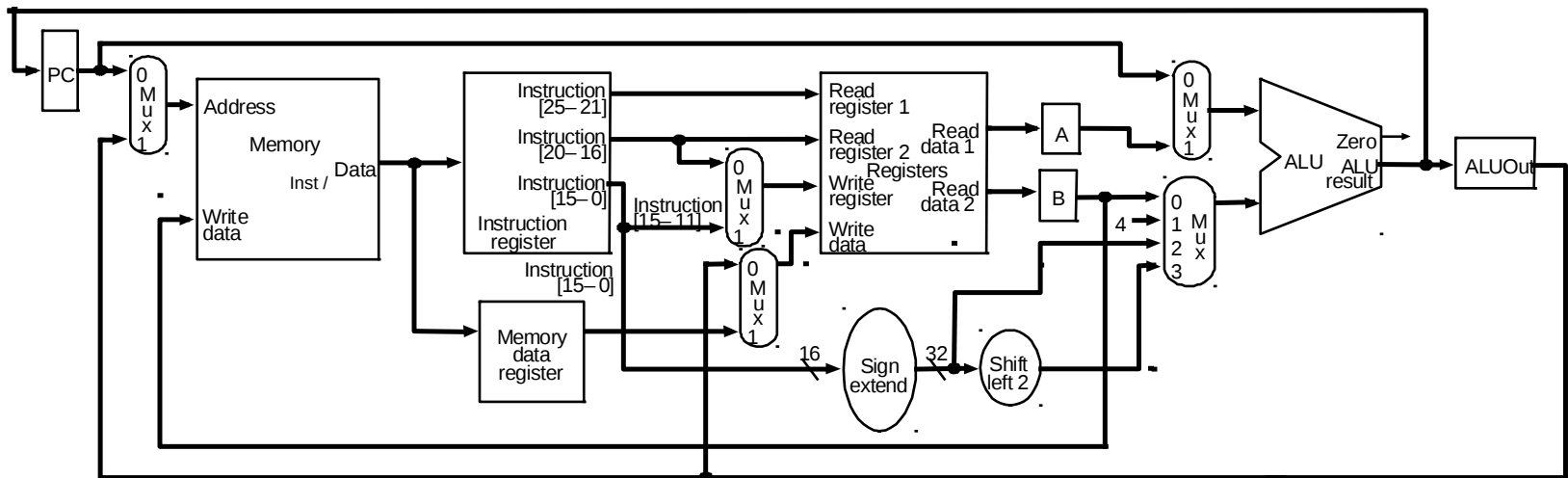
# Multi-Cycle Datapath: Additional Registers

- Additional “internal registers”:
  - Instruction register (**IR**) -- to hold current instruction
  - Memory data register (**MDR**) -- to hold data read from memory
  - A register (**A**) & B register (**B**) -- to hold register operand values from register files
  - ALUOut register (**ALUOut**) -- to hold output of ALU, also serves as memory address register (MAR)
- All registers except IR hold data only between a pair of **adjacent** cycles and thus do **not** need **write** control signals; IR holds instructions till **end** of instruction, hence **needs** a **write** control signal



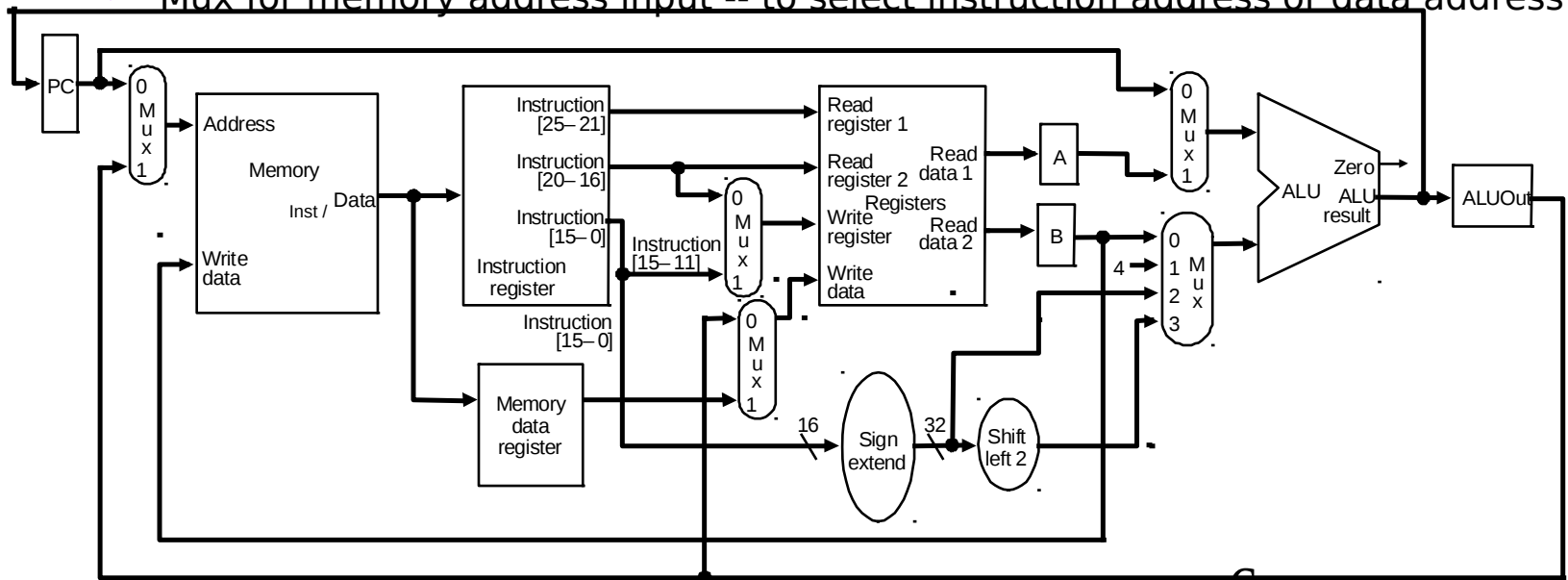
# Multicycle Datapath: Additional Multiplexors

- Additional multiplexors:
  - ✦ Mux for first ALU input -- to select A or PC (since we use ALU for both address/result computation & PC increment)
  - ✦ Bigger mux for second ALU input -- due to two additional inputs: 4 (for normal PC increment) and the sign-extended & shifted offset field (in branch address computation)
  - ✦ Mux for memory address input -- to select instruction address or data address



# Multi-Cycle Datapath & Control

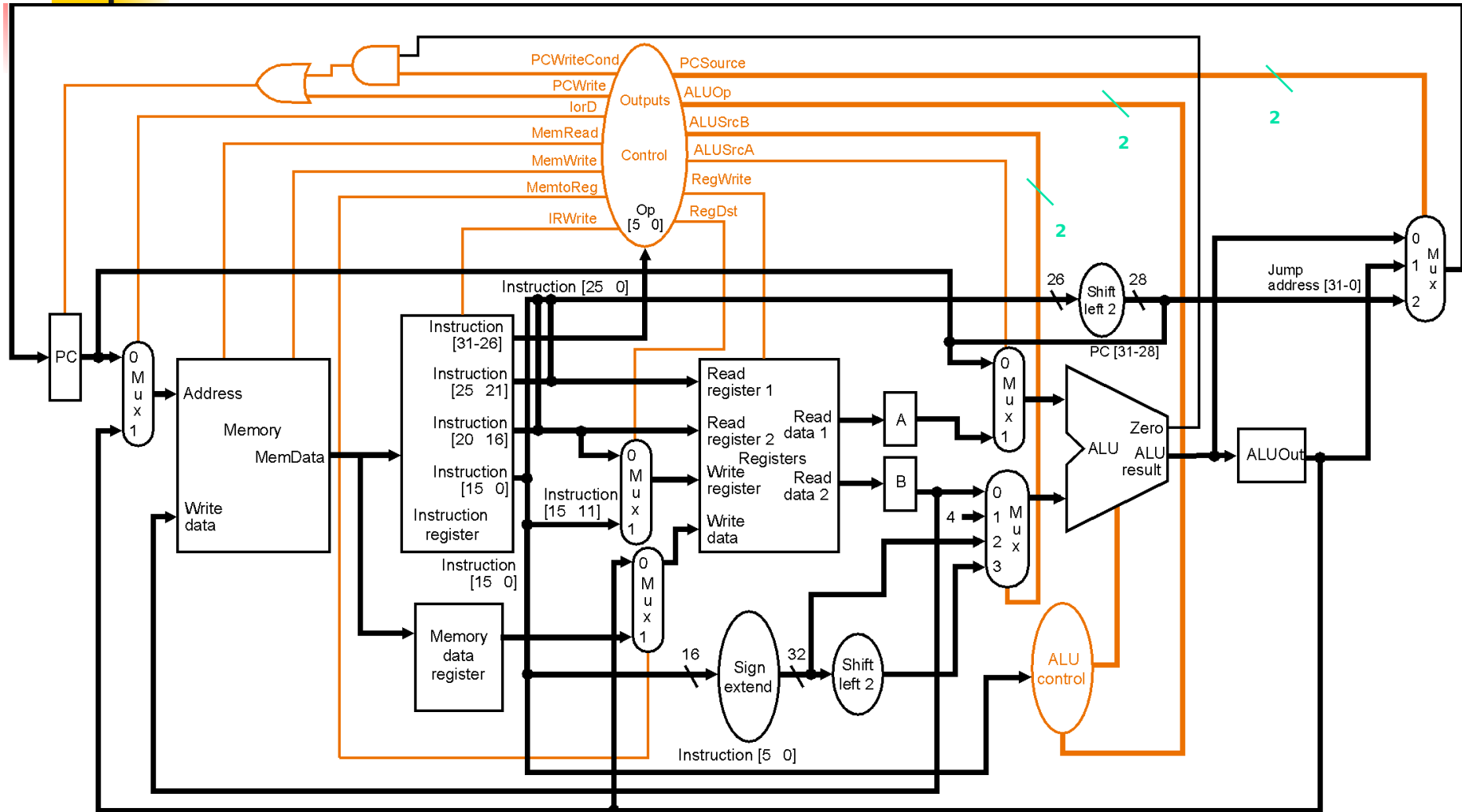

Note the reason for each control signal; also note that we have included the jump instruction



# Control Signals for Multi-Cycle Datapath

---

- Note:
  - three possible sources for value to be written into PC (controlled by **PCSource**): (1) regular increment of PC, (2) conditional branch target from ALUOut, (3) unconditional jump (lower 26 bits of instruction in IR shifted left by 2 and concatenated with upper 4 bits of the incremented PC)
  - two PC write control signals: (1) **PCWrite** (for unconditional jump), & (2) **PCWriteCond** (for “zero” signal to cause a PC write if asserted during beq inst.)
  - since memory is used for both inst. & data, need **lorD** to select appropriate addresses
  - **IRWrite** needed for IR so that instruction is written to IR (IRWrite = 1) during the first cycle of the instruction and to ensure that IR not be overwritten by another instruction during the later cycles of the current instruction execution (by keeping IRWrite = 0)
  - other control signals




# Breaking the Instruction into 3 - 5 Execution Steps

1. Instruction Fetch (All instructions)
2. Instruction Decode (All instructions), Register Fetch & Branch Address Computation (in advance, just in case)
3. ALU (R-type) execution, Memory Address Computation, or Branch Completion (Instruction dependent)
4. Memory Access or R-type Instruction Completion (Instruction dependent)
5. Memory Read Completion (only for lw)

*At end of every clock cycle, needed data must be stored into register(s) or memory location(s).*

*Each step (can be several parallel operations) is 1 clock cycle --> Instructions take 3 to 5 cycles!*

Events during a cycle, e.g.:

 



# Step 1: Instruction Fetch

---

- Use PC to get instruction (from memory) and put it in the Instruction Register
- Increment of the PC by 4 and put the result back in the PC
- Can be described succinctly using RTL "Register-Transfer Language"

```
IR <= Memory[PC];  
PC <= PC + 4;
```

- *Which control signals need to be asserted?*
  - $\text{lorD} = 0, \text{MemRead} = 1, \text{IRWrite} = 1$
  - $\text{ALUSrcA} = 0, \text{ALUSrcB} = 01, \text{ALUOp} = 00, \text{PCWrite} = 1, \text{PCSource} = 00$
- *Why can instruction read & PC update be in the same step? Look at state element timing*
- *What is the advantage of updating the PC now?*

# Step 2: Instruction Decode, Reg. Fetch, & Branch Addr. Comp.

- In this step, we **decode** the instruction in IR (the opcode enters control unit in order to generate control signals). **In parallel**, we can
- Read registers rs and rt, *just in case* we need them
- Compute the branch address, *just in case* the instruction is a branch beq
- RTL:

```
A <= Reg[IR[25:21]];
B <= Reg[IR[20:16]];
ALUOut <= PC + (sign-extend(IR[15:0]) << 2);
```

- Control signals:
  - ALUSrcA = 0, ALUSrcB = 11, ALUOp = 00 (add)
  - Note: no explicit control signals needed to write A, B, & ALUOut. They are written by clock transitions automatically at **end of step**

# Step 3: Instruction Dependent Operation

- One of four functions, **based on** instruction type:
- Memory address computation (for lw, sw):  
$$\text{ALUOut} \leq A + \text{sign-extend}(\text{IR}[15:0]);$$
  - Control signals:  $\text{ALUSrcA} = 1, \text{ALUSrcB} = 10, \text{ALUOp} = 00$
- ALU (R-type):  
$$\text{ALUOut} \leq A \text{ op } B;$$
  - Control signals:  $\text{ALUSrcA} = 1, \text{ALUSrcB} = 00, \text{ALUOp} = 10$
- Conditional branch:  
$$\text{if } (A == B) \text{ PC} \leq \text{ALUOut};$$
  - Control signals:  $\text{ALUSrcA} = 1, \text{ALUSrcB} = 00, \text{ALUOp} = 01$  (Sub),  
 $\text{PCSource} = 01, \text{PCWriteCond} = 1$  (to enable zero to write PC if 1)

*What is the content of ALUOut during this step? Immediately after this step?*
- Jump:  
$$\text{PC} \leq \text{PC}[31:28] \ || \ (\text{IR}[25:0] \ll 2);$$
  - Control signals:  $\text{PCSource} = 10, \text{PCWrite} = 1$

✓ *Note: Conditional branch & jump instructions completed at this step!*

# Step 4: Memory Access or ALU

## (R-type) Instruction Completion

- For lw or sw instructions (access memory):

MDR  $\leq$  Memory[ALUOut];  
or  
Memory[ALUOut]  $\leq$  B;

- Control signals (for lw):  $\text{lorD} = 1$  (to select ALUOut as address),  $\text{MemRead} = 1$ , note that no write signal needed for writing to MDR, it is written by clock transition automatically at end of step
- Control signals (for sw):  $\text{lorD} = 1$  (to select ALUOut as address),  $\text{MemWrite} = 1$
- For ALU (R-type) instructions (write result to register):

$\text{Reg}[\text{IR}[15:11]] \leq \text{ALUOut};$

- Control signals:  $\text{RegDst} = 1$  (to select register address),  $\text{MemtoReg} = 0$ ,  $\text{RegWrite} = 1$



# Step 5: Memory Read Completion

---

- For lw instruction only (write data from MDR to register):

`Reg[IR[20:16]] <= MDR;`

- Control signals: RegDst = 0 (to select register address), MemtoReg = 1, RegWrite = 1

✓ *Note: lw instruction completed at this step!*



# Summary of Execution Steps

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR $\leftarrow$ Memory[PC] PC $\leftarrow$ PC + 4			
Instruction decode/register fetch	A $\leftarrow$ Reg [IR[25:21]] B $\leftarrow$ Reg [IR[20:16]]			
/branch addr comp	ALUOut $\leftarrow$ PC + (sign-extend (IR[15:0]) $\ll$ 2)			
Execution, address computation, branch/ jump completion	ALUOut $\leftarrow$ A op B	ALUOut $\leftarrow$ A + sign-extend (IR[15:0])	if (A == B) then PC $\leftarrow$ ALUOut	PC $\leftarrow$ PC [31:28]    (IR[25:0] $\ll$ 2)
Memory access or R-type completion	Reg [IR[15:11]] $\leftarrow$ ALUOut	Load: MDR $\leftarrow$ Memory[ALUOut] or Store: Memory [ALUOut] $\leftarrow$ B		
Memory read completion		Load: Reg[IR[20:16]] $\leftarrow$ MDR		

*Some instructions take shorter number of cycles, therefore next instructions can start earlier.*

*Hence, compare to single-cycle implementation where all instructions take same amount of time, multi-cycle implementation is faster!*

*Multi-cycle implementation also reduces hardware cost (reduces adders & memory, increases number of registers & muxes)*



# Simple Questions

---

- How many cycles will it take to execute this code?

```
        lw $t2, 0($t3)
        lw $t3, 4($t3)
        beq $t2, $t3, Label1           #assume not
        add $t5, $t2, $t3
        sw $t5, 8($t3)
Label1:    ...
```

- What is going on during the 8th cycle of execution?
- In what cycle does the actual addition of \$t2 and \$t3 takes place?

