

# Latches and Flip Flops

# Basic Stable Memory Element


 


Fig.1: Two cascaded inverters along with their superimposed VTCs.

# Bistable Multivibrators

 

# Latch

- Bistable multivibrator
- State change triggers
  - Level triggered
  - Clock edge triggered (Flip Flops)

# Memory Elements and Their Excitation Functions



To generate the  $Y$ 's: memory devices must be supplied with appropriate input values

- Excitation functions: switching functions that describe the impact of  $x_i$ 's and  $y_j$ 's on the memory-element input
- Excitation table: its entries are the values of the memory-element inputs

Most widely used memory elements: flip-flops, which are made of latches

- Latch: remains in one state indefinitely until an input signals directs it to do otherwise

# Set-Reset (SR) Latch (NOR Gate)

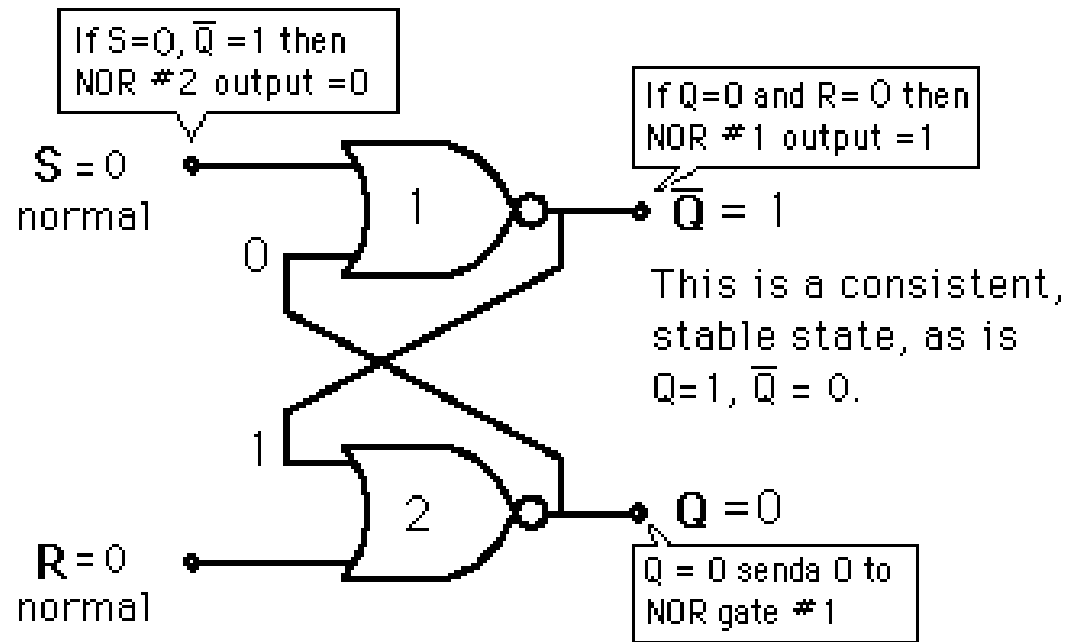 


Truth Table

Set	Reset	Output
0	0	No change*
1	0	$Q=1$
0	1	$Q=0$
1	1	Invalid state


\*can be used for data storage
 
# Working


$(R, S) = (0, 0) \rightarrow$  Hold the previous state as  $(Q_{next}, \overline{Q}_{next}) = (Q, \overline{Q})$



 
$(R, S) = (1, 0) \rightarrow$  Reset as  $(Q_{next}, \overline{Q}_{next}) = (0, 1)$



 
$(R, S) = (0, 1) \rightarrow$  Set as  $(Q_{next}, \overline{Q}_{next}) = (1, 0)$



 $(R, S) = (0, 1) \rightarrow$  Not allowed as  $(Q_{next}, \overline{Q}_{next}) = (0, 0)$  that is not logical



# Set-Reset (SR) Latch (NAND Gate)

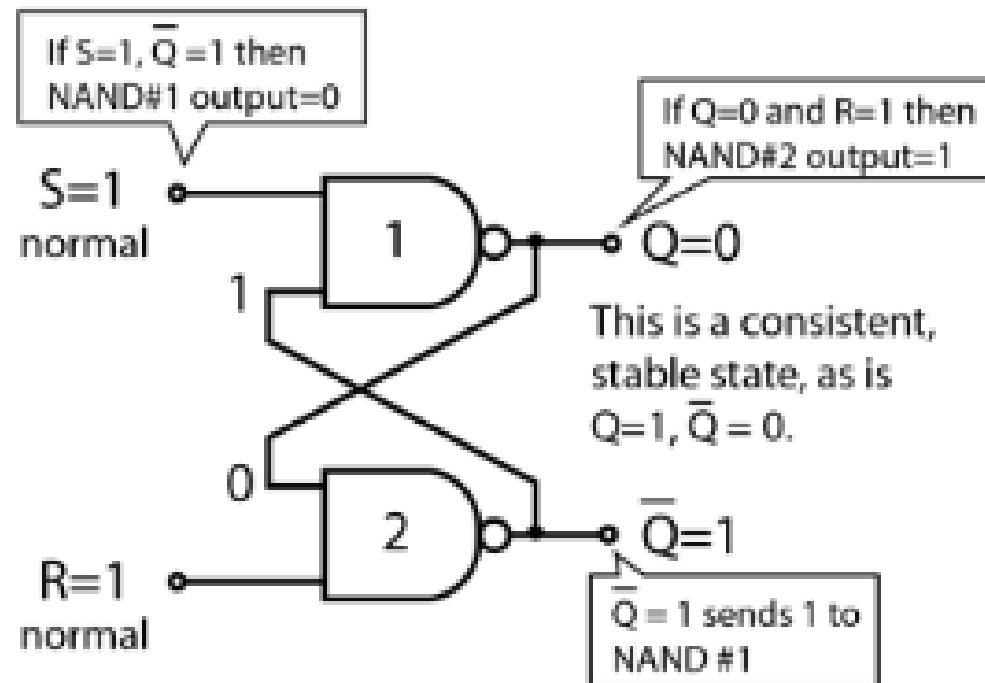

Truth Table


Set	Reset	Output
1	1	No change*
0	1	$Q=1$
1	0	$Q=0$
0	0	Invalid state

\* can be used for data storage



 
# Chatterless Switch



Mechanical switch contacts bounce, taking on the order to milliseconds to settle to their final contact.



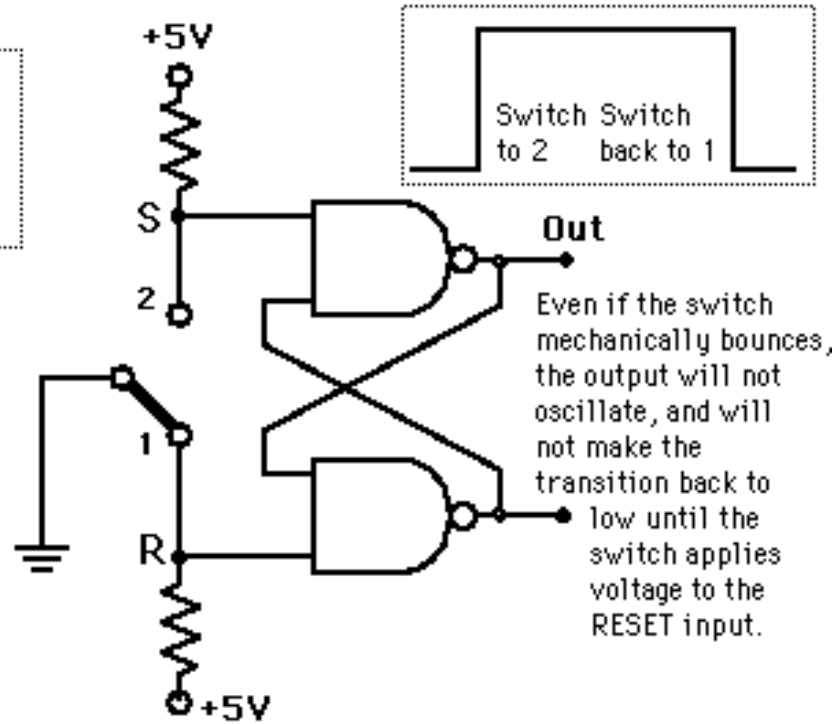
A **NAND gate latch** will take the output to supply voltage in a time on the order of nanoseconds.



# Clocked/Gated SR Latch

 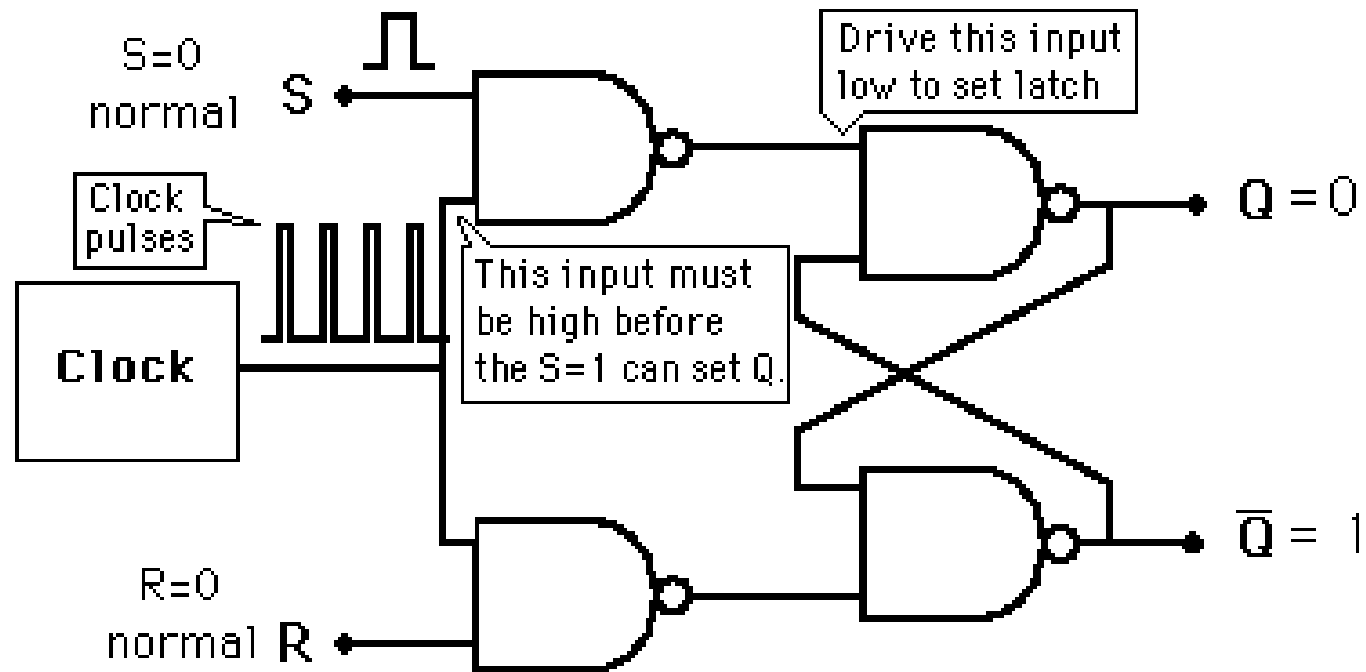


# Timing the SR latch

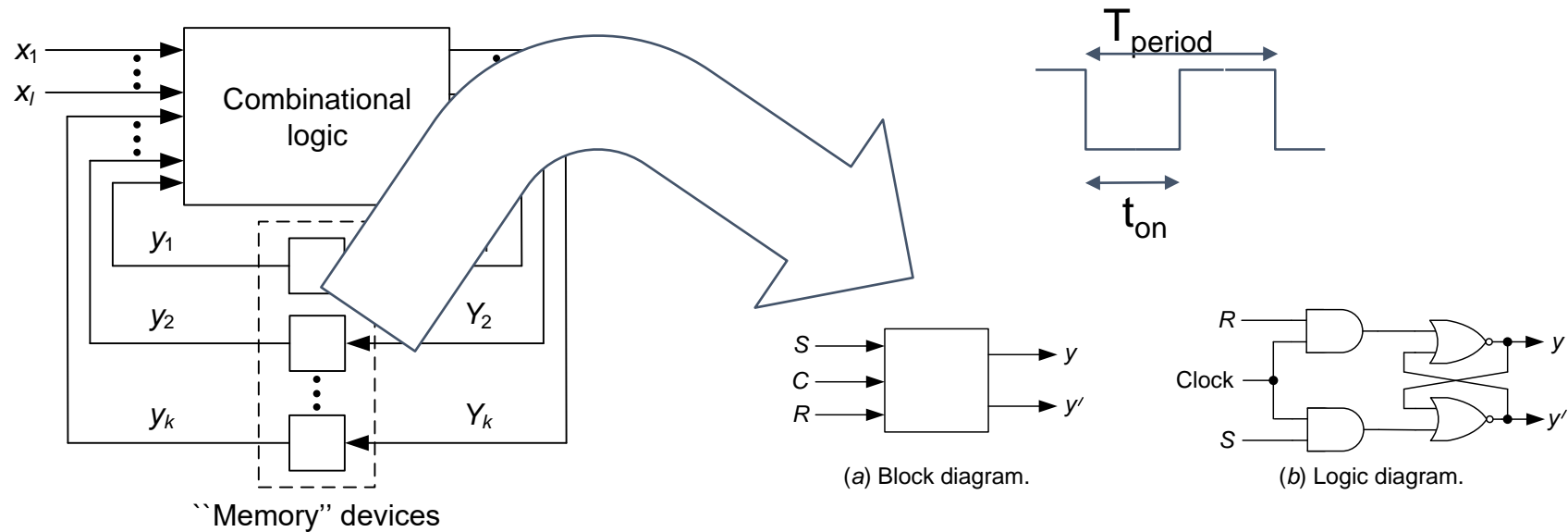


- A clock is a periodic signal that is used to keep time in sequential circuits.
- Duty Cycle is the ration of  $t_{\text{on}}/T_{\text{period}}$
- We want to keep  $t_{\text{on}}$  small so that in the same clock pulse only a single computation is performed.
- We want to keep  $T_{\text{period}}$  sufficient so that there is enough time for the next input to be computed.
 
# Trigger or $T$ Latch

Value 1 applied to its input triggers the latch to change state



(a) Block diagram.

 

(b) Deriving the T latch from the clocked SR latch.

Excitations requirements:

<i>Circuit change</i>		<i>Required value T</i>
<i>From:</i>	<i>To:</i>	
0	0	0
0	1	1
1	0	1
1	1	0


$$\begin{aligned}
 y(t+1) &= Ty'(t) + T'y(t) \\
 &= T \oplus y(t)
 \end{aligned}$$

# The $JK$ Latch

Unlike the  $SR$  latch,  $J = K = 1$  is permitted: when it occurs, the latch acts like a trigger and switches to the complement state



(a) Block diagram.

 

(b) Constructing the JK latch from the clocked SR latch.


Excitation requirements:

<i>Circuit change</i>		<i>Required value</i>	
<i>From:</i>	<i>To:</i>	<i>J</i>	<i>K</i>
0	0	0	–
0	1	1	–
1	0	–	1
1	1	–	0


# The $D$ Latch

The next state of the  $D$  latch is equal to its present excitation:

$$y(t+1) = D(t)$$

 

(a) Block diagram.

 

(b) Transforming the JK latch to the D latch.

# Clock Timing


**Clocked latch:** changes state only in synchronization with the clock pulse and no more than once during each occurrence of the clock pulse

**Duration of clock pulse:** determined by circuit delays and signal propagation time through the latches


- Must be long enough to allow latch to change state, and
- Short enough so that the latch will not change state twice due to the same excitation

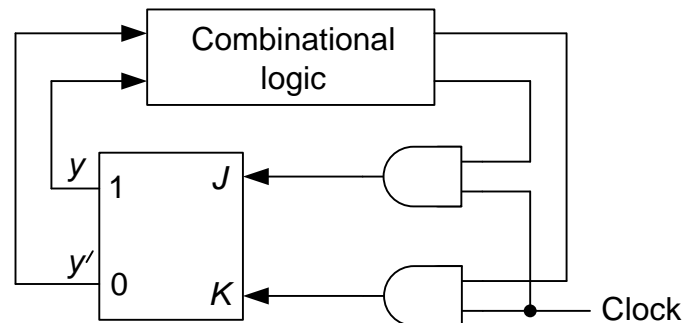**Excitation of a *JK* latch within a sequential circuit:**

- Length of the clock pulse must allow the latch to generate the *y*'s
- But should not be present when the values of the *y*'s have propagated through the combinational circuit




# JK Flip Flop

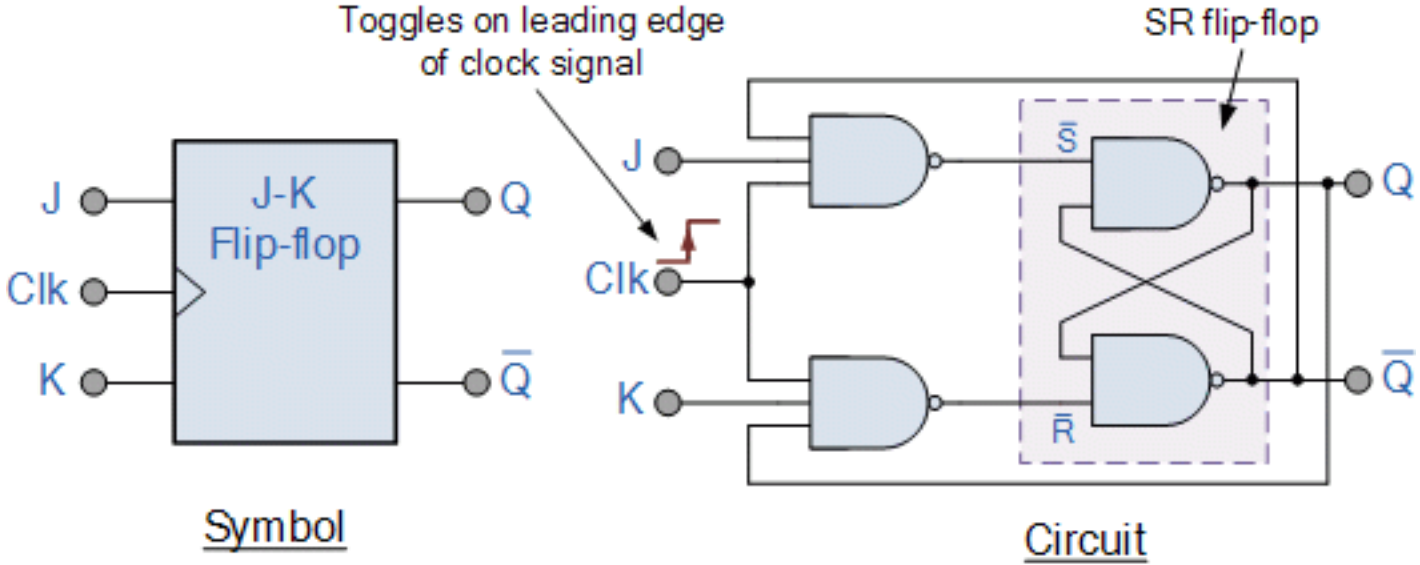

Characteristic table				Excitation table				
J	K	Comment	$Q_{next}$	Q	$Q_{next}$	Comment	J	K
0	0	Hold state	Q	0	0	No change	0	X
0	1	Reset	0	0	1	Set	1	X
1	0	Set	1	1	0	Reset	X	1
1	1	Toggle	$\bar{Q}$	1	1	No change	X	0




# Master Slave JK Flip Flop

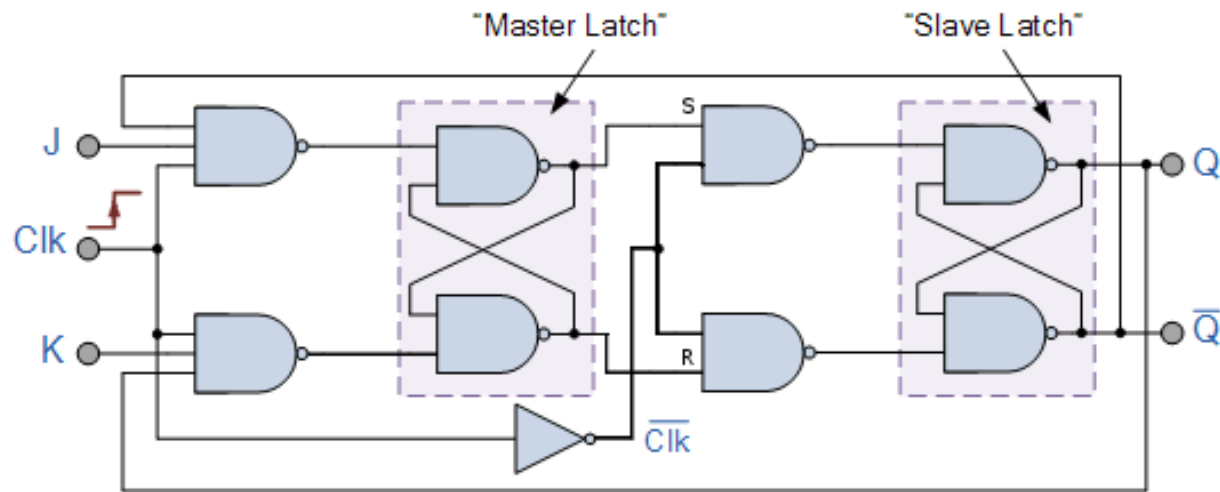


Truth table

Clk	J	K	Q	Q New
0	Master: NC; MLat $\rightarrow$ SLat			
1	Slave: NC			
1 $\rightarrow$ 0	0	0	—	MLat $\rightarrow$ SLat
	0	1	—	0 (S=0, R=1)
	1	0	—	1 (S=1, R=0)
	1	1	1	0 (S=0, R=1)
	1	1	0	1 (S=1, R=0)
 
# D Flip Flop with Asynchronous Preset Clear


 
# D Flip Flop with Synchronous Preset Clear



# Residual problem with above DFF

- Let the gate delay be  $\Delta$
  - Let  $D=0$ ,  $Clk=1$
  - Let  $D=1$  and just before  $\Delta$  time,  $Clk=0$
  - Master latch has the invalid input combination of 00
  - Before valid inputs could appear at the steering gates of the master latch,  $Clk=0$
  - Now, invalid input combination of 11 is presented to the slave steering gates, with  $Clock'=1$
  - Slave latch has the invalid input combination of 00
  - Output of DFF is indeterminate
- 
- Problem may be avoided if  $D$  remains steady when  $Clk=1$ , allowed to change only when  $Clk=0$

# Setup and hold times

- Setup time: It is defined as the minimum amount of time *before* the active clock edge by which the data must be stable for it to be latched correctly; any violation in this required time causes incorrect data to be captured and is known as a setup violation

Time available for data at D2 to reach D1 after active clock edge


$$T_{\text{clk}} + T_{\text{skew}} - T_{\text{setup}}$$

Time needed for data to reach D1 from D2 after active clock edge

$$T_{\text{c2q}} + T_{\text{comb}}$$

Resulting constraint
 
$$T_{\text{c2q}} + T_{\text{comb}} \leq T_{\text{clk}} + T_{\text{skew}} - T_{\text{setup}}$$
$$T_{\text{c2q}} + T_{\text{comb}} + T_{\text{setup}} \leq T_{\text{clk}} + T_{\text{skew}}$$



# Hold time

It is defined as the minimum amount of time *after* the active clock edge by which the data must be stable for it to be latched correctly; any violation in this required time causes incorrect data to be captured and is known as a hold violation

Minimum time for data at D2 to reach D1 after active clock edge

$$T_{c2q} + T_{comb}$$

Time for data to remain steady at D1 after active clock edge

$$T_{sreq} + T_{hold}$$

Resulting constraint

$$T_{c2q} + T_{comb} \geq T_{sreq} + T_{hold}$$


# Edge-triggered Flip-flop

Positive (negative) edge-triggered  $D$  flip-flop: stores the value at the  $D$  input when the clock makes a  $0 \rightarrow 1$  ( $1 \rightarrow 0$ ) transition


- Any change at the  $D$  input after the clock has made a transition does not have any effect on the value stored in the flip-flop

A negative edge-triggered  $D$  flip-flop:

- When the clock is high, the output of the bottommost (topmost) NOR gate is at  $D'$  ( $D$ ), whereas the  $S$ - $R$  inputs of the output latch are at 0, causing it to hold previous value
- When the clock goes low, the value from the bottommost (topmost) NOR gate gets transferred as  $D$  ( $D'$ ) to the  $S$  ( $R$ ) input of the output latch
  - Thus, output latch stores the value of  $D$
- If there is a change in the value of the  $D$  input after the clock has made its transition, the bottommost NOR gate attains value 0
  - However, this cannot change the  $SR$  inputs of the output latch

 

# Positive Edge Triggered DFF

 


- $S_{\Delta} = (C \cdot A)' = C' + A' = C' + B \cdot S = C' + (D' + R') \cdot S$
- $R_{\Delta} = (S \cdot C \cdot B)' = S' + C' + B' = S' + C' + R \cdot D$
- As long as  $C = 0$ ,  $R = S = 1$  and the output latch retains its older value
- When  $C$  changes from 0 to 1,  $R$  and  $S$  change as follows:
  - If  $D=0$ :  $R_{\Delta} = 0$ ,  $S_{\Delta} = 1$  (from  $R = S = 1$ ) and  $Q=0$
  - If  $D=1$ :  $R_{\Delta} = 1$ ,  $S_{\Delta} = 0$  (from  $R = S = 1$ ) and  $Q=1$
  - Thereafter,  $R$  and  $S$  remain stable, while  $C=1$ , irrespective of changes in  $D$
- The invalid state of  $R = S = 0$  is never reached
- If some how  $R = S = 0$ , state immediately changes to  $R = 1$  and  $S = 0$

Transition table

$C$	$D$	$R$	$S$	$R_{\Delta}$	$S_{\Delta}$	$Q_{\Delta}$
0	—	—	—	1	1	$Q$
1	0	1	1	0	1	0
	1	1	1	1	0	1
	—	0	1	0	1	0
	—	1	0	1	0	1
	—	0	0	1	0	1



# Counters

 


State transition diagram

- \* A counter with  $k$  states is called a modulo- $k$  (mod- $k$ ) counter.
- \* A counter can be made with flip-flops, each flip-flop serving as a memory element with two states (0 or 1).
- \* If there are  $N$  flip-flops in a counter, there are  $2^N$  possible states (since each flip-flop can have  $Q = 0$  or  $Q = 1$ ). It is possible to exclude some of these states.  
→  $N$  flip-flops can be used to make a mod- $k$  counter with  $k \leq 2^N$ .
- \* Typically, a reset facility is also provided, which can be used to force a certain state to initialize the counter.





# Binary Ripple Counter (Asynchronous)

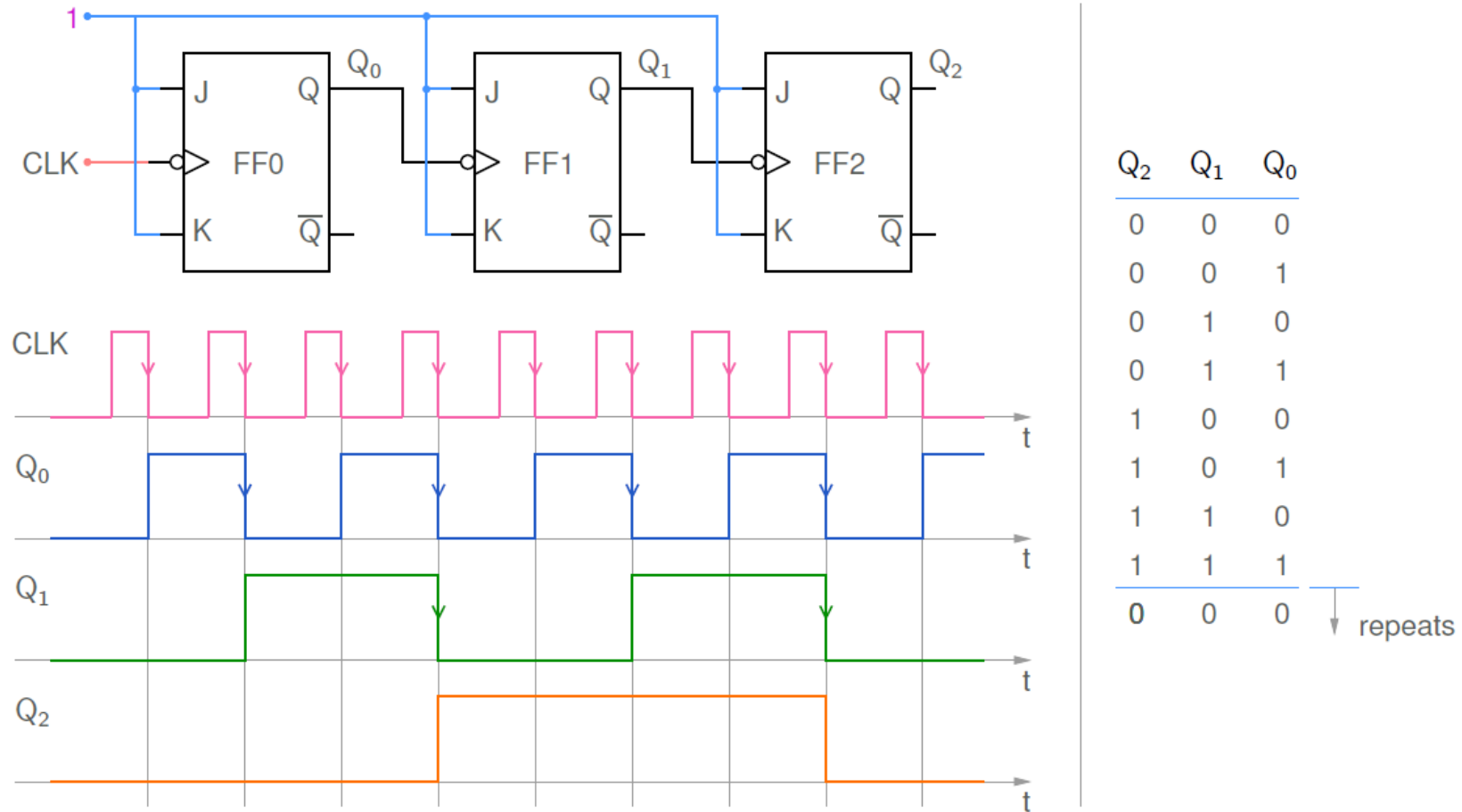


\* If positive edge-triggered flip-flops are used, we get a binary *down* counter (counting down from 111 to 000).



# Up/Down Binary Ripple Counter

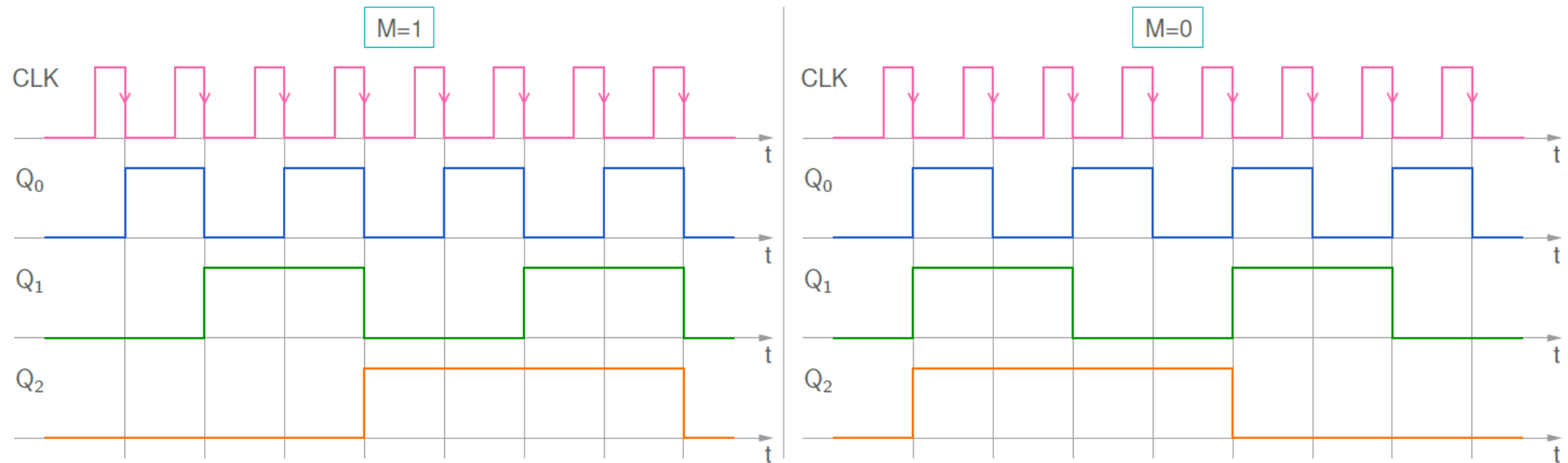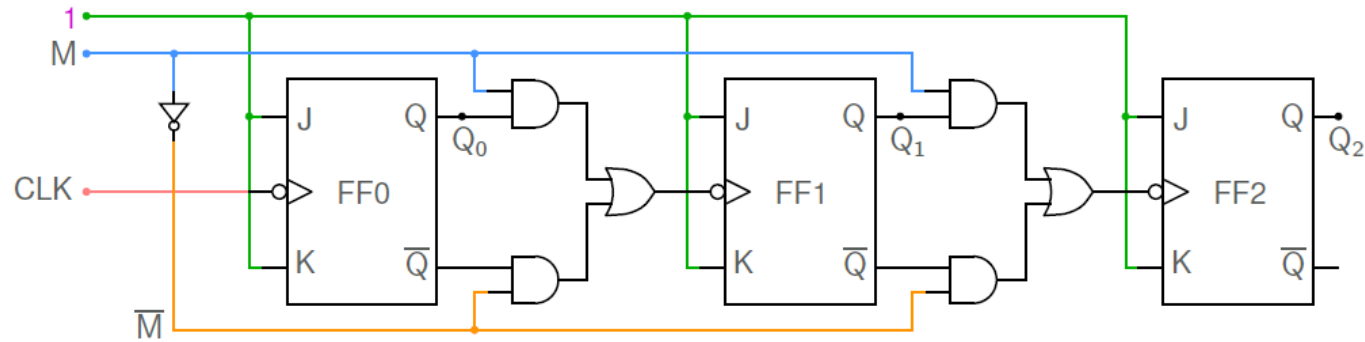

# Decade Counter

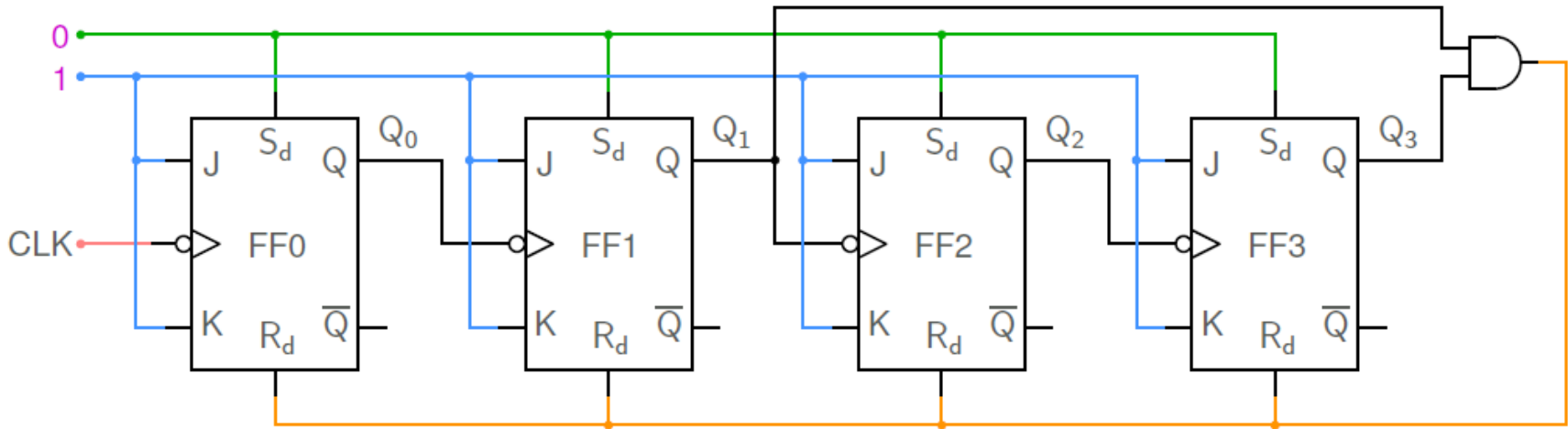


# Combination of Counters

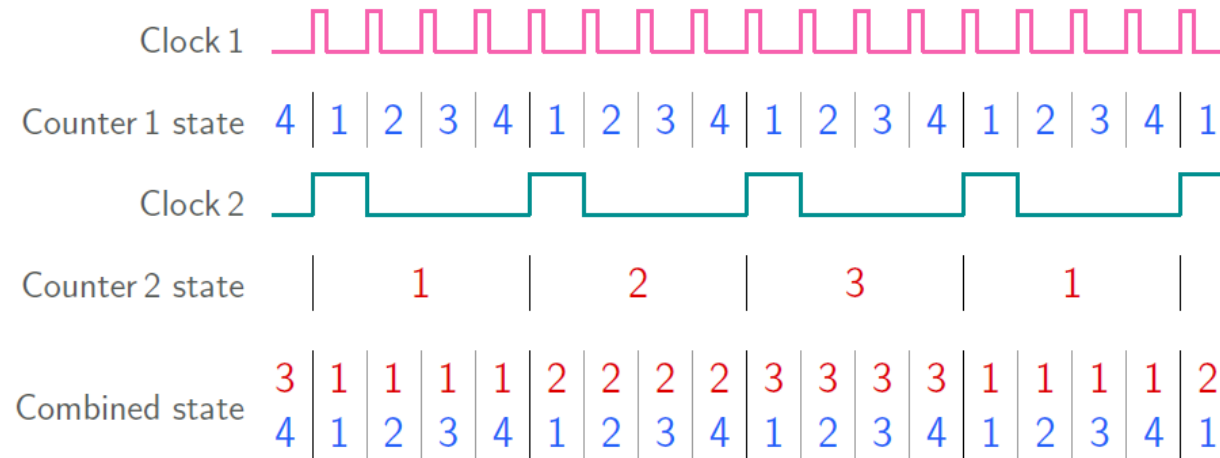 


→ the combined counter is a mod- $k_1k_2$  counter.

# Counter Applications


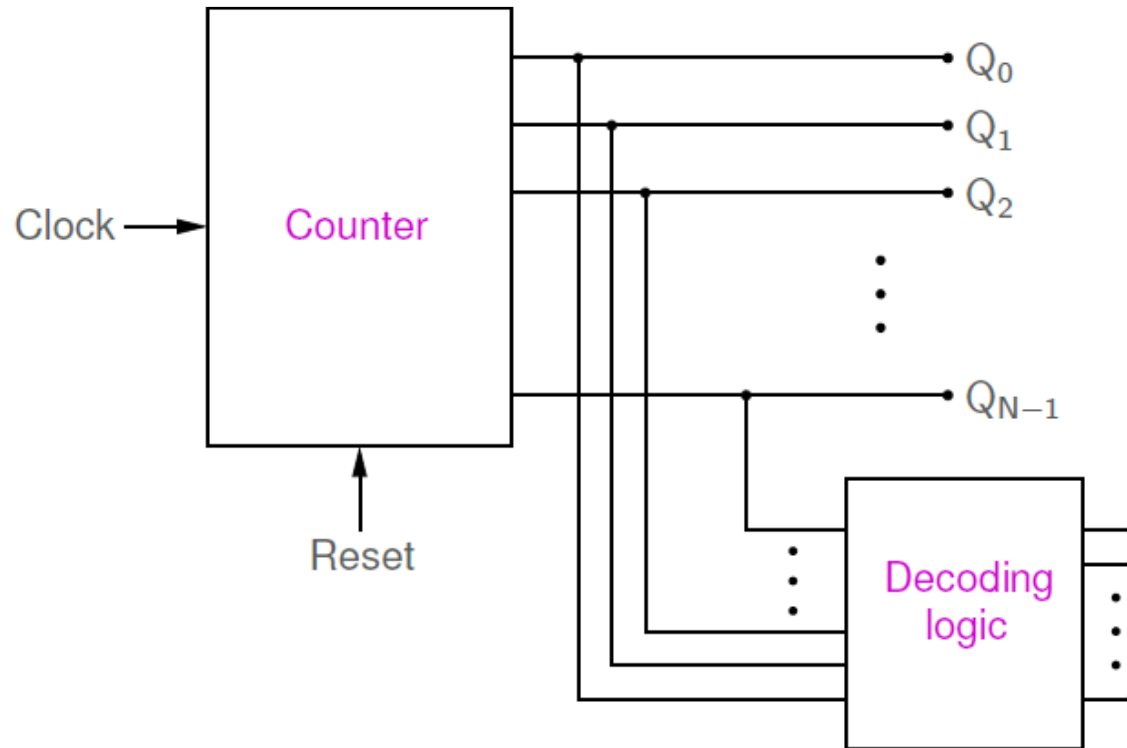


# Glitch (Temporary Undesired States)

 




# Synchronous Counters

  

# Synchronous Counter using JK Flip Flop

state	$Q_2$	$Q_1$	$Q_0$
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
1	0	0	0

↓ repeats

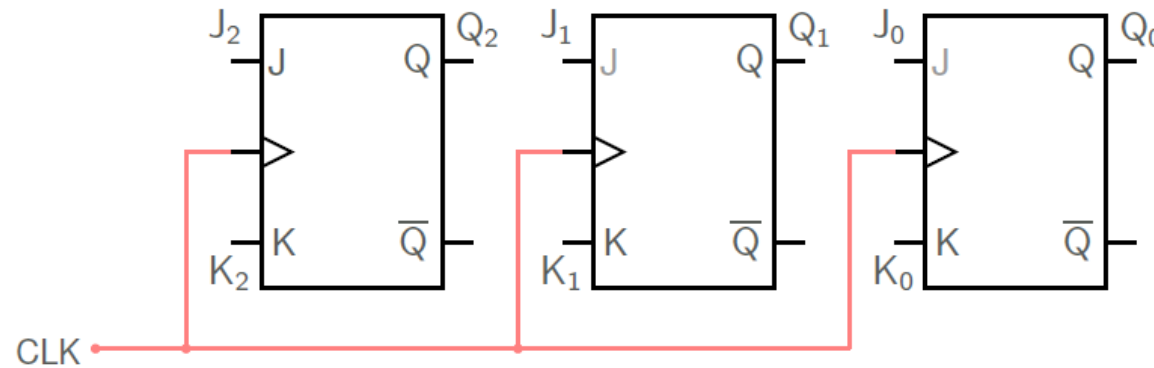

CLK	$Q_n$	$Q_{n+1}$	J	K
↑	0	0	0	X
↑	0	1	1	X
↑	1	0	X	1
↑	1	1	X	0

Design a synchronous mod-5 counter with the given state transition table.

Outline of method:

- \* State 1  $\rightarrow$  State 2 means  
 $Q_2: 0 \rightarrow 0,$   
 $Q_1: 0 \rightarrow 0,$   
 $Q_0: 0 \rightarrow 1.$
- \* Refer to the right table. For  $Q_2: 0 \rightarrow 0,$  we must have  $J_2 = 0, K_2 = X,$  and so on.

# Synchronous Counter

state	$Q_2$	$Q_1$	$Q_0$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
1	0	0	0	0	X	0	X	1	X
2	0	0	1	0	X	1	X	X	1
3	0	1	0	0	X	X	0	1	X
4	0	1	1	1	X	X	1	X	1
5	1	0	0	X	1	0	X	0	X
1	0	0	0						

$J_2$

$Q_2 Q_1$	00	01	11	10
0	0	0	X	X
1	0	1	X	X

$K_2$

$Q_2 Q_1$	00	01	11	10
0	X	X	X	1
1	X	X	X	X

$J_1$

$Q_2 Q_1$	00	01	11	10
0	0	X	X	0
1	1	X	X	X

$K_1$

$Q_2 Q_1$	00	01	11	10
0	X	0	X	X
1	X	1	X	X

$J_0$


$Q_2 Q_1$	00	01	11	10
0	1	1	X	0
1	X	X	X	X

$K_0$

$Q_2 Q_1$	00	01	11	10
0	X	X	X	X
1	1	1	X	X

$$J_2 = Q_1 Q_0, K_2 = 1, J_1 = Q_0, K_1 = Q_0, J_0 = \overline{Q_2}, K_0 = 1.$$


# Synchronous Counter

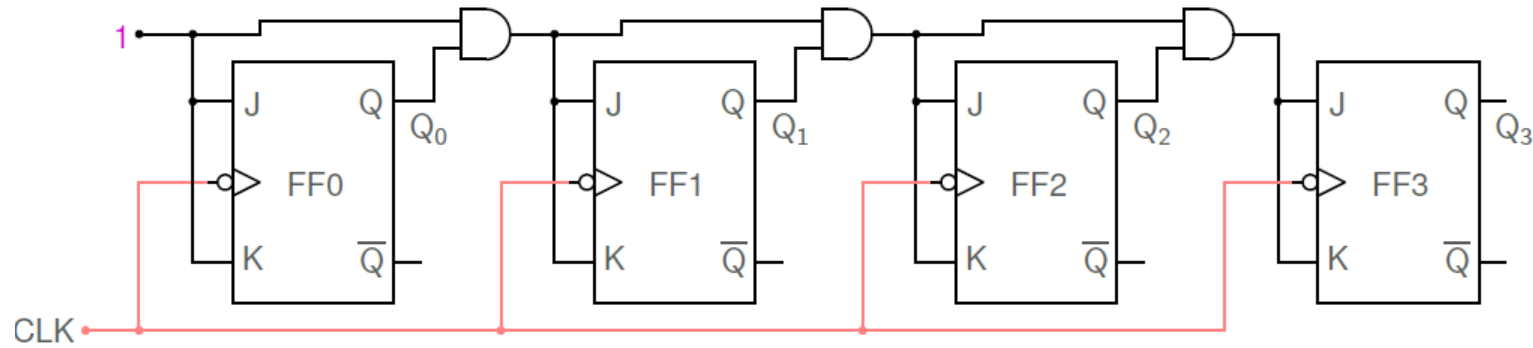


- \* Since all flip-flops are driven by the same clock, the counter is called a “synchronous” counter.
- \*  $J_0 = K_0 = 1$ ,  $J_1 = K_1 = Q_0$ ,  $J_2 = K_2 = Q_1 Q_0$ ,  $J_3 = K_3 = Q_2 Q_1 Q_0$ .
- \* FF0 toggles after every active edge.  
FF1 toggles if  $Q_0 = 1$  (just before the active clock edge); else, it retains its previous state. (Similarly, for FF2 and FF3)

# Up/Down Counter


A four-bit synchronous "up/down" counter

 



# UP Counting

 

# Down Counting

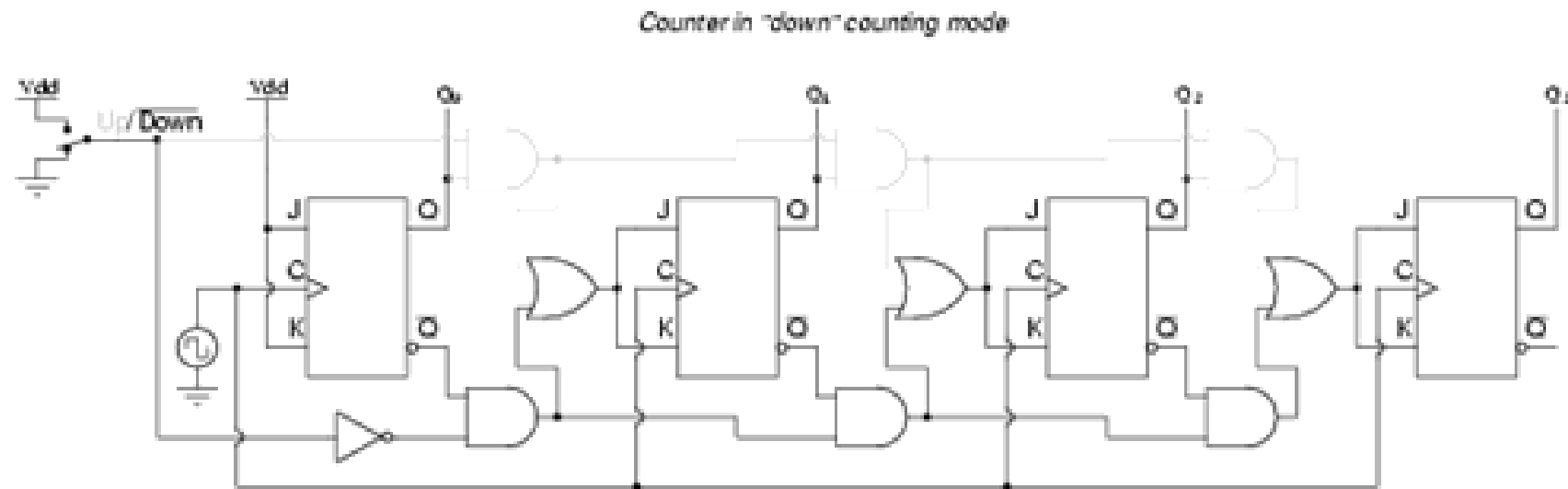

# Shift Registers

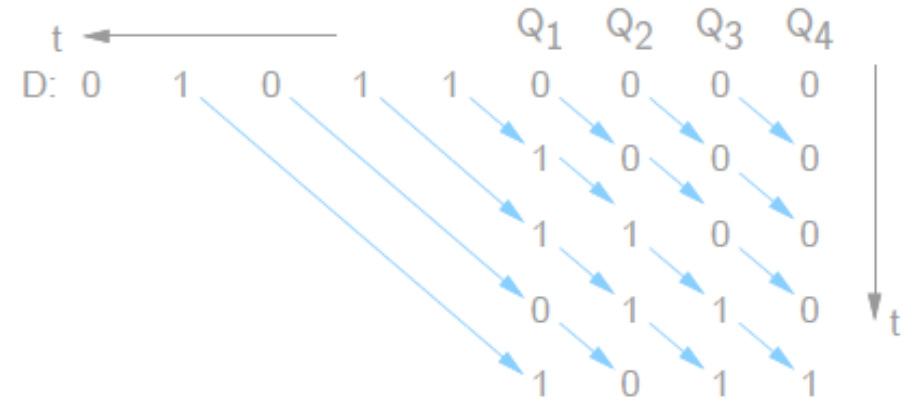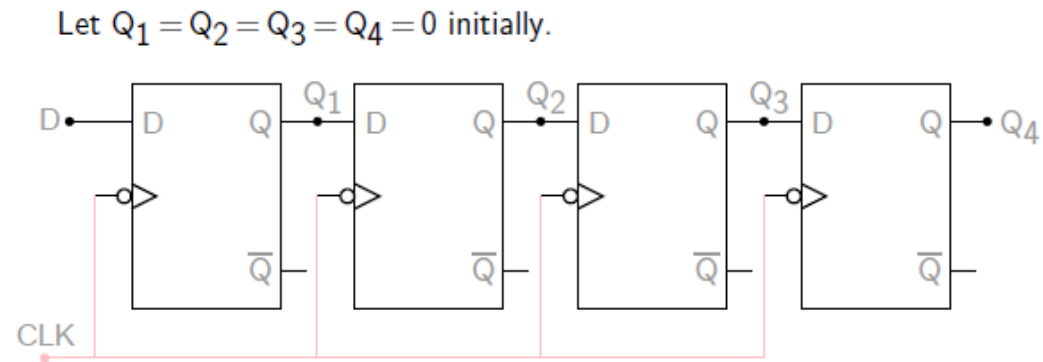


Serial In Parallel Out

Used in Computer Memory as Bit Arrays  
Converts Serial Input to Parallel Output




# Parallel In Serial Out

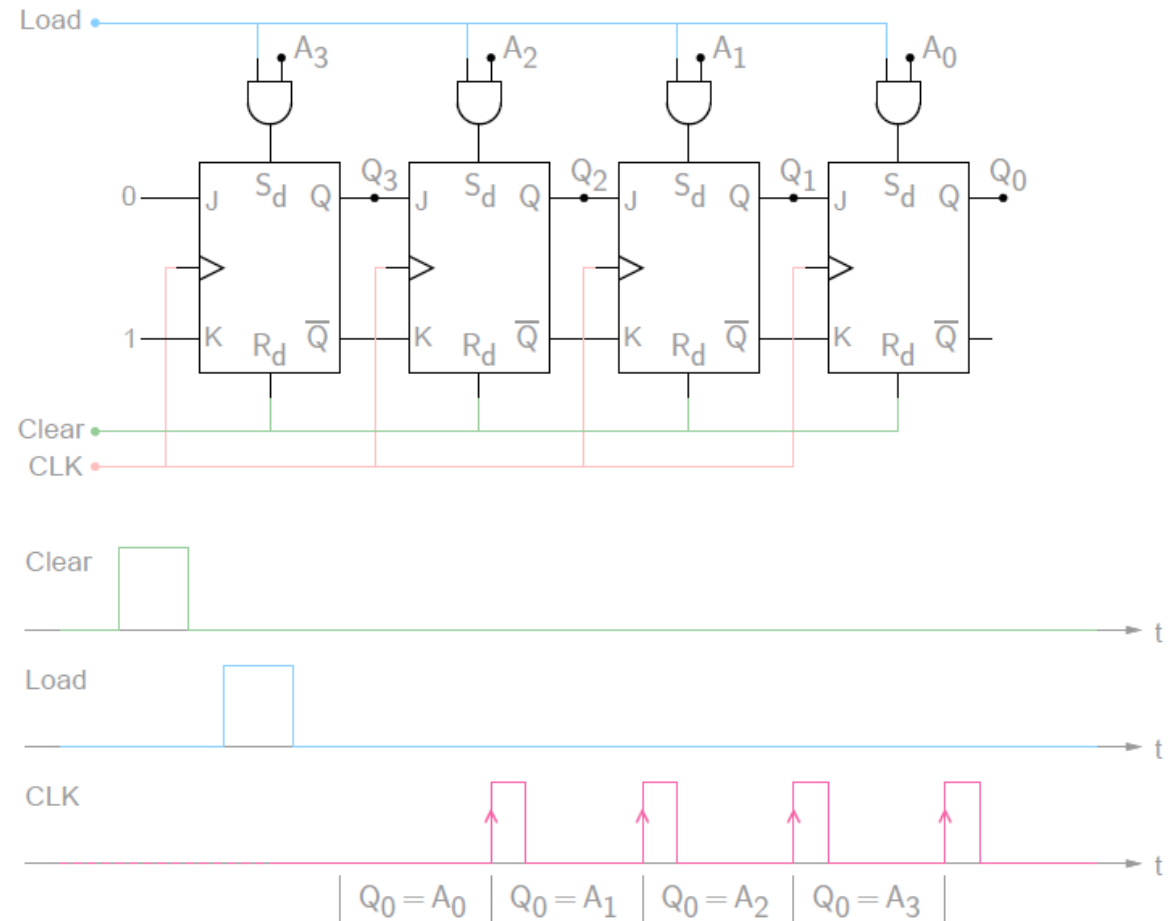

- \* All flip-flops are cleared in the beginning (with  $R_d = \text{Clear} = 1$ ,  $S_d = 0$ ).
- \* When  $\text{Load} = 1$ ,  $S_d = A_i$ ,  $R_d = 0 \rightarrow A_i$  gets loaded into the  $i^{\text{th}}$  flip-flop. (We will assume that CLK has been made 0 in this initial phase.)
- \* Subsequently, with every clock pulse, the data shifts right
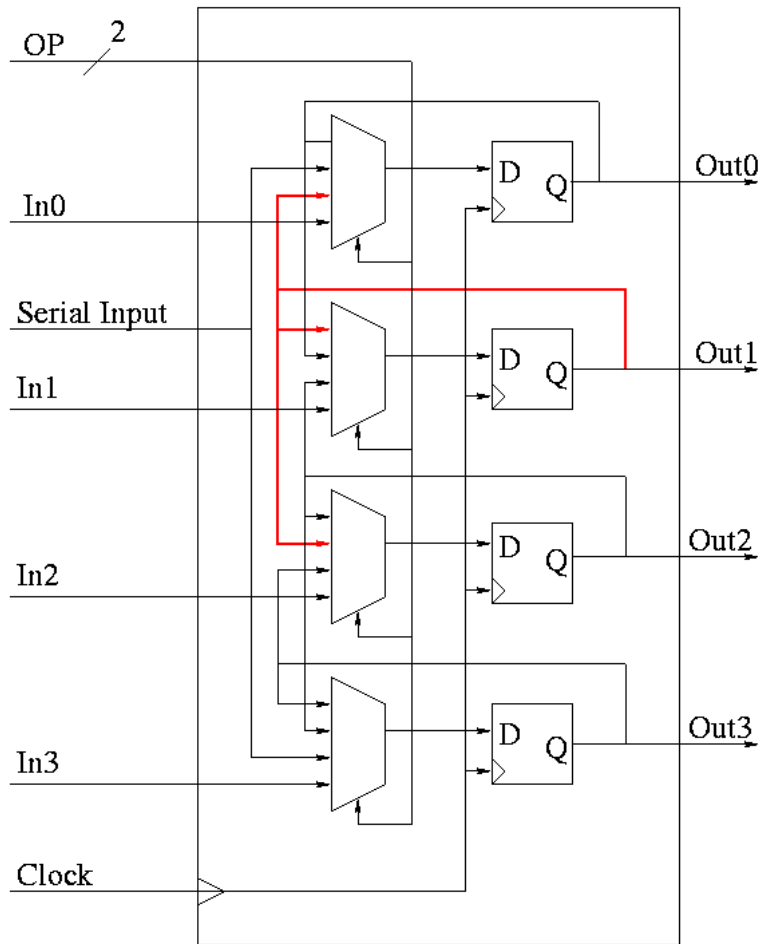
# Bidirectional Shift Register with Parallel IO



4-bit bidirectional shift register with parallel I/O

OP=00: nop   OP=01: left-shift   OP=10: right-shift   OP=11: load

# Barrel Shift/Rotate

